

⇒ Circuit Representation of De-Morgan's first theorem:-

(a) NOR Gate (b) NAND Gate ($\overline{A \cdot B}$)

De-Morgan's first theorem $\overline{A+B} = \overline{A} \cdot \overline{B}$ suggests that a logic system in which a NOT circuit follows an OR gate and is called NOT-OR or NOR gate. (shown Fig 4(a)(b)).

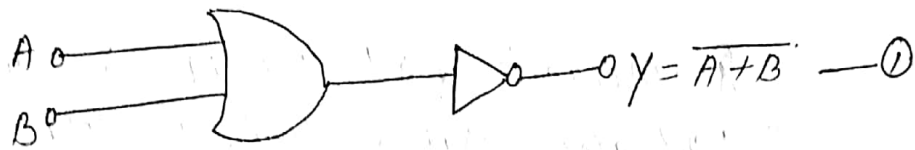


Fig 4(a) NOT-OR Gate


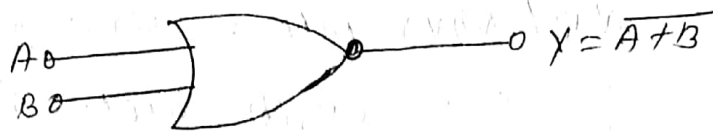


Fig 4(b) NOR-Gate

The truth table of two input NOR gate is given below:-

Input		output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

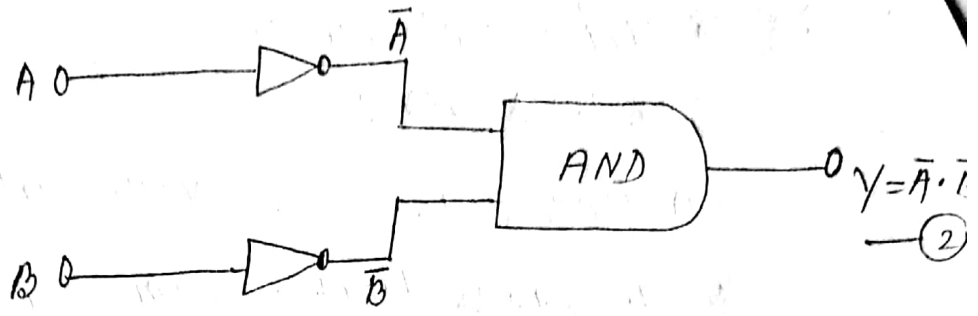(b) This NOR-gate is also equivalent to a logic system in which the inputs to an AND gate are the outputs of two NOT-circuits shown in fig 4(c).



Here Fig-4(a) & Fig-4(c) are the representation of D.M. 1st theorem.

⇒ Circuit Representation of D.M. 2nd theorem

D-Morgan's 2nd theorem is $\overline{A \cdot B} = \bar{A} + \bar{B}$. It indicates that a logic system in which NOT ckt. follows an AND gate is called NAND gate or NOT-AND gate. shown in fig. 5(a), (b) which is equivalent to a logic.

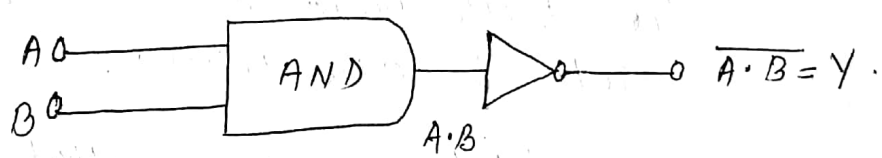


Fig-5(a).


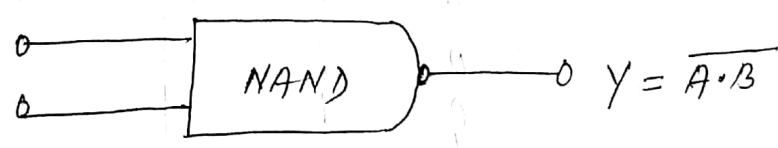


Fig-5(b).

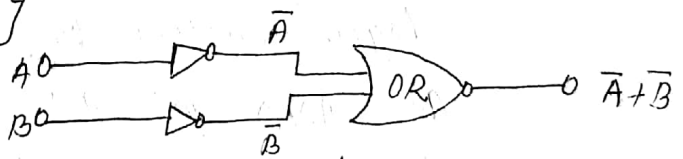System in which the inputs of an OR gates are the outputs from two NOT ckt's [shown in fig-5(c)]



The truth table of NAND gate is shown below:-

inputs		output	input		output
A	B	$Y = A \cdot B$			
0	0	1	1	0	0
0	1	0	1	1	0
1	0	0	0	0	1
1	1	1	0	1	1