

Ex-3. show that

- (i) $A + \bar{A} = 1$
- (ii) $(A + B)(\bar{A} + C) = AC + \bar{A}B$
- (iii) $AB + AC + B\bar{C} = AC + B\bar{C}$

Ans:- (i) putting, $A=0$; $A + \bar{A} = 0 + \bar{0} = 0 + 1 = 1$
 putting, $A=1$; $A + \bar{A} = 1 + \bar{1} = 1 + 0 = 1$ proved.
 $\therefore A + \bar{A} = 1$ proved.

(ii) This identity can be proved by finding the truth tables for the left and right hand representation (as below).

A	B	C	\bar{A}	$A+B$	$\bar{A}+C$	$(A+B)(\bar{A}+C)$	AC	$\bar{A}B$	$AC + \bar{A}B$
0	0	0	1	0	1	0	0	0	0
0	0	1	1	0	1	0	0	0	0
0	1	0	1	1	1	1	0	1	1
0	1	1	1	1	1	1	0	1	1
1	0	0	0	1	0	0	0	0	0
1	0	1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0	0	0
1	1	1	0	1	1	1	1	0	1

$\therefore (A+B)(\bar{A}+C) = AC + \bar{A}B$

(iii) show that, $AB + AC + B\bar{C} = AC + B\bar{C}$.
 For this expression truth Table II is given below:-

A	B	C	\bar{C}	AB	AC	$B\bar{C}$	$AB + AC + B\bar{C}$	$AC + B\bar{C}$
0	0	0	1	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	1	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0
1	0	1	0	0	1	0	1	1
1	1	0	1	1	0	1	1	1
1	1	1	0	1	1	0	1	1

Hence;
 $AB + AC + B\bar{C} = AC + B\bar{C}$
 proved

⇒ Q-1 An AND gate is followed by a NOT gate using two inputs A & B find the Boolean expⁿ for the output (C).

Ans:- The AND-gate followed by NOT gate is shown in fig. 7.

As A & B are the two inputs of the AND gate, its output is AB

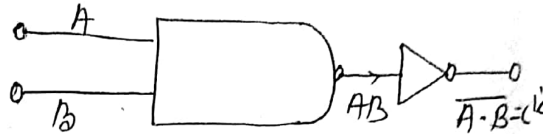


Fig. 7.

which is the input of a NOT gate. Hence output of (AND-NOT) gates = $C = \overline{AB}$.

⇒ Q-2. Show how an OR-gate & an AND-gate can be constructed with NAND-gate.

see before fig. 6(b) & 6(c) for AND-gate & fig. 6(d) for OR-gate.

⇒ Explain how an OR-gate may be constructed with AND and NOT gates:-

Since AND-gate followed by NOT-gate gives a NAND gate and by using 3 NAND-gates as shown in fig. 6(d) OR gate can be constructed.

⇒ Ex-Change the logic CKT fig. 8. into a simple OR

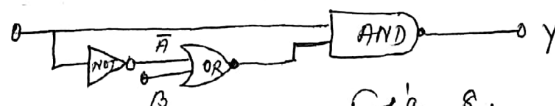


Fig. 8.

A is the input of AND-gate and NOT-gate. Hence \bar{A} & B are the inputs of OR-gate. The output of OR-gate is therefore $\bar{A} + B$. This output is the another input of AND-gate whose output is $Y = A(\bar{A} + B)$.

This is modified as,

$A(\bar{A} + B) = A\bar{A} + AB = AB$ ($A\bar{A} = 0$)
 AB gives an AND gate with two inputs A & B shown as in fig 9.



Fig. 9.