
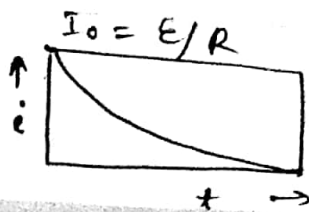
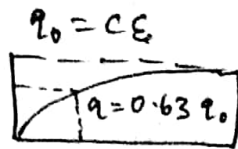


Eqn ① a fig show the charge of a capacitor at any time to reach maximum value

06

May Thursday 127-239

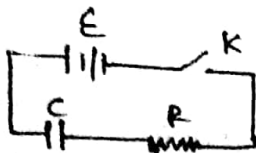

Since when  $t=0$ ,  $q=0$ , hence

const =  $-C \log_e \frac{E-q}{E}$  and therefore

$$\log_e \left( \frac{E-q}{E} \right) = -\frac{t}{CR} + \log_e E$$

$$\therefore \log_e \frac{E-q}{E} = -\frac{t}{CR}$$

$$\frac{E-q}{E} = e^{-t/CR}$$

$$q = CE(1 - e^{-t/CR}) = q_0(1 - e^{-t/CR})$$

07 19 WEEK

May Friday 128-238

where  $q_0 = CE =$  maximum charge across with the capacity.

The current

$$i = \frac{dq}{dt} = \frac{CE}{CR} e^{-t/CR} = \frac{E}{R} e^{-t/CR}$$

The current and charge are therefore both exponential functions of time. At a time  $t = RC$ , the current has decreased to  $1/e^{\text{th}}$  of its initial value. The prod

$RC$  is known as the time constant or the relaxation time of the circuit. It is the time taken for the capacitor to acquire 63% of its maximum charge

M	T	W	T	F	S	S	M	T	W	T	F	S	S	M	T	W	T	F	S
					1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
17	18	19	20	21	22	23	24	25	26	27	28	29	30	31					