

CHARGING :

A Capacitor C may be charged or discharged through a resistor R.

a battery of emf  $\mathcal{E}$ , capacitor C and a resistor R in series. charging is done by connecting

If  $i$  is the instantaneous value of current at an instant  $t$  through R, the potential difference across the capacitor will be  $\mathcal{E} - Ri$ .

If  $q$  is the instantaneous charge on the capacitor at this instant  $t$ , then we have

$$\mathcal{E} - Ri = q/c$$

$$\text{or } \mathcal{E} - q/c = Ri$$

Since  $i = \frac{dq}{dt}$ , hence

$$\mathcal{E} - \frac{q}{c} = R \frac{dq}{dt}$$

$$\text{or } \frac{dq}{\mathcal{E} - q/c} = \frac{dt}{R}$$

On integrating, assuming  $\mathcal{E}$  and C as constants, we get

$$-C \log_e (\mathcal{E} - q/c) = t/R + \text{const.}$$

M	T	W	T	F	S	S	M	T	W	T	F	S	S	M	T	W	T	F	S	S
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21
22	23	24	25	26	27	28	29	30												