

26

July Monday

GROUPING OF RESISTANCE

31 WEEK

208-158

8

1. Series connection:

9

10

11

12

1

2

3

4


5

6

Evening

If same current flows through different resistances, then they are said to be connected in series. The figure represents the series connection of resistances. For two resistances in series, we have.

$$R_s = R_1 + R_2$$

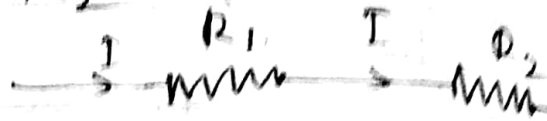

Clearly,

$R_s > R_1$; and also

$R_s > R_2$. As a matter

27

July Tuesday

31 WEEK

209-157

8

9

10

11

12

1

2

3

4

5

6

Evening

of fact the equivalent resistance in series connection is equal to the sum of the individual resistances.


Also, due to series connection of resistances, the conductance, current and the load on the cell (if the voltage supply is constant) will decrease, whereas as resistance of the circuit will increase.

2) Parallel Connection: Figure below

represents parallel connection of two resistances. Resistances are said to be in parallel to each other if same

September 04

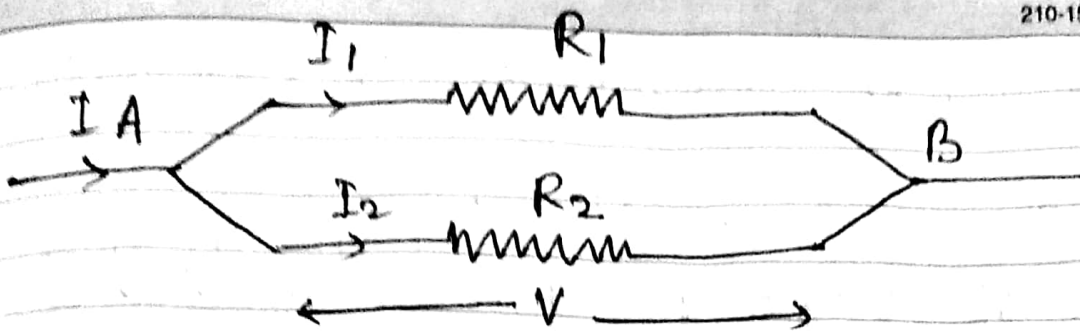exists also. For two resistances in parallel, we have,



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\text{or, } R_p = \frac{R_1 R_2}{R_1 + R_2}$$

In this case clearly $R_p < R_1$ and also $R_p < R_2$. Therefore, when the resistances are connected in parallel then conductance, current and the load on the cell (if voltage supply is constant) increases whereas as the resistance of the circuit decreases.

Also, we have,

$$V_A - V_B = I_1 R_1 = I_2 R_2$$

$$\therefore \frac{I_2}{I_1} = \frac{R_1}{R_2}$$

It can also be proved that

$$I_1 = \frac{R_2}{R_1 + R_2} I ; \text{ and}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$