

POWER IN AN AC CIRCUIT

May 24
Monday
145-221
WEEK 22

The rate of doing work or the activity of a current, in the case of a steady current, is given by VI . In an alternating current both V and I vary harmonically and differ in phase. If $v = V_0 \sin \omega t$ is the applied emf across the circuit at any instant t and the corresponding current is given by $i = I_0 \sin(\omega t - \phi)$, where ϕ is the phase difference between the emf and the current. If emf and current are in volts and amperes respectively, then the instantaneous power in watts is given by

May 25
Tuesday
146-220
WEEK 22

$$vi = V_0 I_0 \sin \omega t \sin(\omega t - \phi)$$

$$= V_0 I_0 \left[\sin^2 \omega t \cos \phi - \frac{1}{2} \sin 2\omega t \sin \phi \right]$$

The mean rate of doing work or the average power,

$$P = \frac{1}{T} \int_0^T vi dt = \frac{1}{2} V_0 I_0 \cos \phi$$

$$= \frac{V_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cos \phi$$

$$= \text{Virtual volts} \times \text{Virtual amperes} \times \cos \phi \quad \text{--- (1)}$$

Where the term $\cos \phi$ is known as power factor.

If i is said to be leading v if current leads voltage, lagging if current lags voltage.