

Four Layer P-N-P-N Switching Devices

(Shockley Diode)

Lecture – 2

TDC PART – II

Paper - III (Group - A)

Chapter - 4

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L. S. College, BRA Bihar University,
Muzaffarpur.**

Four Layer P-N-P-N Switching Devices (Shockley Diode)

Lecture – 2

TDC PART – II

Paper - III (Group - A)

Chapter - 4

- **P-N-P-N Diode or Shockley Diode**
- **Lecture Content :-**
 - **(1) Basic Introduction**
 - **(2) Introduction to Shockley Diode**

P-N-P-N Diode or Shockley Diode

■ Basic Introduction

- The **SCR** is a **Four Layer (P-N-P-N)** structure that effectively blocks the current through two terminals until it is **Turn ON** by a small signal at a third terminal. There are many varieties of the basic **P-N-P-N** structure, and we shall not attempt to cover all of them; however, we can discuss the basic operation and physical mechanisms involved in the devices.

- We shall begin by investigating the current flow in a **Two-Terminal P-N-P-N Device** and then extend the discussion to include triggering by a third terminal. We shall see that the **P-N-P-N Structure** can be considered for many purposes as a combination of **PNP and NPN Transistors**; before discussing the control of an **SCR** using a third terminal, it is important to understand the basic transistor action at work in a **P-N-P-N Structure**. Therefore, in this section we analyze the four-layer **P-N-P-N Structure** with only **Two Terminals**.


- In this Lecture, we will learn about **P-N-P-N Diode or Shockley Diode**. Even though it is not available commercially (production stopped in 1950's) and it is not particularly useful, the model technique of **P-N-P-N Diode or Shockley Diode** is very useful in creating other types of **Thyristors** like **SCR, DIAC and TRIAC** etc.

- **Shockley Diode** is the first member of **Thyristor family** devices and it is named after the inventor **William Bradford Shockley**. Once we understand this basic operation of **Shockley Diode**, we will easily understand the next concepts covered in **Thyristors like SCR, DIAC and TRIAC** etc. Let us know about the **P-N-P-N Diode or Shockley diode** working and applications.


Introduction to Shockley Diode

- The Shockley Diode or P-N-P-N Diode is a Four Layer (P-N-P-N), Two Terminals (namely Anode (A) and Cathode (K)) Semiconductor Switching Device. It is also called as Four Layer Diode. It functions like a normal diode without any trigger inputs, in Reverse Biased condition, no Current flows through it and in Forward Biased condition Current flows through it when the voltage across it is more than the Break-over Voltage of it.

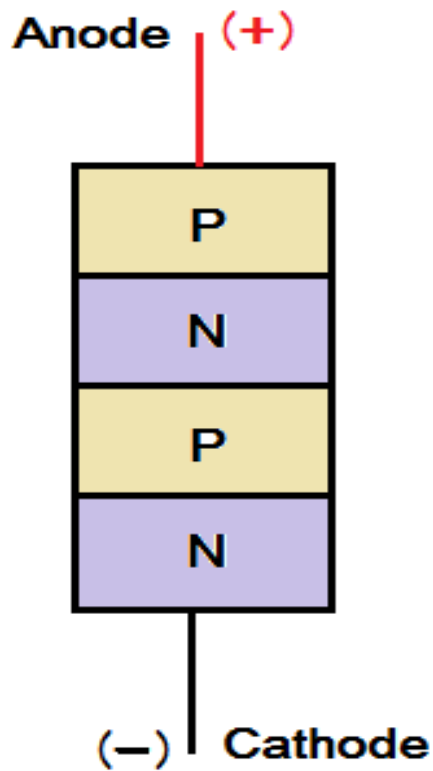- These **Shockley Diodes** have only **Two States**, either **ON** or **OFF** that's why these are classified as a **Thyristors**. The **Basic Construction** and **Circuit Symbol** of the **Four Layer P-N-P-N Shockley Diode** are shown in below **Figure (1)**.




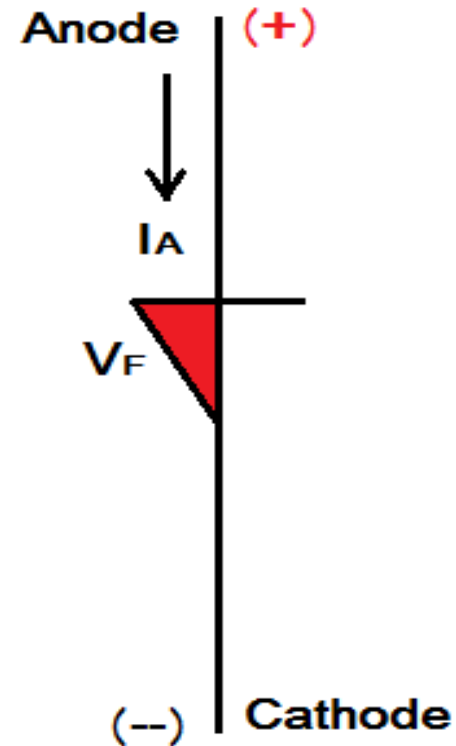
A Two Terminal PNPN Diode Basic Construction



A Two Terminal PNPN Diode Circuit Symbol

- Fig (1) Shown Basic Construction and Circuit Symbol of a Four Layer P-N-P-N Shockley Diode

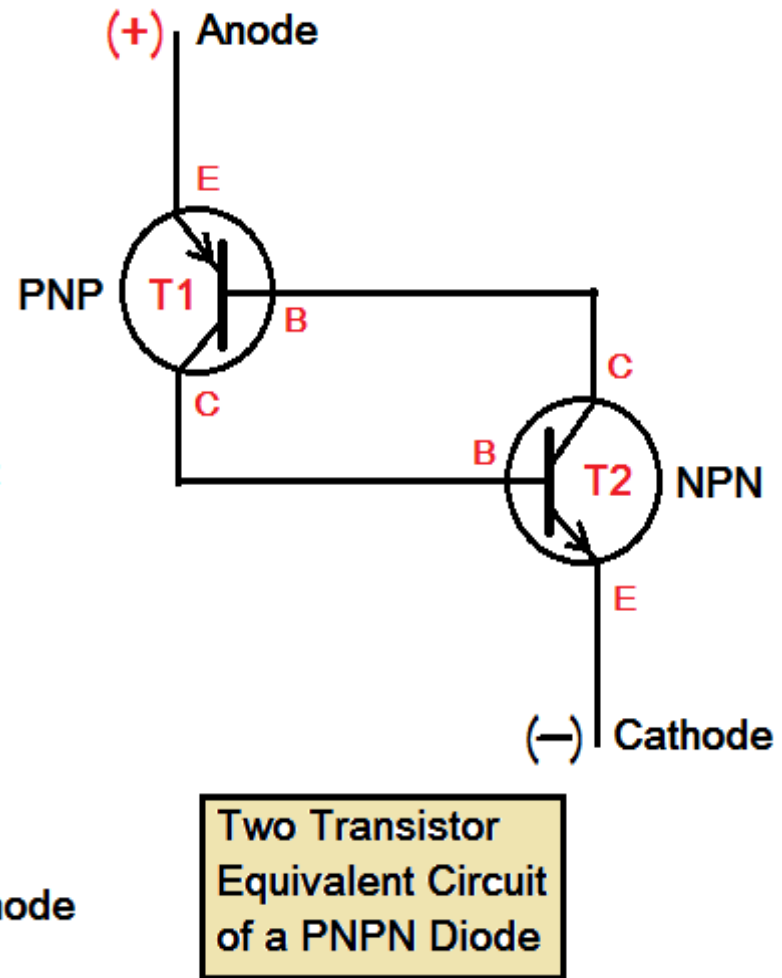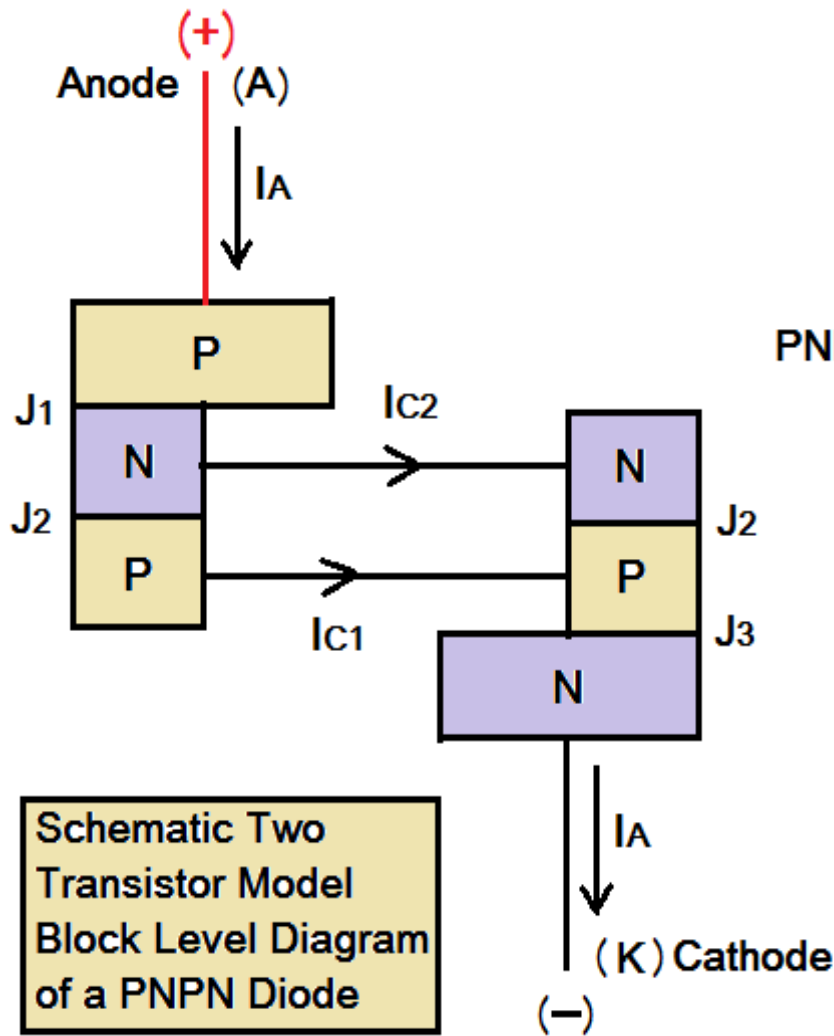- The construction of this **Diode** is simple: it is constructed by joining the **Four Layers** to form **P-N-P-N Junction**. Two Transistor Model Block Diagram and Two Transistors Equivalent Circuit of a Four Layer **P-N-P-N** Shockley Diode is shown in above **Figure (2)** where in the collector of a **Transistor T1** is connected to the **Base of Transistor T2**.



- **Fig (2) Shown Two Transistor Model Block Diagram and Two Transistor Equivalent Circuit of a Four Layer P-N-P-N Shockley Diode**

- The Junction J1 is formed at the Emitter Base Junction of Transistor T1, Junction J2 is at common connected Base Collector Junction between Transistor T1 and T2, and the Junction J3 is at Base Emitter Junction of Transistor T2. Therefore, as the Base Emitter Junctions, J1 and J3 must be Forward Biased and as a Collector Base Junction, J2 must be Reverse Biased for linear operation.

to be continued