

Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

Lecture – 3

TDC PART – II

Paper - III (Group - A)

Chapter - 4

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L.S. College, BRA Bihar University,
Muzaffarpur.**

Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

Lecture – 3

TDC PART – II

Paper - III (Group - A)

Chapter - 4

- (Uni Junction Transistor)
- Lecture Content :-
 - UJT Parameters
 - (1) Inter- Base Resistance (R_{BB})

UJT Parameters


(1) Inter Base Resistance (R_{BB})

- The Total Resistance of the Silicon Bar i.e., the Resistance between Terminals B1 and B2 with Emitter (E) Terminal open i.e. when Emitter Current $I_E = 0$, called as Inter-Base Resistance (R_{BB}).

- It is the **Resistance** between (**Base2**) **B2** and (**Base1**) **B1** *i.e.* it is the **Total Resistance** of the **Silicon Bar** from one end to the other with **Emitter (E) Terminal** open *i.e.* When **Emitter Current** $I_E = 0$. **Inter Base Resistance (R_{BB})** shown in below **Figure (9)**. In simple words, it is the **Resistance** of the **N-type Bar** when measured **Lengthwise**.

■ If R_{B1} is the **Resistance** of the **Bar** from **Emitter (E)** to **Base1 (B1)** and R_{B2} is the **Resistance** of the **Bar** from **Emitter (E)** to **Base2 (B2)**. From the **Simplified Equivalent Circuit** of UJT shown in below **Figure (10)**, it is seen that **UJT Inter-Base Resistance (R_{BB})** can be expressed as,

■ $R_{BB} = R_{B2} + R_{B1}$

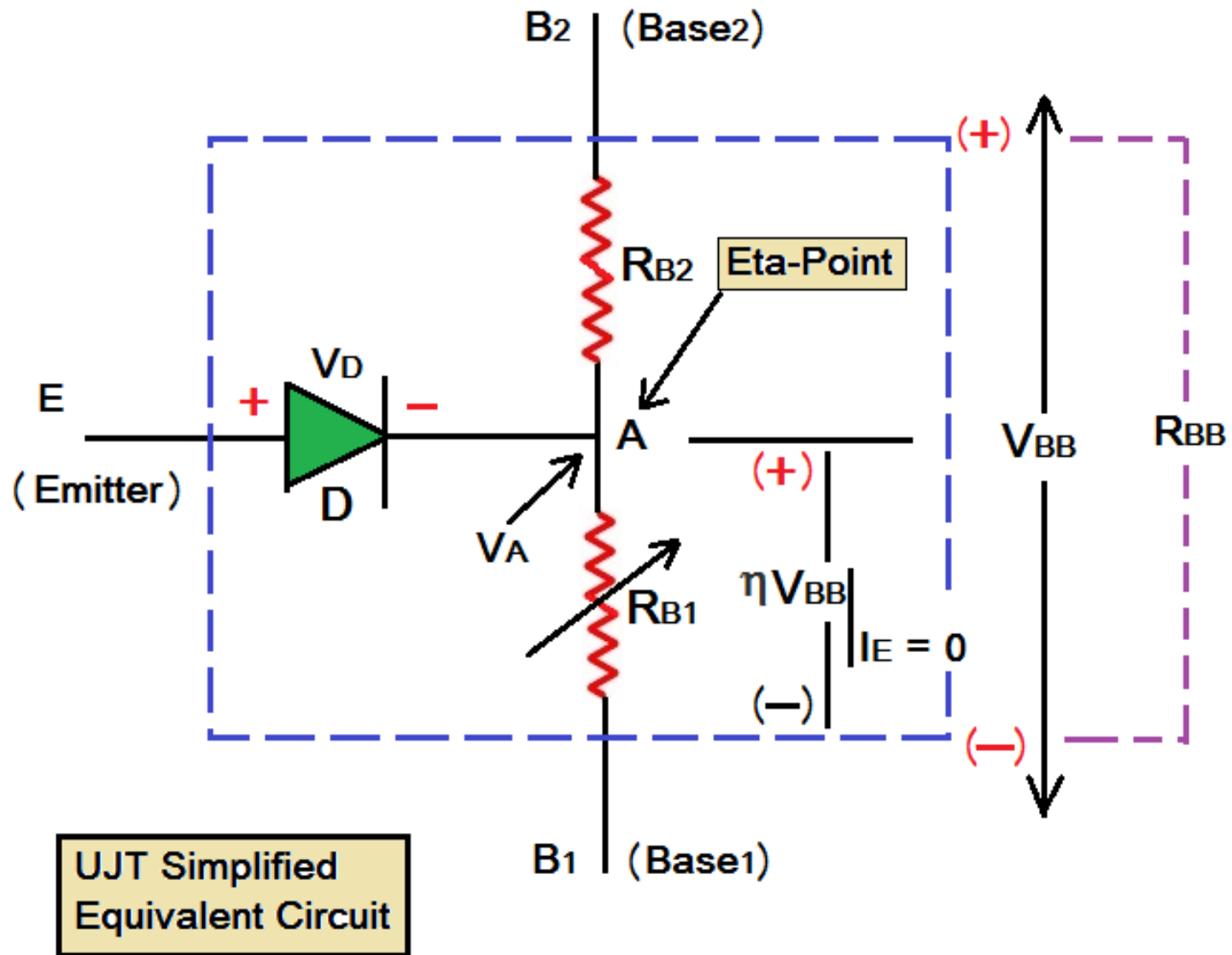

■ Fig (10) Shown UJT Simplified Equivalent Circuit Diagram with Voltage Divider.

- Where R_{B2} is the Resistance of Silicon Bar between $B2$ and the point at which Emitter Junction Lies and R_{B1} is the Resistance of Silicon Bar between $B1$ and Emitter Junction. The Resistance R_{B1} is variable because its value depends upon the Biasing Voltage (V_{BB}) across P-N Junction.

- It should also be noted that **Point A** also called **“Eta-Point”** is such that $R_{B1} > R_{B2}$. Usually, $R_{B1} = 60\%$ of R_{BB} . The Resistance R_{B1} has been shown in above **Figure (10)** act as a **Variable Resistor** because its value depends upon the **Bias Voltage (V_{BB})** across **P-N Junction** and varies inversely as **Emitter Current I_E** . The typical range of **Inter Base Resistance $R_{BB} = R_{B1} + R_{B2}$** is from **4K Ω** to **10K Ω** .

to be continued