

# **Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)**

## **Lecture – 7**

**TDC PART – II  
Paper - III (Group - A)  
Chapter - 4**

**by:**

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,  
Muzaffarpur.**

# Four Layer P-N-P-N Switching Devices (Uni Junction Transistor)

## Lecture – 7

TDC PART – II

Paper - III (Group - A)

Chapter - 4

- (Uni Junction Transistor)
- Lecture Content :-
  - UJT Parameters
  - (4) Theory of UJT Operation

# UJT Parameters

## ■ (4) Theory of UJT Operation

- Initially imagine that the **Emitter Supply Voltage** is turned down to **Zero** then  $V_E$  is **Zero**. Then the **Intrinsic Stand-off Voltage**, **Reverse-Biases** the **Emitter Diode D**. If  $V_D$  is the **barrier voltage** of the **Emitter Diode D**, hence some **Reverse Emitter Current  $I_E$**  flows until, the value of  $V_E$  reaches a point at which
- $V_E = \eta V_{BB}$

- This is the point where the curve touches the **Y-axis** then the total **Reverse Bias Voltage  $V_E$**  is

- $V_E = V_A + V_D$

- When  $V_{BB}$  is **Switched ON**,  $V_A$  is developed and **Reverse-Biases the Junction**. If (**Silicon Diode Forward Voltage drop**)  $V_D$  is the barrier voltage of the **P-N Junction**, then total **Reverse Bias Voltage  $V_E$**  is

- $V_E = V_A + V_D$

■ From Lecture – 5 and equation (5),

■  $V_A = \eta V_{BB}$ , then we get


■  $V_E = \eta V_{BB} + V_D$

■ Value of  $V_D$  for Si is **0.7 V**.

■  $V_E = \eta V_{BB} + V_D$

■  $V_E = \eta V_{BB} + 0.7 \text{ V}$

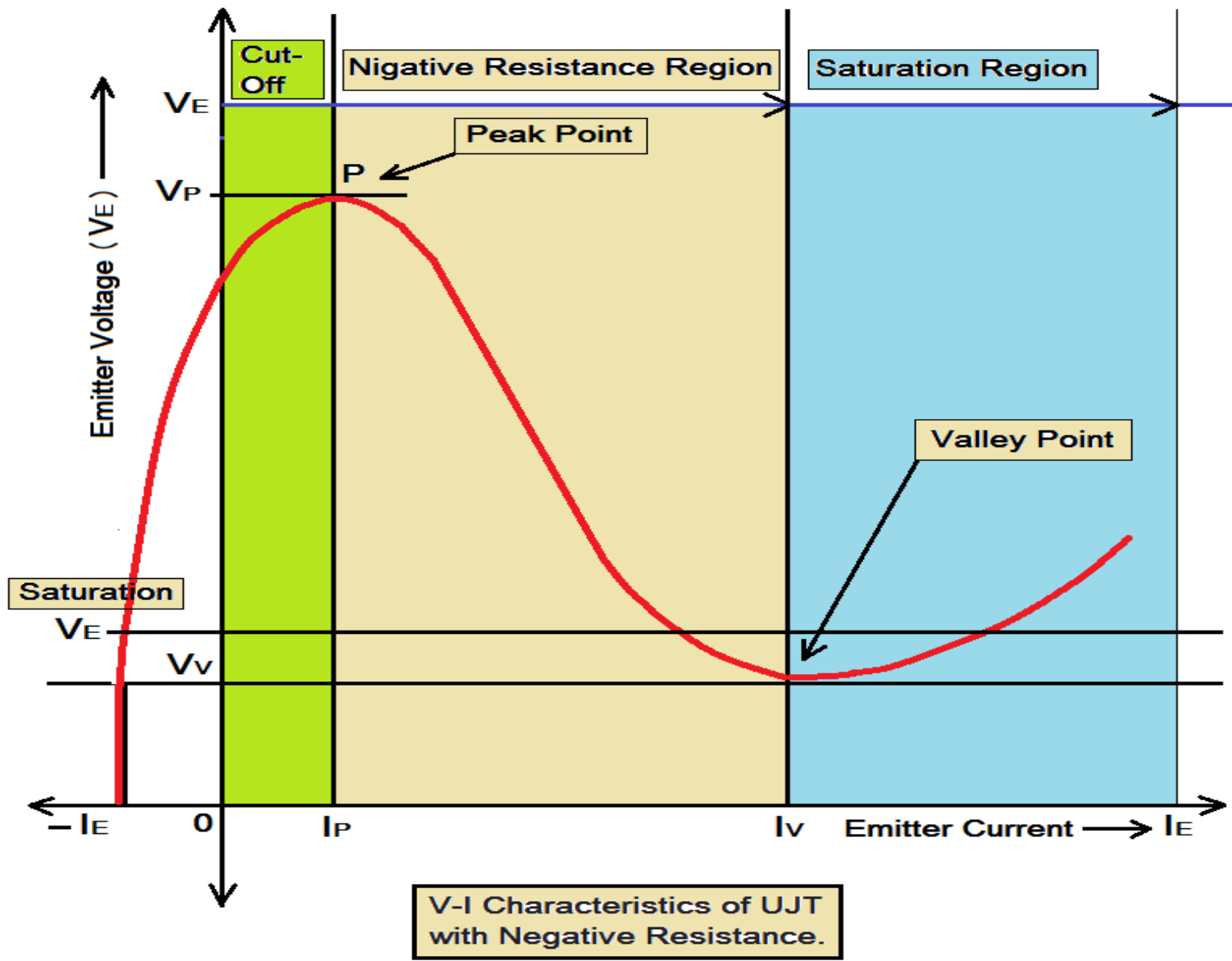- It is obvious that **Emitter Junction** will not become **Forward-Biased** unless its applied voltage  $V_E$  exceeds  $(\eta V_{BB} + V_D)$  or  $V_E = \eta V_{BB} + 0.7 V$ . This value of  $V_E$  is called **Peak-Point Voltage  $V_P$**  which is shown in below **Figure (16)**.



■ Fig (16) Shown V-I Characteristics of UJT with Negative Resistance.

- When  $V_E = V_P$ , Emitter Peak Current  $I_P$  starts to flow through  $R_{B1}$  to ground (i.e.  $B_1$ ). The UJT is then said to have been Fired or **Turned ON**. Due to the flow of  $I_E (= I_P)$  through  $R_{B1}$ , number of charge carriers in  $R_{B1}$  is Increased which **Reduces** its Resistance. As  $\eta$  depends on  $R_{B1}$ , its value is also **Decreased**.



- Hence, we find that as  $V_E$  and hence  $I_E$  **Increases** (beyond  $I_P$ ),  $R_{B1}$  **Decreases**,  $\eta$  **Decreases** and  $V_A$  **Decreases**. This **Decrease** in  $V_A$  causes more **Emitter Current** to flow which causes a further **Reduction** in  $R_{B1}$ ,  $\eta$  and  $V_A$ . Obviously, the process is **Regenerative**;  $V_A$  as well as  $V_E$  quickly drops as  $I_E$  **Increases**. Since,  $V_E$  **Decreases** when  $I_E$  **Increases** the UJT Possesses **Negative Resistance**.

- Beyond the **Valley Point  $V_v$** , UJT is in **Saturation Region** and  $V_E$  **Increases Very Little** with an **Increasing  $I_E$** . It is seen that only **Terminals E and B1** are the active terminals whereas **B2** is the bias terminal i.e. it is meant only for applying external voltage across the **UJT**.

- Generally, **UJT** is triggered into conduction by applying a **suitable Positive Pulse** at its **Emitter Terminal E**. It can be brought back to **OFF State** by applying a **Negative Trigger Pulse**. **Three other important Parameters for the UJT** is  **$I_P$ ,  $V_V$  and  $I_V$**  and is defined below:

- **Peak-Point Emitter Current. ( $I_P$ )** : - It is the Emitter Current at the Peak Point. It represents the Minimum Current that is required to trigger the device (UJT). It is Inversely Proportional to the Inter-Base Voltage  $V_{BB}$ .

- **Valley Point Voltage ( $V_v$ )** :- The Valley Point Voltage is the Emitter Voltage at the Valley Point. The Valley Voltage **Increases** with the **Increase** in Inter-Base Voltage  $V_{BB}$ .

- **Valley Point Current ( $I_V$ )** :- The Valley Point Current is the Emitter Current at the Valley Point. It **Increases** with the **Increase** in Inter-Base Voltage  $V_{BB}$ .

**to be continued .....**