

Silicon Controlled Rectifier (SCR)

Lecture – 19

TDC PART – I

Paper - II (Group - B)

Chapter - 5

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L.S. College, BRA Bihar University,
Muzaffarpur.**

Silicon Controlled Rectifier (SCR)

Lecture – 19

TDC PART – I

Paper - II (Group - B)

Chapter - 5

- **SCR Turning-OFF Methods (PART – 7)**
- **Lecture Content :-**
 - **(2) Forced Commutation**
 - **(IV) Class-D Commutation - (Impulse Commutation)**


(IV) Class-D Commutation - (also Known as Impulse Commutation or Auxiliary Commutation)

- Class-D Commutation is a Commutation method used to **Turn OFF SCR (thyristor) in a DC circuit** by the application of a sudden **Reverse Voltage across the terminals of SCR**. This is the reason, it is also called **Impulse Commutation**.

- A **Class-D Commutation** circuit consists of **Main SCR (thyristor) T₁, Auxiliary Thyristor T_A, Capacitor C, Diode D and Inductor L.** **Load Current I_L** is assumed to be constant throughout the discussion. Let us consider the commutation circuit shown in **Figure (94)** below for better understanding. Reference direction of capacitor current and capacitor voltage is shown in **Figure (94)**.

- **Figure (94)** shows the **Class-D Commutation** circuit diagram which consists of two SCR (thyristor) such as main SCR (thyristor) T_1 and Auxiliary SCR (thyristor) T_A , Inductor L , Diode D and a Commutation Capacitor C . The Main SCR (thyristor) T_1 and Load Resistor R_L act as a **Power Circuit** but Inductor L , Diode D and Auxiliary SCR (thyristor) T_A are used to form the **Commutation Circuit**.

- **Figure (94)** shows the typical **Class-D Commutation Circuit**. In this commutation method, an **Auxiliary SCR (thyristor) T_A** is required to commutate the **Main SCR (thyristor) T_1** , Assuming ideal **SCRs (thyristors)** and the lossless components, then the **waveforms** are as shown in **Figure (98)**. Here, **Inductor L** is necessary to ensure the correct polarity on **Capacitor C** . **Main SCR (thyristor) T_1** and **Load Resistance R_L** form the power circuit, whereas **Inductor L** , **Diode D** and **Auxiliary SCR (thyristor) T_A** form the commutation circuit.

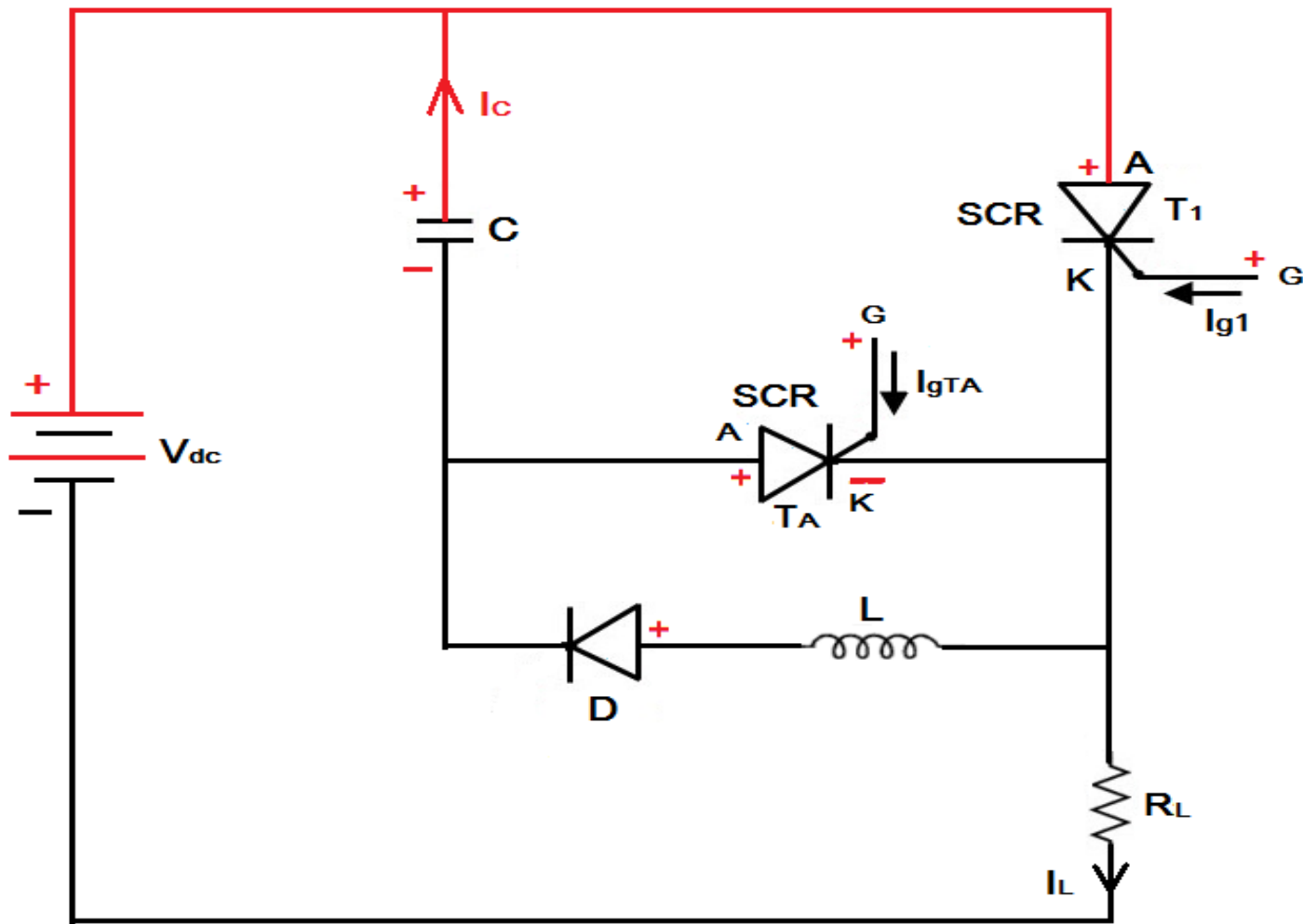

Class-D
Commutation

- Fig (94) Shown the Class-D Commutation Circuit Diagram which consists of two SCRs, one Capacitor, one Inductor and one Diode .

Circuit Operations :-

■ **MODE - 0 [Initial Operation] :-**

■ Initially when the **Battery V_{dc}** is connected, the **DC Voltage V_{dc}** is applied to circuit, the **SCRs (thyristors) T1 and TA** are in **OFF-State**. There is no current Flow through DC supply and commutation circuit as both **SCRs (thyristors) T1 and TA** are **OFF**. Hence, initially, the state / conditions of the circuit components **T1 and TA** and **Capacitor C** may be represented by,

- T1 is in OFF State,
- TA is OFF State and
- $V_c = 0$

MODE - 1 :-


- Initially, the triggering pulse is applied to **Auxiliary SCR (thyristor) T_A** , **SCR (thyristor) T_A** will be **Turned ON** and **Capacitor C** gets **charged** with the polarity shown in **Figure (95)** below. . The **Capacitor Charging Current (I_c)** flows through the path,

- $V_{dc+} - C+ - C- - T_A - R_L - V_{dc-}$

- As soon as **Capacitor C** is fully charged to V_{dc} , the **Auxiliary SCR (thyristor) T_A** Turns OFF. This is due to the fact that, as the **voltage across the Capacitor C** increases gradually, the **current flow through the Auxiliary SCR (thyristor) T_A** decreases slowly since **Capacitor C and Auxiliary SCR (thyristor) T_A** form the series circuit.

■ Hence in this **MODE – 1 Operation**, as shown in **Figure (95)** below, the **State / Conditions** of circuit components **T₁** and **T_A** and **Capacitor C** may be represented by,

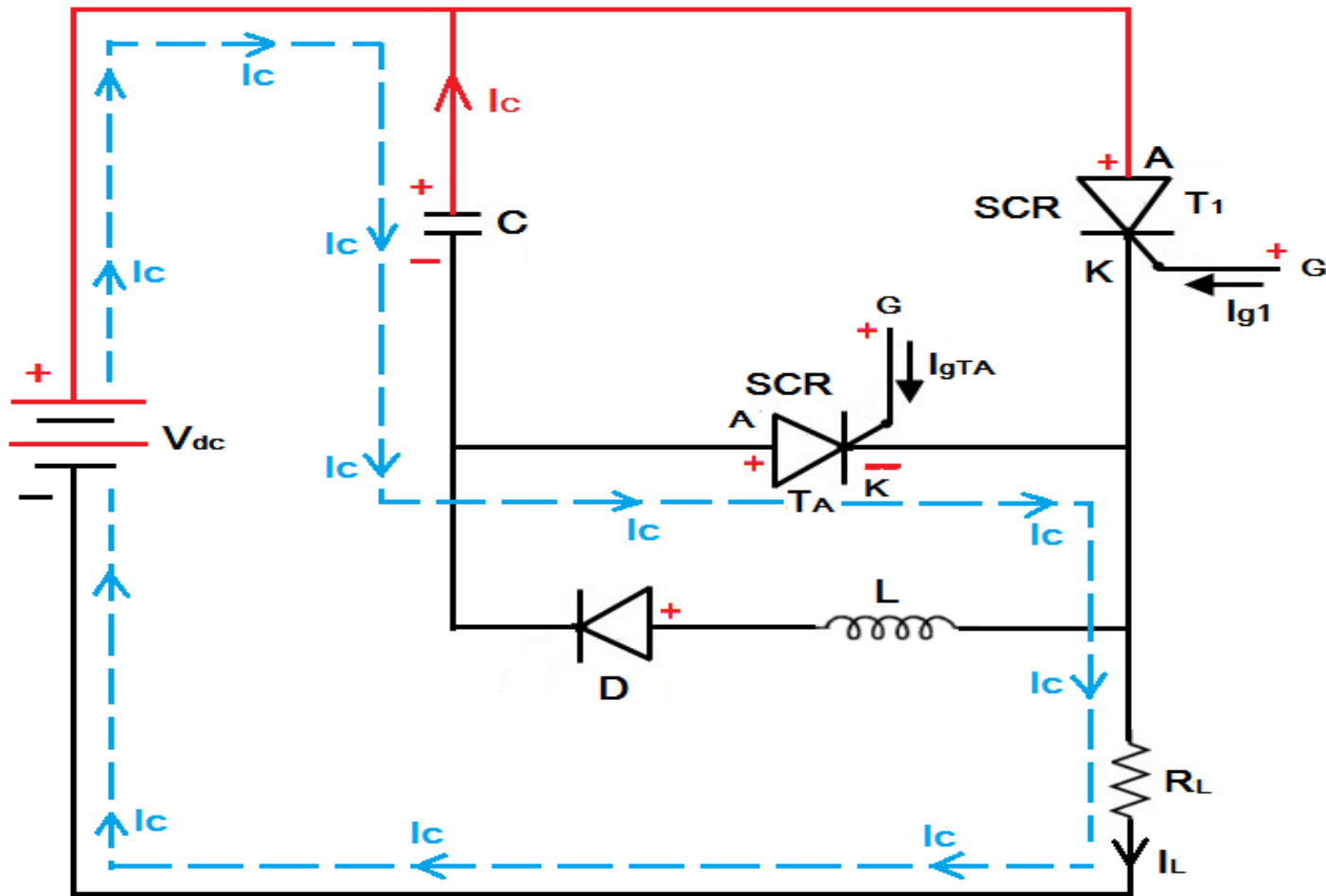- **T₁** is in **OFF State**,
- **T_A** is **OFF State** and
- **V_C = V_{dc}**



Class-D
Commutation


- **Fig (95)** Shown the **Class-D Commutation** Simplified Circuit Diagram which consists of two SCRs and one Capacitor C with SCR T_1 is in OFF State and SCR T_A is OFF State.

MODE - 2 :-

- When the triggering pulse is applied to **Main SCR (thyristor) T₁**, the current flows in two different paths,
- (a) The **Load Current I_L** follows through the following path,
- $V_{dc+} - T_1 - R_L - V_{dc-}$

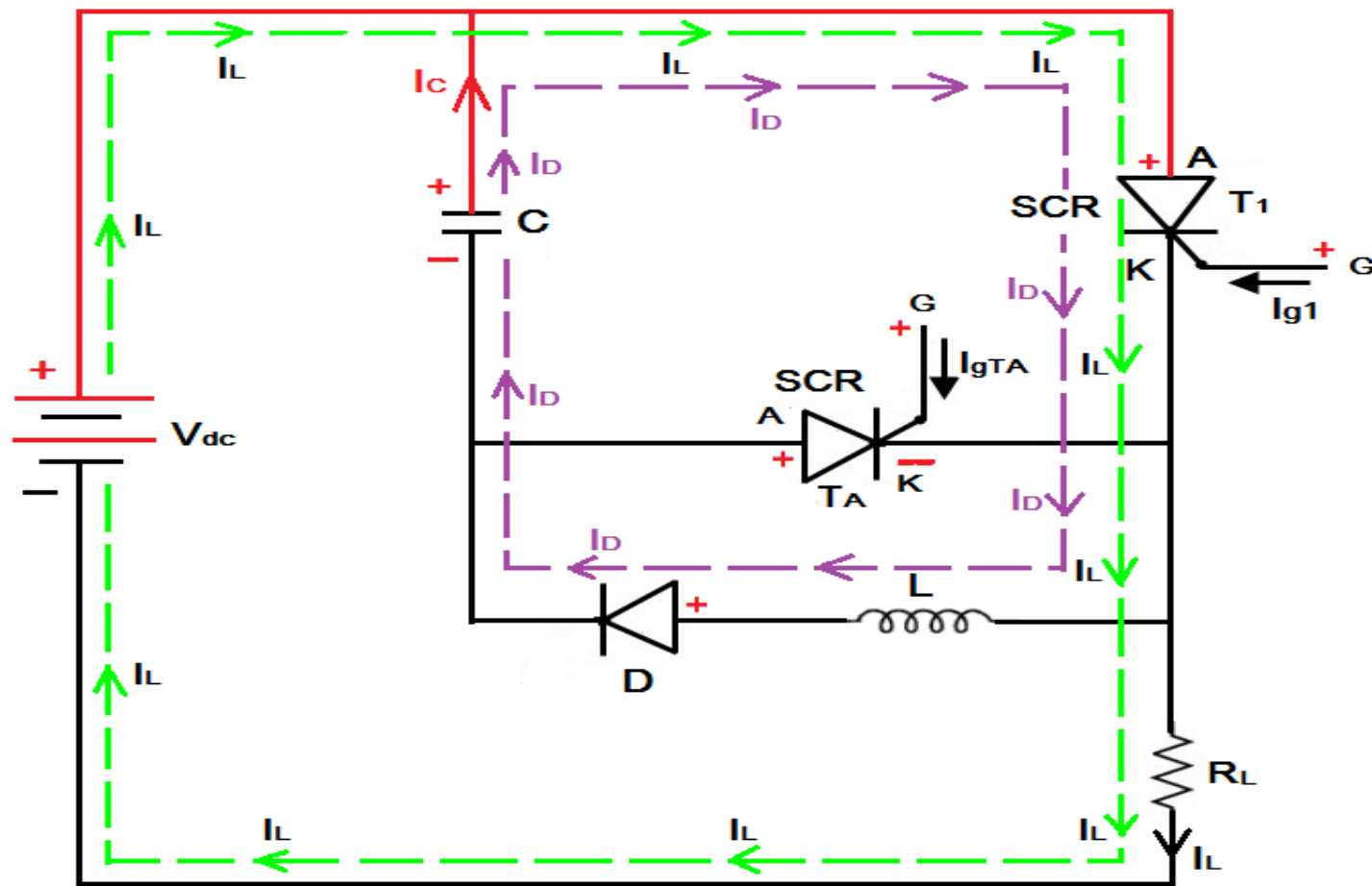- (b) and **Commutation Current (Capacitor-Discharges Current) (I_D)** flows through the following path,
 - **$C^+ - T_1 - L - D - C^-$**
- After the **Capacitor C** has completely discharged, its polarity will be reversed, i.e., its **Upper Plate** will acquire **Negative Charge** and the **Lower Plate** will acquire, **Positive Charge**. Reverse discharge of **Capacitor C** will not be possible due to presence of blocking **Diode D**.

- Therefore, at the end of **Mode – 2 Operation**, as shown in **Figure (96)** below, the **State / Condition** of the circuit components **T1** and **TA** and **Capacitor C** may be represented by,
 - **T1** is in **ON** State,
 - **TA** is in **OFF** State and
 - $V_C = -V_{dc}$



Class-D
Commutation


- **Fig (96)** Shown the **Class-D Commutation** Simplified Circuit Diagram which consists of two SCRs, one Capacitor, Inductor, and a Diode with SCR T_1 is in ON State and SCR T_A is in OFF State.

MODE - 3 :-

- In this mode, whenever the **Auxiliary SCR** (thyristor) T_A is triggered and **Turned ON**, **Capacitor C** starts to **discharge** through the following path,

- $C+ - T_{A(A-K)} - T_1(k-A) - C-$

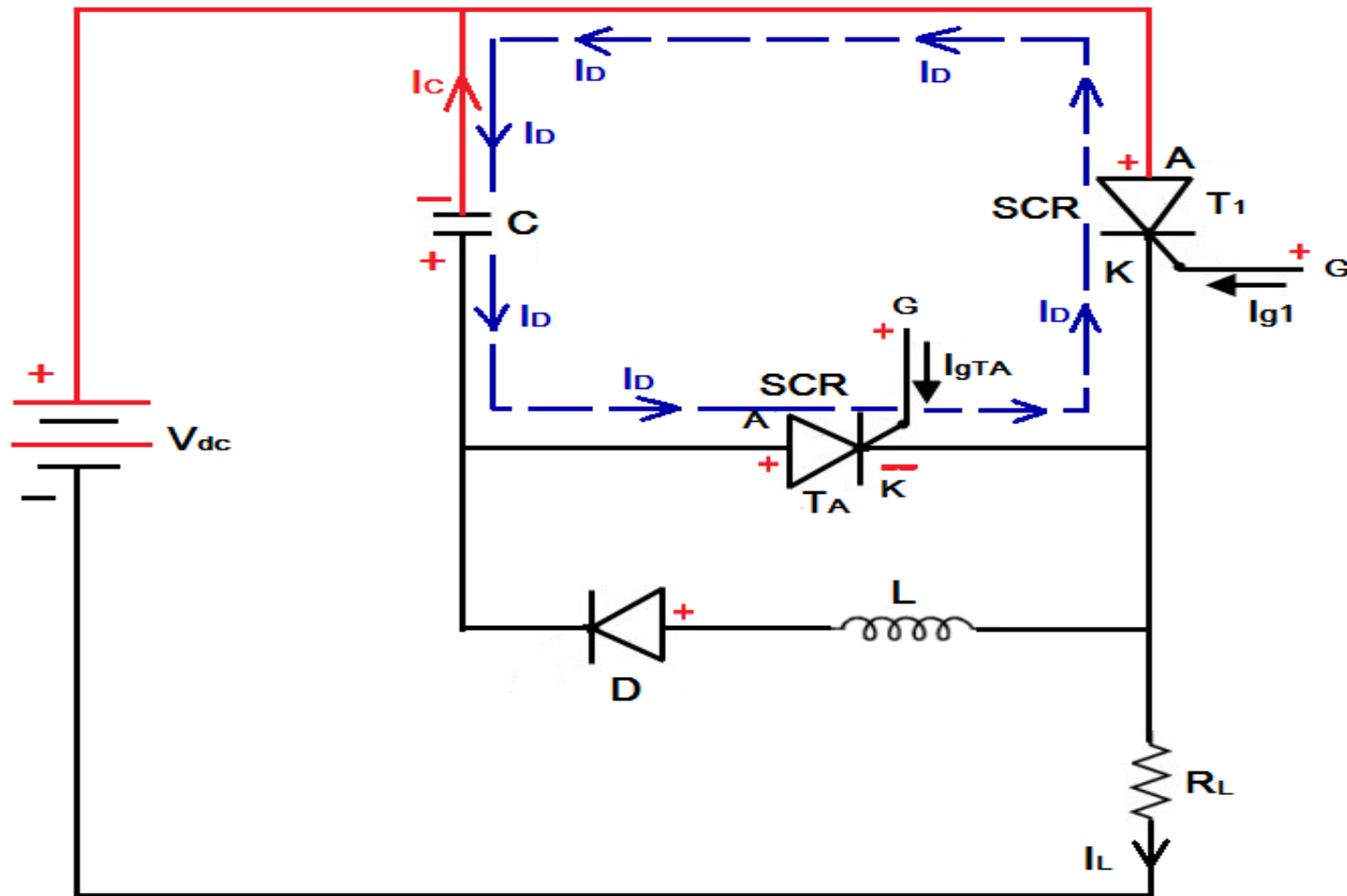
- When this **Commutation Current (Discharging Current of Capacitor C) (I_D)** becomes more than the **Load Current I_L** , SCR (thyristor) **T1** gets **Turned OFF**.
- Therefore, at the end of **Mode – 3 Operation**, as shown in **Figure (97)** below, the **State / Condition** of circuit component **T1** and **T_A** becomes,
 - **T1** is in **OFF State** and
 - **T_A** is **OFF State**



Class-D
Commutation

- **Fig (97)** Shown the **Class-D Commutation** Simplified Circuit Diagram which consists of two SCRs, one Capacitor, Inductor, and a Diode with SCR T_1 is in OFF State and SCR T_A is in OFF State.

- Again, Capacitor C will charge to the Supply Voltage V_{dc} with the polarity as shown in **Figure (95)** and hence Auxiliary SCR (thyristor) T_A gets Turned OFF. Therefore, SCRs (thyristors) T_1 and T_A both get Turned OFF, which is equivalent to Mode - 0 operation. Since the Commutation Energy rapidly transfers to the load, high efficiency is possible in **Class-D Commutation**. This Commutation is most commonly used in **Jones Chopper Circuit**.

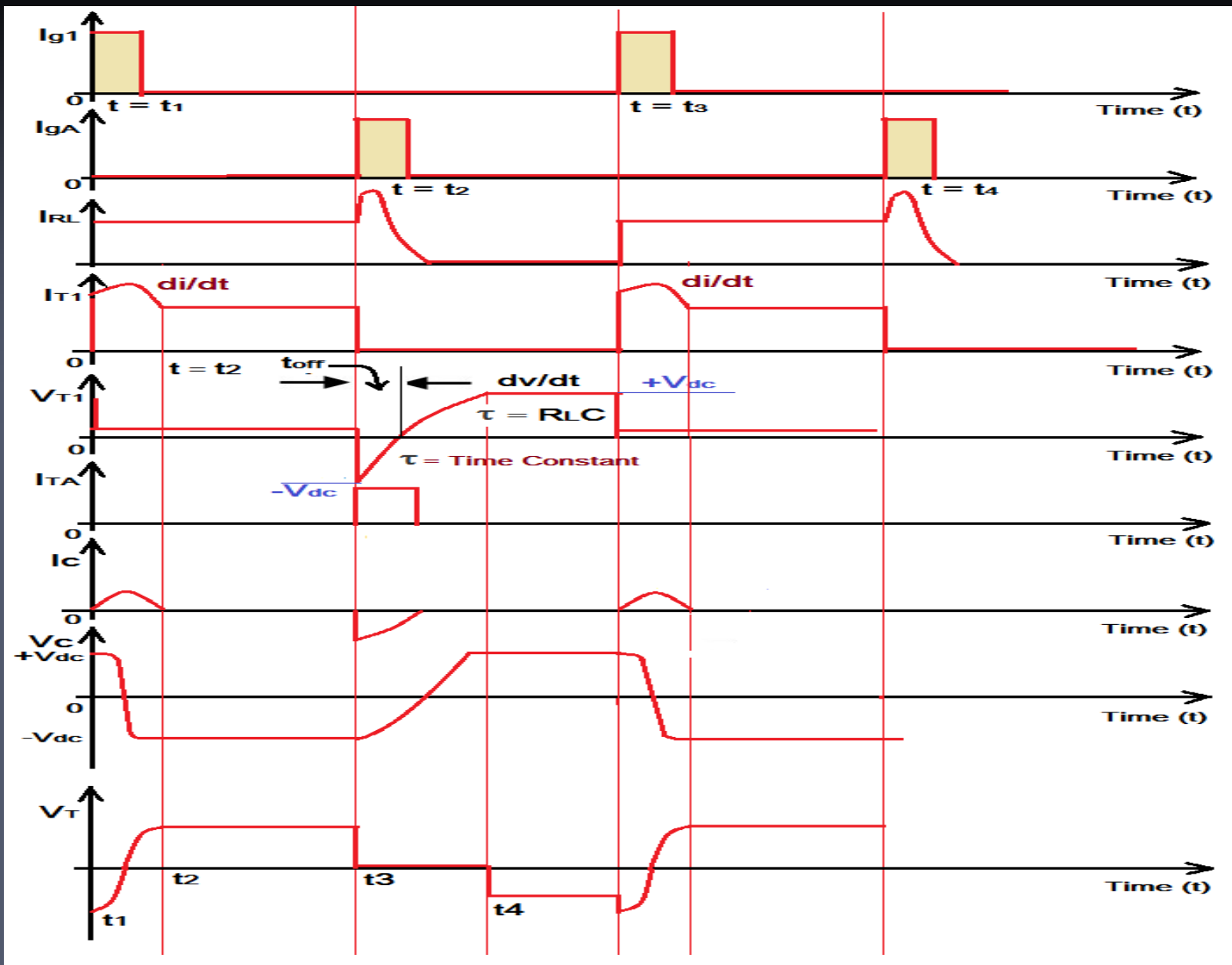

■ Fig (98) Shown Voltage and Current Waveforms of Class-D Commutation.

- **Class-D Commutation** is also known as **Auxiliary Commutation** due to the fact that **Auxiliary SCR (thyristor) T_A** is used for the **commutation of Main SCR (thyristor) T_1** . When **Auxiliary SCR (thyristor) T_A** is **ON**, **Capacitor C** gets connected across the terminals of **Main SCR (thyristor) T_1** , therefore this method of commutation is also called **Parallel Capacitor Commutation**.

to be continued