

Paper 1, TDC Part-1

Source Transformation

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Source Transformation

Source Conversion

A practical voltage source is always with a series resistance of small value. A practical voltage source will be considered as much as ~~good~~ better voltage source as ~~much~~ low is the value of the series resistance. This series resistance is called internal resistance of the practical voltage source.

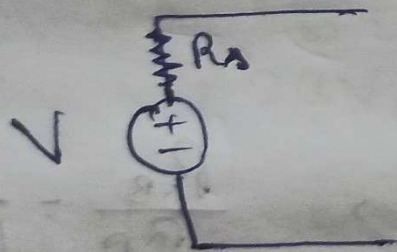


Figure (2.1) A practical voltage source with series resistance R_s .

Source Transformation

Figure (2.1) is a practical voltage source with series resistance R_s .

Let the current I flow through the resistor ' R_s ' when the voltage source is connected with any load resistor ' R_L '. So the ^{actual} voltage supplied by the practical voltage source is

$$V' = V - I R_s$$

where $I R_s$ is voltage drop across the ~~series~~ internal resistance R_s .

Source Transformation

Similarly a practical current source is always considered to be a current source with a $||l$ resistance R_p as shown below.

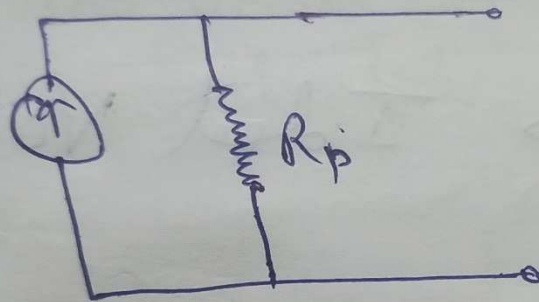


Figure 2.2 → A practical current source with $||l$ resistance R_p .

For a good practical current source the value of the $||l$ resistor R_p should be as much high as possible, so that the minimum

Source Transformation

current flows through this 11Ω resistor R_p and most of the current delivered by the current source should be ~~de~~ available to the load resistor R_L . The actual current ~~source~~ available to load resistor by the practical current source is,


$$I' = I - \frac{I \times R_p}{(R_L + R_p)} = I \left(1 - \frac{R_p}{R_L + R_p} \right)$$
$$= I \left(\frac{R_L}{R_L + R_p} \right)$$

On other hand

A ideal voltage source is that voltage source whose internal resistance (i.e. series resistance) value is zero. The ^{maximum} voltage ~~delivered~~ supplied by the ideal voltage source is V' .

Source Transformation

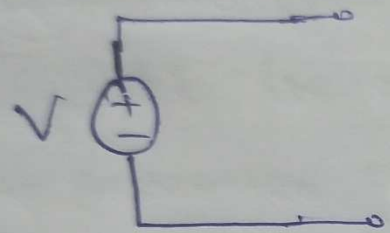A ideal voltage source can be represented by
~~the~~ as shown below :-



→ Ideal Voltage Source

Similarly an ideal current source is that
current source whose parallel resistance is
infinite (i.e. parallel resistor $R_p = \infty$) or we
can say it to be open circuited. So the
current delivered by Ideal current source
to load resistor is I .

Source Transformation

Current delivered by Ideal current source to load resistor is I .

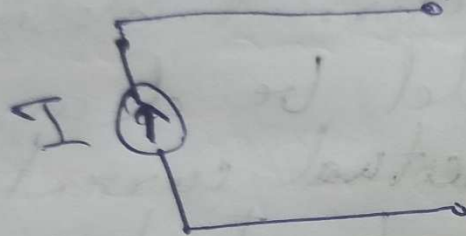



fig 2.3 - Ideal current source

A given practical voltage source with a series resistance (R_s) can be converted ~~into~~ and replaced by equivalent practical current source. Conversely, a ^{practical} current source with a $|R_s|$ resistance (R_p) can be


Source Transformation

Converted into a voltage source with a series resistance, R_s .

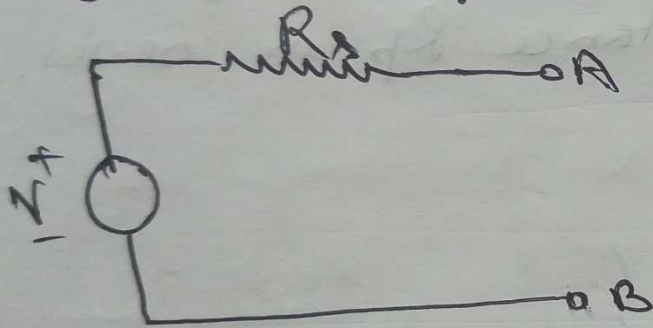Convert the voltage source shown in below figure to equivalent current source.



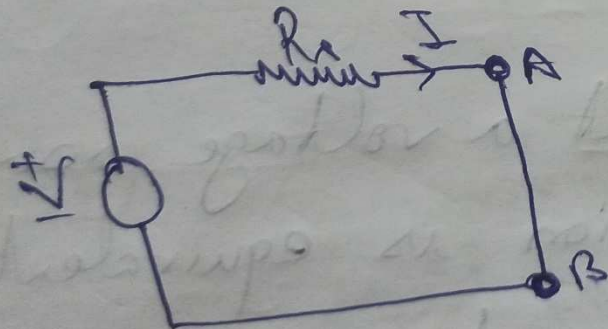First we will short the terminal A and B to find the current supplied by the source voltage V !



Current I due to voltage source is $I = \frac{V}{R_s}$

Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You

Contd. In next lecture