

Waveform Generation

Lecture - 12

(24/04/2021)

B.Sc (Electronics)

TDC PART - III

Paper – 6

Unit – 8

by:

Dr. Niraj Kumar

Assistant Professor (Guest Faculty)



Department of Electronics

L. S. College, BRA Bihar University, Muzaffarpur.

➤ **Transistor Mono-Stable Multivibrator Circuit Details (PART – 2)**

- ⇒ A **Mono-Stable Multivibrator** or a **One-Short Multivibrator** or a **Univibrator** has **one stable state**, i.e., **Permanent** and the other as **Temporary**, i.e., **Quasi-Stable State**. When an **External Trigger** is applied to the **input**, the multivibrator changes the state from **Stable State** to **Quasi-Stable State**. It stays in **Quasi-Stable State** for a **predetermined length of time** and after which the **circuit returns** to its **Original Stable State** automatically. The circuit produces the **output pulses of variable width** at the required moment (time).

⇒ A generalized circuit of a **Mono-Stable Multivibrator** using two Active Devices A1 and A2 is shown below in **Figure (3)**. Next **Figure (4)** shows below the **Collector-couple NPN Transistor Mono-Stable Multivibrator**.

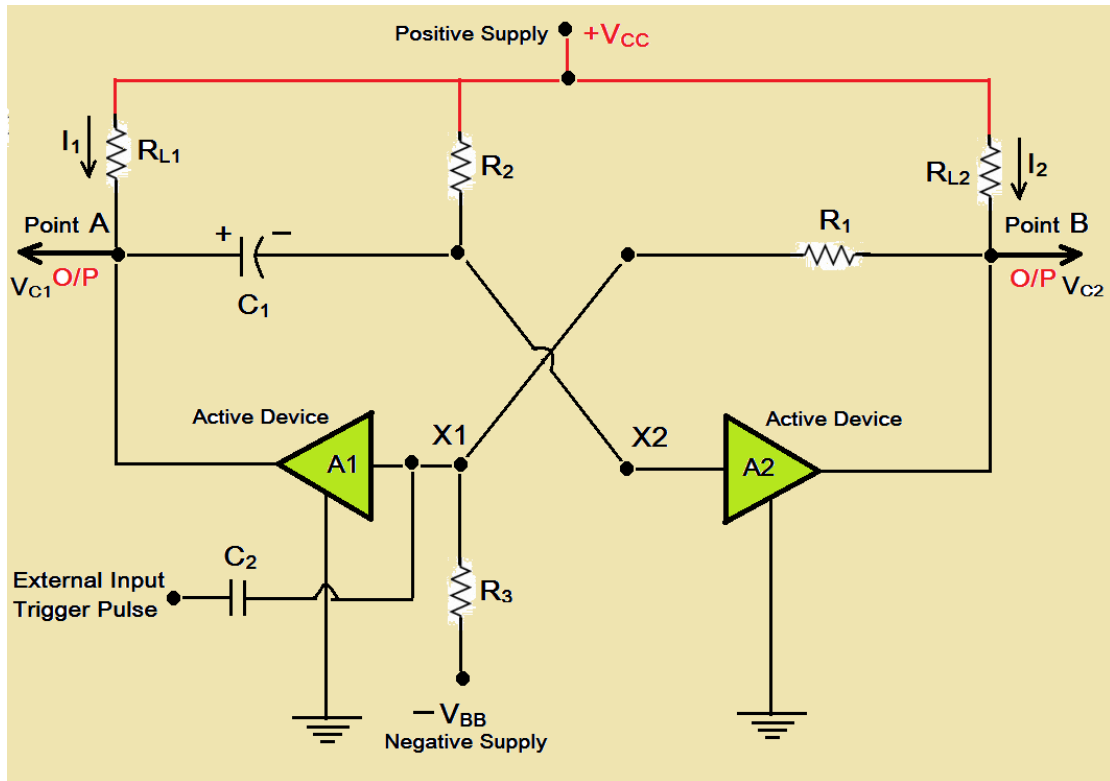


Fig. (3) Shown A generalized Circuit Configuration of a Mono-stable Multivibrator

⇒ Suppose that a **signal trigger** is applied to **X2 terminal** and a **regenerative action** takes place which drives **Active Device A2** to completely **Cut-OFF**. The **Voltage** at **Point B** rises approximately to **Positive Supply +VCC** . Now **Active Device A1** comes in **Conduction**. The device may be driven into **Saturation** or it may operate within its **Active region**. In either case a **Current I1** exists in **Load Resistor RL1** which causes a **Voltage Drop $I_1 R_{L1}$** at **Point A** and thereby **decreasing** the **Voltage** at **terminal X2** by the same amount because the **voltage** across **Capacitor C1** cannot change instantaneously. The **multivibrator** is now in its **Quasi-Stable State**. The **circuit will remain** in this state only for a **finite time** because **terminal X2** is connected to **Positive Supply +VCC** through **Resistor R2**. Now **terminal X2** will rise in voltage.

⇒ When the Voltage at terminal X2 is equal to the **Cut-IN Voltage** of Active Device A2, a regenerative action take place. This turns Active Device A1 **Cut-OFF** and eventually **returning the multivibrator** to its **initial stable state**. A **Collector-couples Mono-Stable Multivibrator** circuit using **NPN Transistors** is shown below in **Figure (4)**.

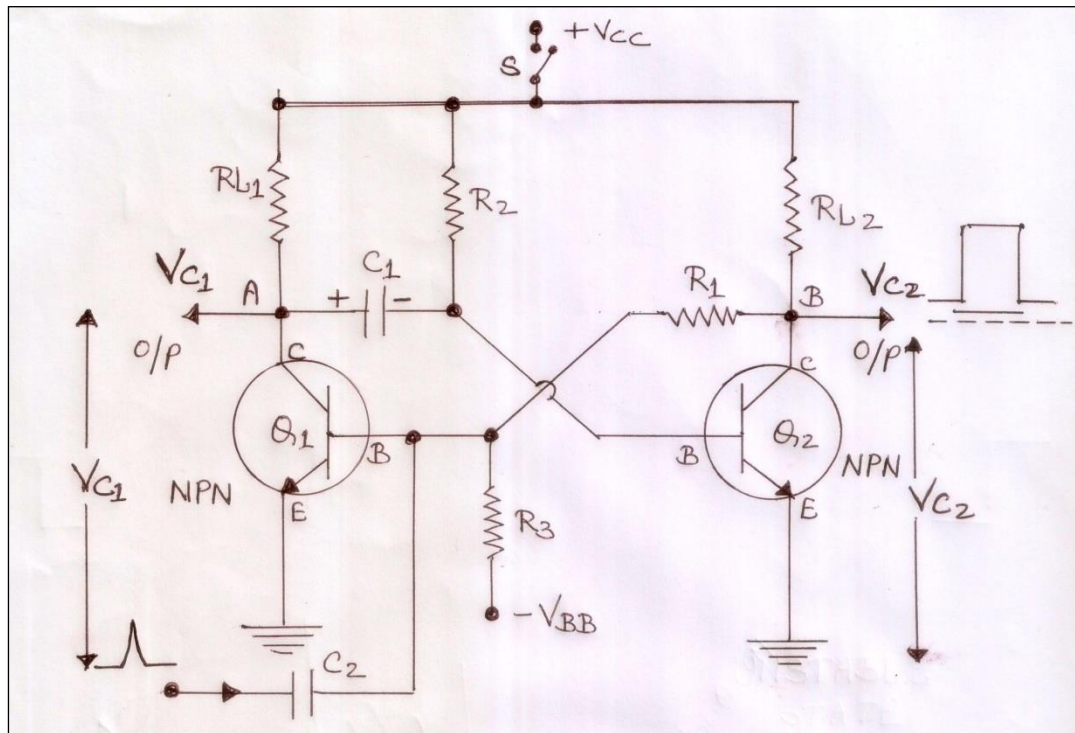


Fig. (4) Shown the Circuit Diagram of a Transistor Mono-Stable Multivibrator.

⇒ Above **Figure (4)** shows the circuit diagram of a transistor **Mono-Stable Multivibrator**. Here, **Collector terminal** of Transistor **Q1** is coupled to Transistor **Q2 Base** through **Capacitor C1** as in an **Astable Multivibrator** but the other coupling is different. It consists of **two similar NPN Transistors Q1 and Q2** with **equal Collector Loads** i.e. $R_{L1} = R_{L2}$. The values of negative supply $-V_{BB}$ and **Resistor R3** are such as to **Reverse bias** NPN Transistor **Q1** and keep it at **Cut-OFF**. The **Collector Supply** $+V_{CC}$ and **Resistor R2** **Forward bias** NPN Transistor **Q2** and keep it at **saturation**. The **External Input Trigger Pulse** is given through **Capacitor C2** to the **Base terminal** of NPN Transistor **Q1**.

⇒ To obtain the **Square Wave Output** again it can be taken from **Collector terminal of NPN Transistor Q1 at Point A or NPN Transistor Q2 at Point B**. In the **Mono-Stable Multivibrator** circuit diagram the Function of **Resistors R_{L1} and R_{L2}** is to limit **Collector current** of both **Transistors Q1 and Q2**. **Resistors R_1 & R_2** will provide base current for **Transistors Q1 & Q2** respectively during **ON condition**. In this **Mono-Stable Multivibrator**, a single narrow **Input Positive Trigger Pulse** produces a single **Square Wave or Rectangular Wave pulse** whose **amplitude, pulse width** and **wave shape** depend upon the values of **circuit components (RC)** rather than upon the **trigger pulse**.

⇒ Detailed **of the Transistor Mono-Stable Multivibrator Circuit Operation** is discussed in next **Lecture – 13**.

to be continued
