

Waveform Generation

Lecture - 13

(26/04/2021)

B.Sc (Electronics)

TDC PART - III

Paper – 6

Unit – 8

by:

Dr. Niraj Kumar

Assistant Professor (Guest Faculty)



Department of Electronics

L. S. College, BRA Bihar University, Muzaffarpur.

➤ **Transistor Mono-Stable Multivibrator Circuit Operation (PART – 3)**

⇒ **The operation of the Mono-Stable Multivibrator (MMV) circuit illustrated in Fig (5), (6) and (7) is as follows:-**

⇒ When the **Mono-Stable Multivibrator (MMV) Power supply +V_{CC}** is switched ON by closing the **Switch S**, both **Transistors Q1 and Q2 start conducting**. Then one transistor starts conducting slightly more than the other due to small differences in their **operating characteristics of the transistors**. This starts a series of events.

(1) MMV Initial Condition (STABLE STATE)

⇒ In the absence of a **Triggering Pulse** at Capacitor C_2 and with Switch S closed,

(1) Positive Power Supply $+V_{CC}$ provides **Reverse Bias** for C/B junctions of Transistors Q1 and Q2 but **Forward-Bias** for E/B junction of Transistor Q2 only. Hence, Transistor Q2 gets into **Saturation** and Conducts (ON-State).

(2) Negative Power Supply $-V_{BB}$ supply and Resistor R3 **Reverse Bias** Transistor Q1 and keep it **Cut-OFF** and **Non-conducts (OFF-State)**.

(3) Capacitor C1 **charges to nearly Positive** $+V_{CC}$ through Load Resistor R_{L1} to ground by the **Low-Resistance** path provided by **Saturated Transistor Q2**.

⇒ As seen, the **Initial Stable State** is represented by

(i) Transistor Q2 **Conducting (ON State)** at **Saturation** and

(ii) Transistor Q1 **Cut-OFF (OFF State)**.

⇒ **Figure (5)** Shown below **Mono-Stable Multivibrator Initial Stable State Condition**,

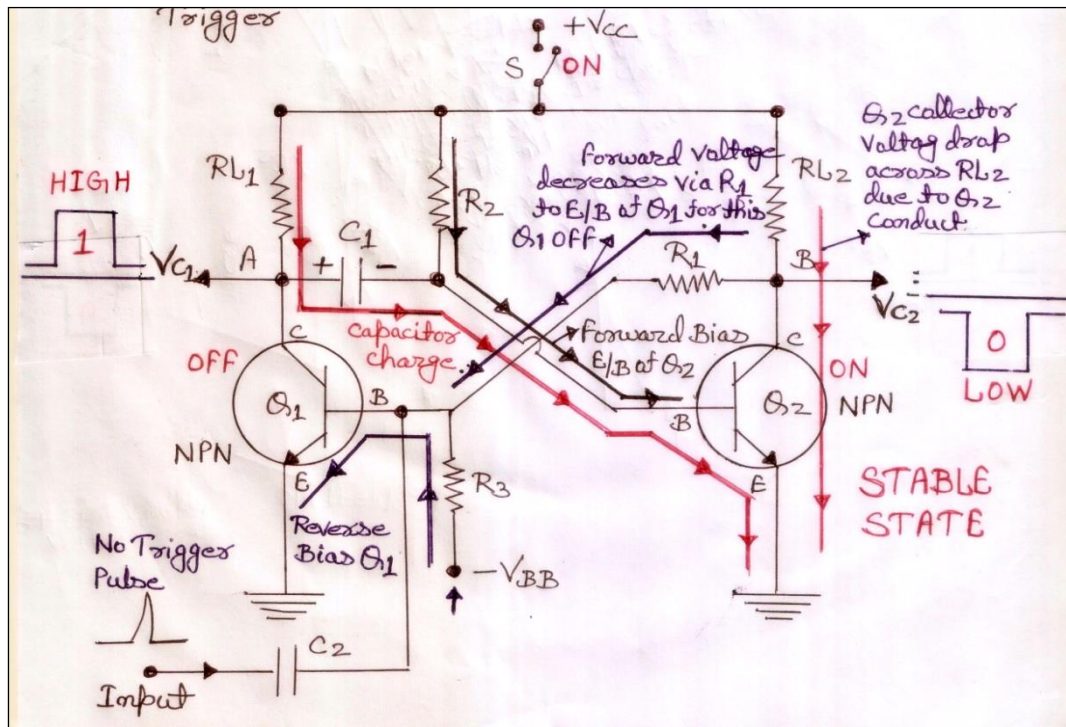


Fig (5) Shown MMV Initial Condition when No Trigger Pulse applied (STABLE STATE)

(2) When Trigger Pulse is Applied (UNSTABLE STATE)

⇒ When an External **Positive Trigger Pulse** is applied to NPN Transistor Q1 through Capacitor C2, **Mono-Stable Multivibrator** will switch to its **Opposite Unstable State** where Transistor Q2 is **Cut-OFF (OFF-State)** and Transistor Q1 Conducts (**ON-State**) at **Saturation**. The chain of circuit actions is as under:-

(1) If **Positive Trigger Pulse** is of sufficient amplitude, it will over-ride the **Reverse Bias** of the E/B junction of Transistor Q1 and give it a **Forward Bias**. Hence, Transistor Q1 will start Conducting (**ON-State**).

(2) As Transistor Q1 Conducts (**ON-State**), its **Collector Voltage** falls due to voltage drop across **Load Resistor RL1**. It means that potential of **Point A** falls (**negative-going signal**). This **Negative-going voltage** is fed to Transistor Q2 via Capacitor C1 where it decreases its **Forward Bias**.

- (3) As **Collector Current** of Transistor Q1 starts decreasing, potential of **Point B** increases (**Positive-going Signal**) due to lesser drop over Load Resistor R_{L2} . Soon, Transistor Q2 comes out of Conduction State (ON-State).
- (4) The **Positive-going Signal** at **Point B** is fed via Resistor R_1 to the **Base** of Transistor Q1 where it increases its **Forward Bias** further. As Transistor Q1 Conducts more, potential of **Point A** approaches 0 V (volt).
- (5) This action is **Cumulative** and ends with Transistor Q1 Conducting (ON-State) at Saturation and Transistor Q2 Cut-OFF (OFF-State).

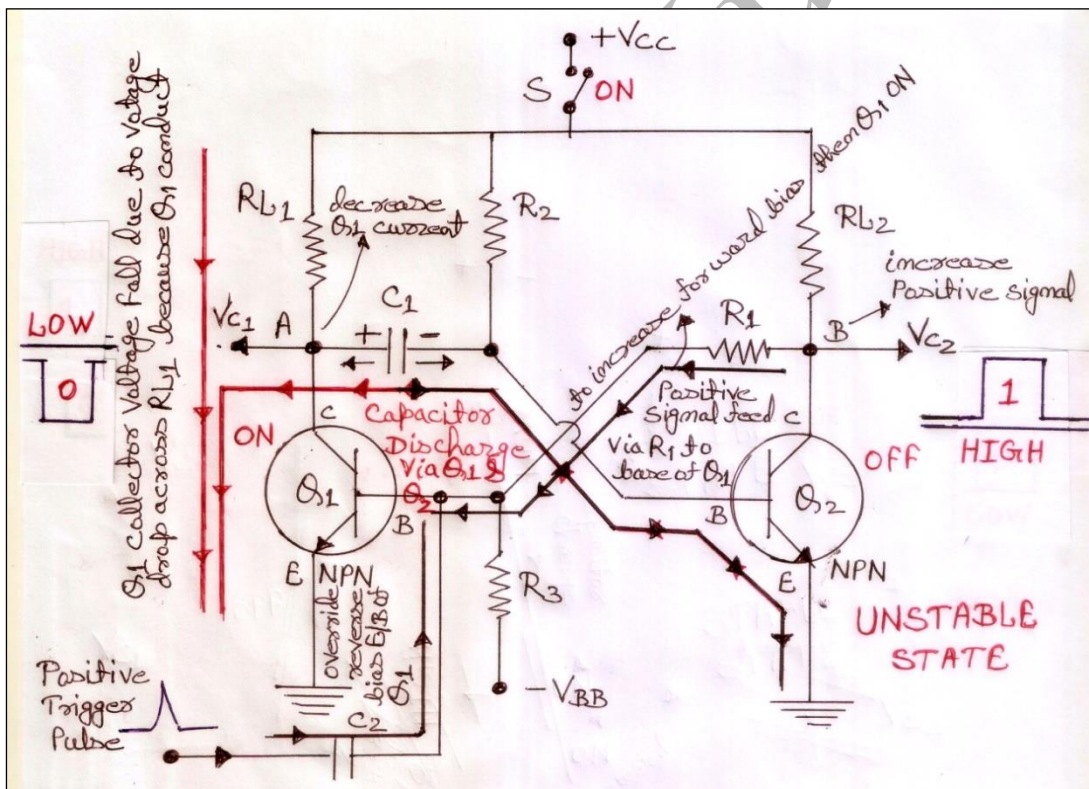


Fig (6) Shown MMV Circuit Diagram when Positive Trigger Pulse is applied (UNSTABLE STATE)

(3) Return to Initial Stable State (BACK TO STABLE STATE)

(1) As Point A is at almost 0 V (volt), Capacitor C_1 Starts to Discharge through Saturated (ON) Transistor Q1 to ground.

(2) As Capacitor C_1 Discharges, the Negative Potential at the Base of Transistor Q2 is decreased. As Capacitor C_1 Discharges further, Transistor Q2 is pulled out of Cut-OFF (OFF-State).

(3) As Transistor Q2 Conducts further, a Negative-going Signal from Point B via Resistor R_1 drives Transistor Q1 into Cut-OFF (OFF-State).

⇒ Hence, the circuit reverts to its Original Initial Stable State with Transistor Q2 Conducting (ON-State) at Saturation and Transistor Q1 Cut-OFF (OFF-State). It remains in this Original Initial Stable State till another Trigger Pulse comes along when the entire cycle repeats itself. It is shown below in Figure (7), when Mono-Stable Multivibrator (MMV) back to Original Initial Stable State.

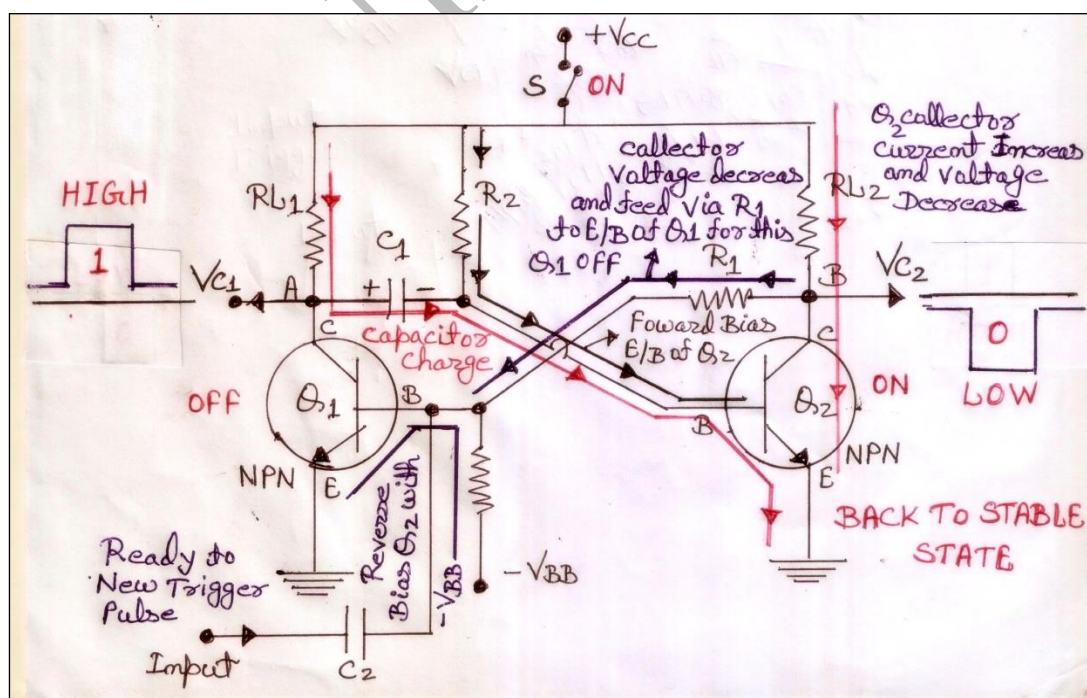


Fig (7) Shown MMV Circuit Diagram when MMV return to Initial Stable State (BACK TO STABLE STATE)

⇒ The **output** is taken from the **Point A of Collector terminal** of Transistor Q2 though it can also be taken from **Point A of Transistor Q1** as shown in above **Figure (5), (6) and (7)**. The **Width of this Pulse** is determined by the **Time Constant** of **R_2C_1** . Since this **Mono-Stable Multivibrator** produces **One Output Pulse** for every **Input Trigger Pulse** it receives, it is called **Mono or One-Shot Multivibrator**.

⇒ Detailed **of the Transistor Mono-Stable Multivibrator Output Waveforms, Its Advantage, Disadvantage and Applications** are discussed in next **Lecture – 14**.

to be continued

Dr. Niraj Kumar