

TRANSISTOR BIASING WITH EMITTER FEEDBACK

Lecture - 36

TDC PART -3

PAPER 6(GROUP B)

Chapter -6

BY:

DR. NAVIN KUMAR

(ASSISTANT PROFESSOR)


(GUEST FACULTY)

Department of Electronics

L.S COLLEGE, BRA Bihar University, Muzaffarpur.

Transistor biasing with emitter feedback

 - This type of transistor biasing configuration, often called self-emitter biasing, uses both emitter and base-collector feedback to stabilize the collector current even further.
- This is because resistors R_1 and R_2 as well as the base-emitter junction of the transistor are all effectively connected in series with the supply voltage, V .



Collector Feedback Bias

DEMERITS

- The downside of this emitter feedback configuration is that it reduces the output gain due to the base resistor connection.
- The collector voltage determines the current flowing through the feedback resistor, R_1 producing what is called “degenerative feedback”.

- The polarity of this voltage reverse biases the base-emitter junction, $I_{(current)}$ automatically decrease. Therefore the emitter current increase less than it would have done had there been no self biasing resistor.



USES

- This type of transistor biasing configuration works best at relatively low power supply voltages due to the configuration of “R”resistance
- 