

# Uni-Junction Transistor (UJT)

## Lecture – 2

TDC PART – I

Paper – I (Group – B)

Chapter - 8

by:

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S College, BRA Bihar University,**

**Muzaffarpur.**

# UJT Parameters

## (1) Inter Base Resistance ( $R_{BB}$ )

- It is the resistance between **(Base2)  $B_2$**  and **(Base1)  $B_1$**  *i.e.* it is the **total resistance of the silicon bar from one end to the other with emitter terminal open** *i.e.* When  $I_E = 0$ . **Inter Base Resistance  $R_{BB}$**  shown in **Fig. (3) (a)**. In simple words, it is the resistance of the **N-Type** bar when measured lengthwise. If  **$R_{B1}$**  is the resistance of the bar from **E** to  **$B_1$**  and  **$R_{B2}$**  is the resistance of the bar from **E** to  **$B_2$** .
- From the equivalent circuit of UJT shown in **Fig (3) (b)**, it is seen that  **$R_{BB}$**  can be expressed as,

$$R_{BB} = R_{B2} + R_{B1}$$

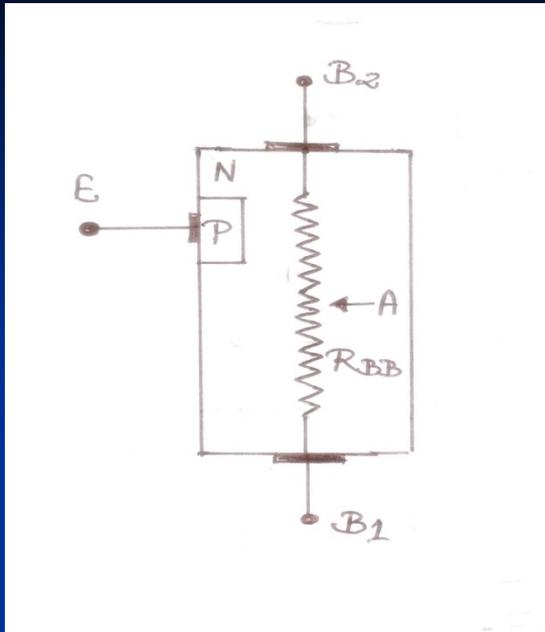


Fig. (3) (a)

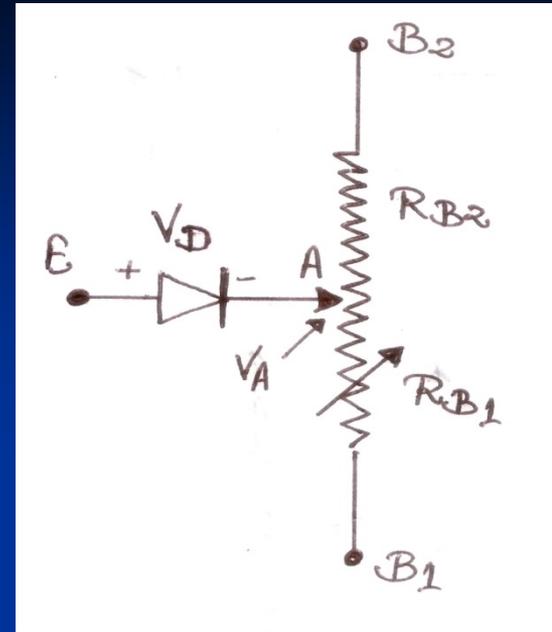


Fig. (3) (b)

Fig. (3) (a) Shown UJT internal view with Inter-Base Resistance  $R_{BB}$ .

Fig. (3) (b) Shown UJT Equivalent Internal Circuit With voltage Divider.

- It should also be noted that point  $A$  is such that  $R_{B1} > R_{B2}$ . Usually,  $R_{B1} = 60\%$  of  $R_{BB}$ . The typical range of Inter Base Resistance  $R_{BB}$  is from  $4K\Omega$  to  $10K\Omega$ . The resistance  $R_{B1}$  has been shown in Fig. (3) (b) as a variable resistor because its value varies inversely as Emitter Current  $I_E$ .

## (2) Intrinsic Stand-off Ratio ( $\eta$ )

- As seen from **Fig. (4) (a)**, when a battery of **30 V** is applied across **(Base2)  $B_2$**  and **(BASE1)  $B_1$** , there is a progressive fall of voltage over  **$R_{BB}$**  provided **(Emitter)  $E$**  is open. It is obvious from **Fig. (4) (b)** that Emitter acts as a voltage-divider tap on fixed resistance  **$R_{BB}$** . With emitter open,  **$I_1 = I_2$** , the **Inter-base Current** is given by Ohm's Law.

$$I_1 = I_2 = V_{BB} / R_{BB}$$



## For example: -

- For example: - if  $V_{BB} = 30 \text{ V}$  and  $R_{BB} = 15 \text{ K}$ ,  $I_1 = I_2 = 2 \text{ mA}$ .
- It may be noted that part of  $V_{BB}$  is dropped over  $R_{B2}$  and part on  $R_{B1}$ . Let us call the voltage drop across  $R_{B1}$  as  $V_A$ . Using simple **voltage divider** relationship,

$$V_A = V_{BB} (R_{B1} / R_{B1} + R_{B2})$$

- The **voltage division factor** is given a special symbol ( $\eta$ ) and the name of '**intrinsic stand – off ratio**'. **Intrinsic stand – off ratio** is the ratio of  $R_{B1}$  to the sum of  $R_{B1}$  and  $R_{B2}$ . It can be expressed as,

$$\eta = R_{B1} / R_{B1} + R_{B2}$$

$$V_A = \eta V_{BB}$$

- The **Intrinsic Stand-off Ratio** ( $\eta$ ) is the property of the **UJT** and is always **less than unity (0.4 to 0.85)**. If  $V_{BB} = 30$  V and  $\eta = 0.6$ , then potential of point **A** with respect to point **B1** =  $0.6 \times 30 = 18$  V. The remaining 12 V drop across  $R_{B2}$ .

## (2) Intrinsic Stand off Ratio ( $\eta$ ) by 2nd Method

- Fig. (5), show a battery  $V_{BB}$  connected across Base  $B_2$  and  $B_1$  of equivalent circuit of UJT. Here emitter point  $E$  acts as a Voltage Divider Tapon the fixed resistance  $R_{BB}$ . It is obvious that part of  $V_{BB}$  is dropped over  $R_{B2}$  and part on  $R_{B1}$ . Let the voltage drop across  $R_{B1}$  is  $V_{RB1}$ , then the magnitude of  $V_{RB1}$  (with  $I_E = 0$ ) is equal to  $V_A$ . According to the simple voltage divider rule we get,

$$V_{RB1} = V_A = V_{BB} ( R_{B1} / R_{B1} + R_{B2} ) \text{ ---- } I_E = 0$$

..... (1)

Where,  $R_{BB} = R_{B1} + R_{B2}$

- $R_{BB}$  Inter Base Resistance when no voltage is applied to the emitter).

- From equation (1), we have,

$$V_A / V_{BB} = R_{B1} / R_{B1} + R_{B2} \dots\dots\dots (2)$$

- The ratio  $V_A / V_{BB}$  is called the intrinsic- stand off ratio and is represented by  $\eta$ .

Hence ,

$$\eta = R_{B1} / R_{B1} + R_{B2} = R_{B1} / R_{BB} \text{ ---- } I_E = 0$$

..... (3)

- The **Intrinsic Stand-off Ratio** ( $\eta$ ) is the property of the UJT and is always less than unity(0.4 to 0.85). Voltage across  $R_{B1}$  is,

$$V_{RB1} = V_A = ( R_{B1} / R_{BB} ) V_{BB} \text{ ---- } I_E = 0$$

..... (4)

$$V_{RB1} = V_A = \eta V_{BB} \text{ ---- } I_E = 0$$

..... (5)

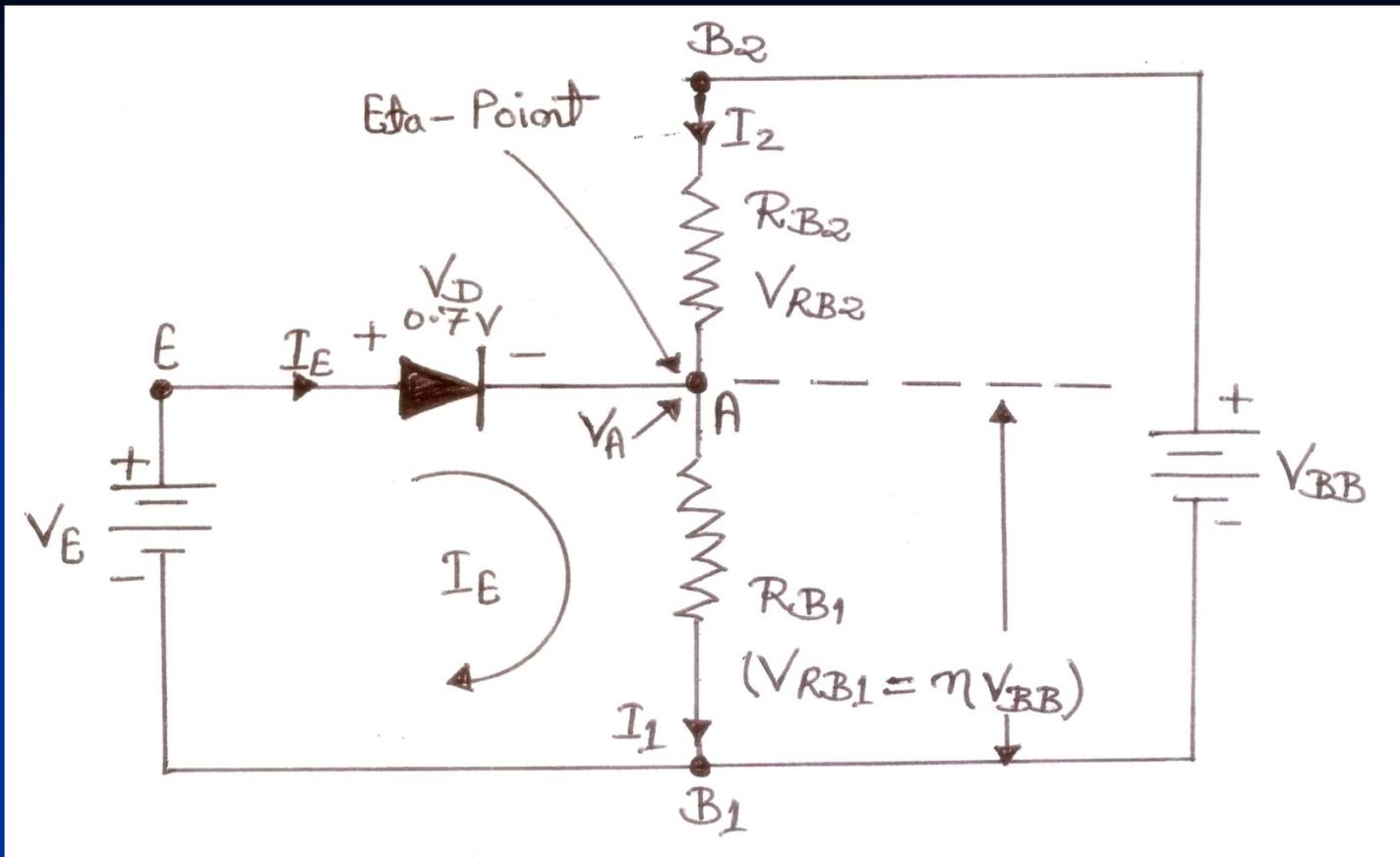


Fig. (5) Shown Typical UJT Equivalent Circuit Diagram.

- The voltage  $\eta V_{BB}$  appearing across  $R_{B1}$  Reverse-Biases the diode and hence the Emitter Current  $I_E = 0$

## (2) Intrinsic Stand off Ratio ( $\eta$ ) by 3rd Method

- **Intrinsic Stand off Ratio (  $\eta$  )** can be describe as, when Inter Base Voltage ( $V_{BB}$ ) is applied across the two base terminals B1 and B2 shown in Fig. (5) the potential of point A with respect to B1 is given by

$$V_{AB1} = ( V_{BB} / R_{B1} + R_{B2} ) R_{B1}$$

$$V_{AB1} = ( R_{B1} / R_{B1} + R_{B2} ) V_{BB}$$

$$V_{AB1} = \eta V_{BB}$$


Where,  $\eta = R_{B1} / R_{B1} + R_{B2}$

- $\eta$  (nita) is called the **Intrinsic Stand off Ratio (  $\eta$  )**.
- The **Intrinsic Stand off Ratio** is the property of the **UJT** and is always **less then Unity**. The typical value of  $\eta$  are .51 to .82.

### (3) Circuit Arrangement For UJT V-I Characteristics

- For ease of understanding, the internal model of the UJT is used in the circuit shown in Fig (6). (Base2) B2 terminal of the UJT is made positive with respect to (Base1) B1 terminal using the voltage source  $V_{BB}$ . Emitter terminal E of the UJT is forward biased using the voltage source  $V_E$ . Current starts flowing into the emitter only when the bias voltage  $V_E$  has exceeded the forward voltage drop of the internal diode ( $V_D$ ) (0.7V) plus the voltage drop across  $R_{B1}$  ( $V_{RB1}$ ). This condition can be expressed using the following equation below,

$$V_E = V_D + V_{RB1}$$

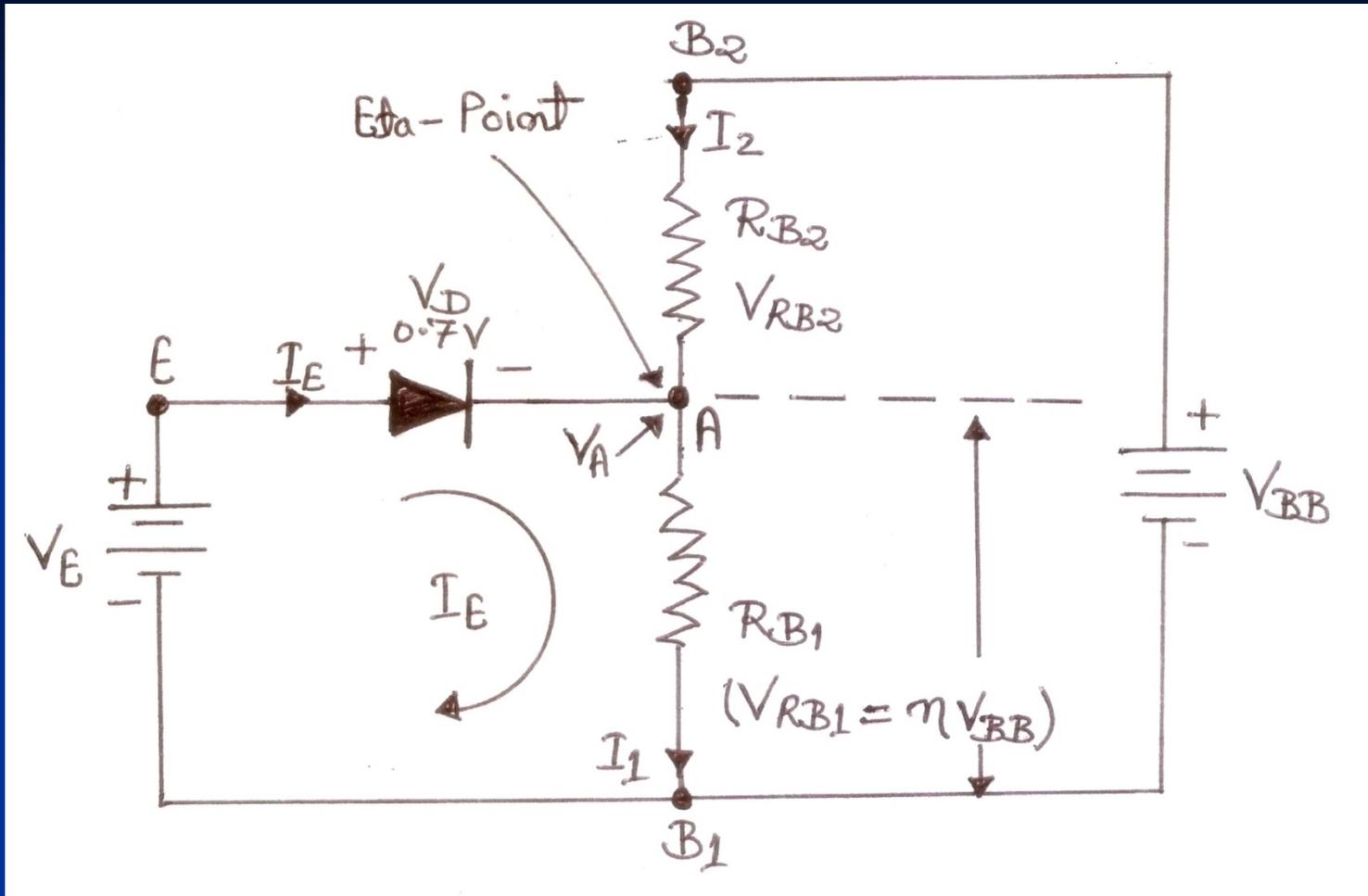

**Fig. (6) Shown Typical UJT Equivalent Circuit Diagram for V – I Characteristics**

- Considering the intrinsic stand off ratio

$$\eta = R_{B1} / ( R_{B1} + R_{B2} ),$$

then the equation becomes

$$V_E = V_D + \eta V_{BB}$$


- A typical silicon diode has a forward voltage drop of  $V_D = 0.7V$ . When this factor is considered, the equation can be re written as,

$$V_E = 0.7V + \eta V_{BB}$$

- This minimum value of the Emitter Voltage  $V_E$  for which the Emitter Current  $I_E$  starts to flow is called the **Firing Voltage of UJT.**

- As the **Emitter Voltage  $V_E$**  is increased the **emitter current  $I_E$**  is also increased and the junction behaves like a typical **P-N junction**. But the **Emitter Voltage  $V_E$**  can be only increased up to a particular point called  **$V_P$  (peak voltage)**.
- At this point a considerable amount of **Emitter Current  $I_E$**  flows and a significant number of **holes** are injected into the junction. These holes are repelled by **(Base2)  $B_2$**  and attracted by **(Base1)  $B_1$** . As a result, the region between **Emitter (E)** and **(Base1)  $B_1$**  terminal starts **Saturating by holes** and the **conductivity** of this region starts to **increase**. This phenomenon of increasing conductivity by the insertion of holes is called **Conductivity Modulation**.

- This increased conductivity reduces  $R_{B1}$  and Intrinsic Stand of Ratio ( $\eta$ ). This results in a condition where emitter current  $I_E$  increases and the emitter voltage  $V_E$  decrease. This situation is similar to a Negative Resistance scenario. In the  $V$  -  $I$  Characteristic of UJT which shown is in Fig. (7) in next slide, we can see that the regions between  $V_P$  (peak voltage point) and  $V_V$  (valley voltage) have a negative slope. This negative resistance region in the UJT characteristics is employed in **Oscillator Circuit**.

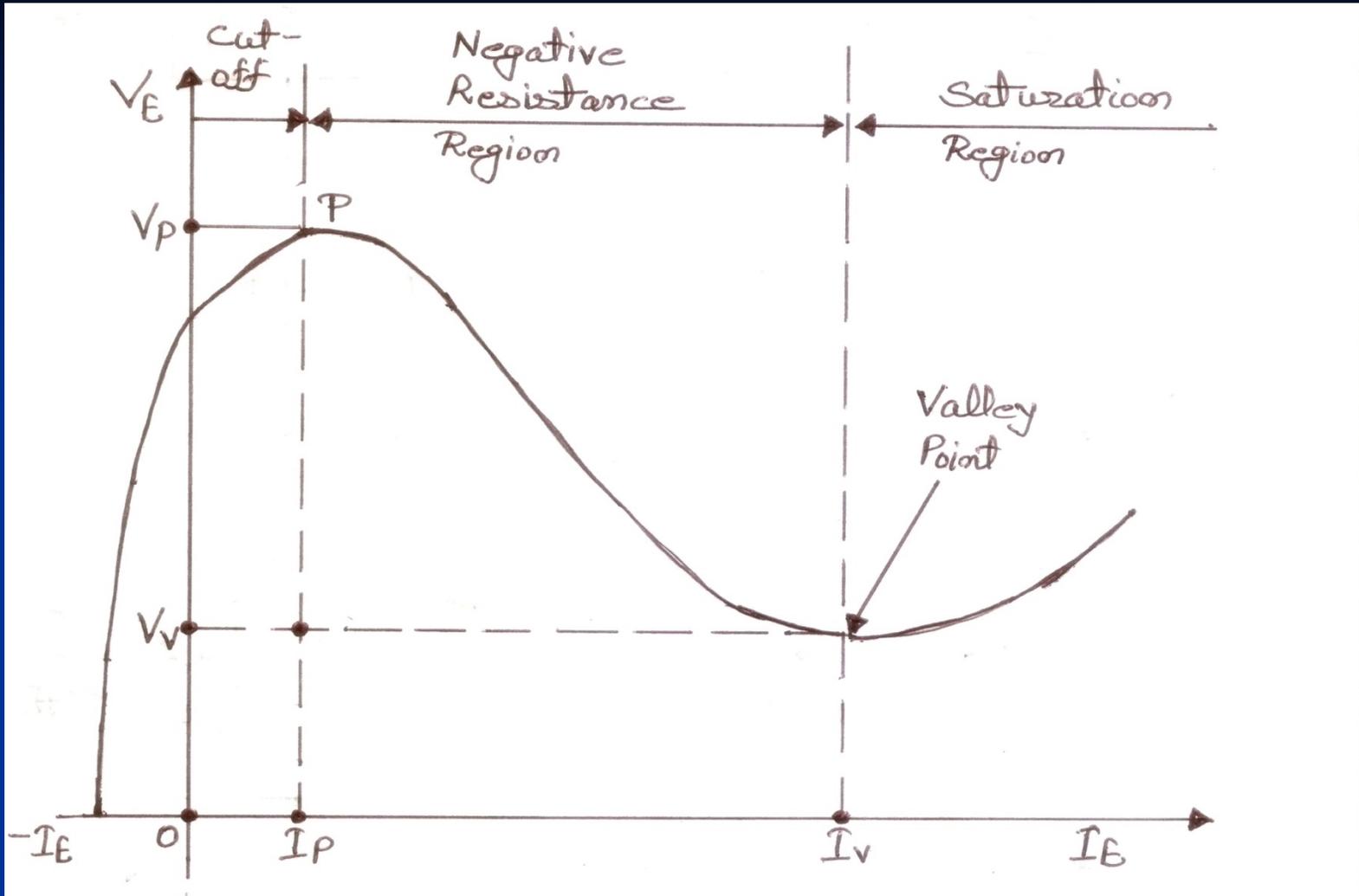

■ Fig. (7) Shown V-I Characteristics of UJT with Negative Resistance.

- At last the emitter current  $I_E$  will be increased to a point that no more increase in conductivity is possible. This point is called “**Valley point**”. The emitter current corresponding to valley point is denoted as  $I_v$  and the corresponding **Emitter Voltage** is denoted as  $V_v$ . Beyond the valley point, the **UJT** is **Fully Saturated** and the junction behaves like a **Fully saturated P-N junction**.

**to be continued.....**