

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Inductor Lecture 5

By:

Mayank Mausam

Assistant Professor (Guest Faculty)


Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar


Introduction to Passive Elements- Inductor

Discharging of Inductor:->

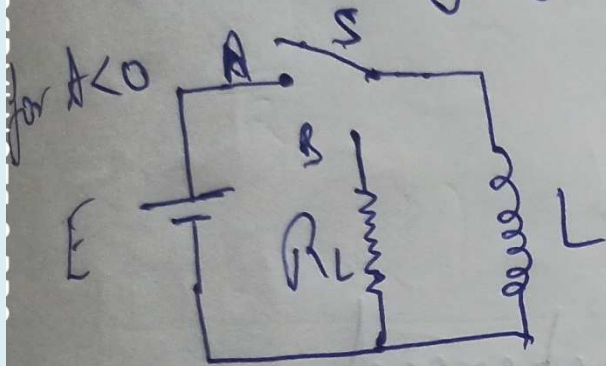

At $t < 0$ the ckt is open & switch S is at open condition.

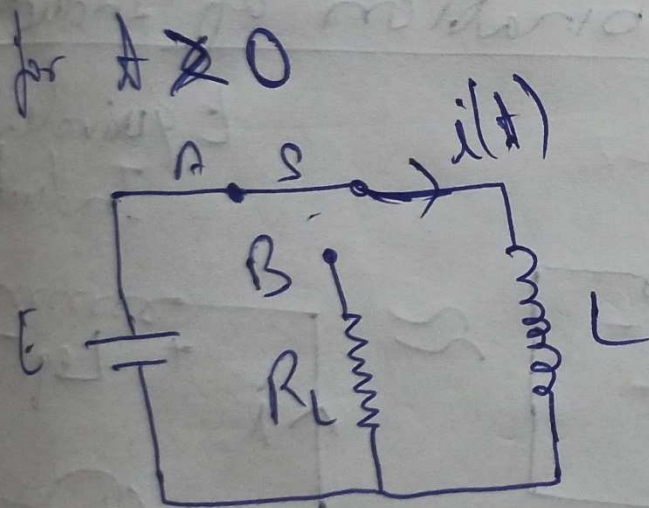
Now at $t = 0$ we have ~~enclosed~~ closed the switch then we have current



$$\text{So } i(t) = \frac{E}{L} t$$

Introduction to Passive Elements- Inductor

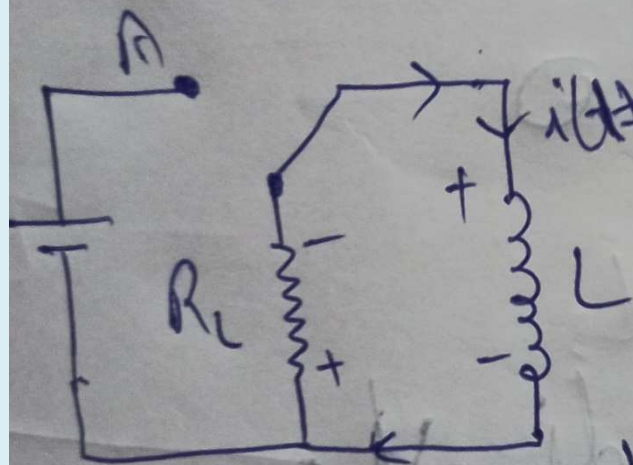Now at $t = 2s$ the switch S is moved to position B then we have,



at $t = 2s$, R_L is connected across the inductor with initial current $i(t=2s)$ which has been inherited by inductor L .

For this new case we can say,

$$\cancel{L \frac{di(t)}{dt} + R_L i(t) = 0} \quad L \frac{di}{dt} + R_L i = 0$$


Introduction to Passive Elements- Inductor

$$\text{or, } \frac{di}{dt} + \frac{R_L}{L} i = 0$$

As done previously we get

$$i_L(t) = i(\phi=2) e^{-\frac{R_L}{L} t}$$

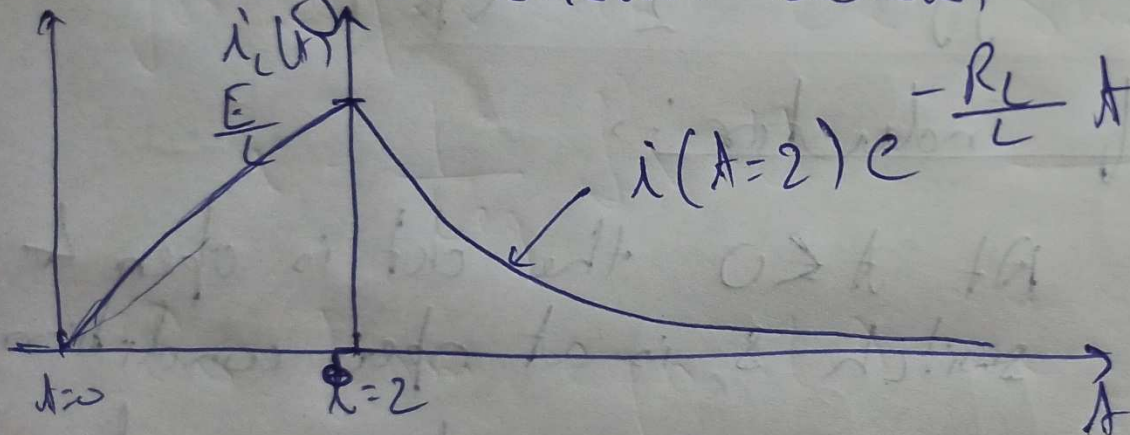So this inductor current will decay, exponentially as shown below,



So this way inductor get discharged.

Introduction to Passive Elements- Inductor

Series & Parallel Combination of Inductance
Series Connection

Equivalent Inductance

As we know by KVL

$$-V + V_1 + V_2 + V_3 = 0$$

or, $V_1 + V_2 + V_3 = V$

$$L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} = V \quad \text{--- (i)}$$

Also for equivalent ckt. shown in

Introduction to Passive Elements- Inductor

We have,

$$L_{eq} \frac{di}{dt} = V \quad \text{--- (ii)}$$

from eqn (i) & (ii) we can write

$$L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

$$\text{or, } L_{eq} \frac{di}{dt} = (L_1 + L_2 + L_3) \frac{di}{dt}$$

$$\text{or, } L_{eq} = L_1 + L_2 + L_3$$


So in series combination of inductances the equivalent inductance is the sum of all inductance connected in series.

Introduction to Passive Elements- Inductor

Let n inductances with respective inductance of $L_1, L_2, L_3, \dots, L_n$ are connected in series then the equivalent inductance ~~of the~~ is given by,

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

Parallel Connection of Inductance

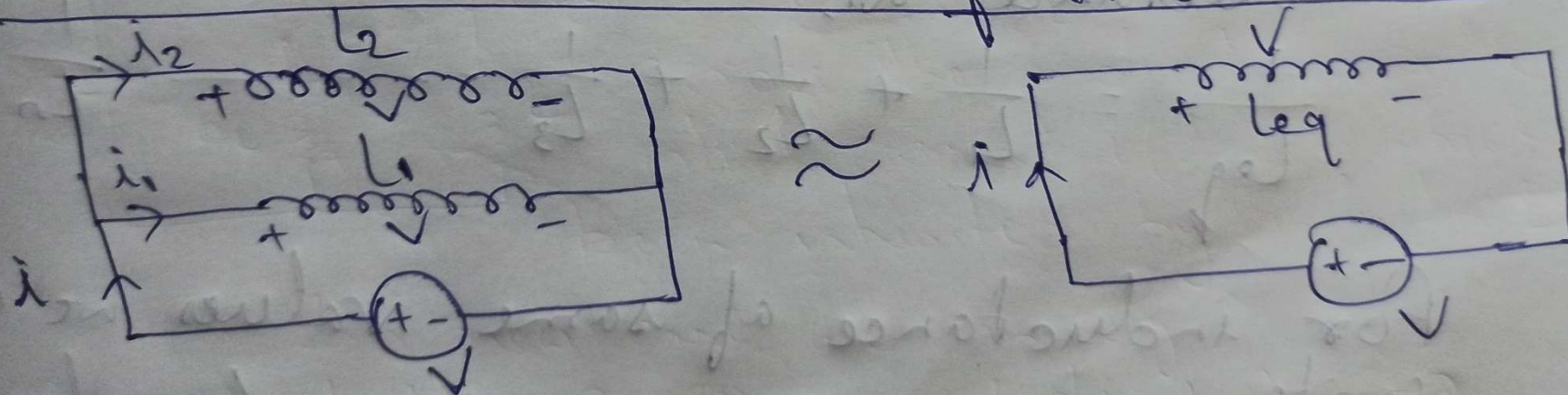

Introduction to Passive Elements- Inductor

As we know as per KCL we have. and there is no initial current, $i(0) = 0$

$$i = i_1 + i_2$$

$$i = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt \quad \text{--- (i)}$$

for equivalent ckt shown.

$$i = \frac{1}{L_{eq}} \int v dt \quad \text{--- (ii)}$$

So from eqn. (i) & (ii) we have

$$\frac{1}{L_{eq}} \int v dt = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt$$

Introduction to Passive Elements- Inductor

$$\text{or } \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\text{or } L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

So for n nos of inductors connected in parallel we ~~have~~ can give equivalent inductance or,

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}$$

For inductance of same values we can write,

$$\frac{1}{L_{eq}} = \frac{n}{L} \quad \text{or, } L_{eq} = \frac{L}{n} \quad \text{where } n = \text{any positive integer.}$$

Introduction to Passive Elements - Inductor

For any query contact- 9771474020

Thank You

To be Contd..