

Paper 1, TDC Part-1
Chapter– 3, Mesh and Node Analysis

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Mesh and Nodal Analysis in Passive Circuits

Nodal Analysis

This is another method for analysing circuits.
This method is based on 'KCL'.

What is node?

→ It is a point in a circuit where terminals (ends) of two or more circuit elements meet.

In nodal analysis method we consider (take) those nodes of a circuit where at least 3 or more circuit elements meet.

Mesh and Nodal Analysis in Passive Circuits

In a complex circuit the number of nodes increases. Let the circuits have ' N ' nodes in all. One of these nodes is chosen as the reference (datum) node. The voltages of remaining $(N-1)$ nodes with respect to the reference node form an independent set of variables that implicitly satisfies KVL equations.


$(N-1)$ KCL equations are written down at the nodes.

For a resistive network this step results in $(N-1)$ simultaneous algebraic equations in $(N-1)$ nodal voltages. Once the nodal

Mesh and Nodal Analysis in Passive Circuits

voltages are obtained, any voltage and current in the network can be obtained from these.

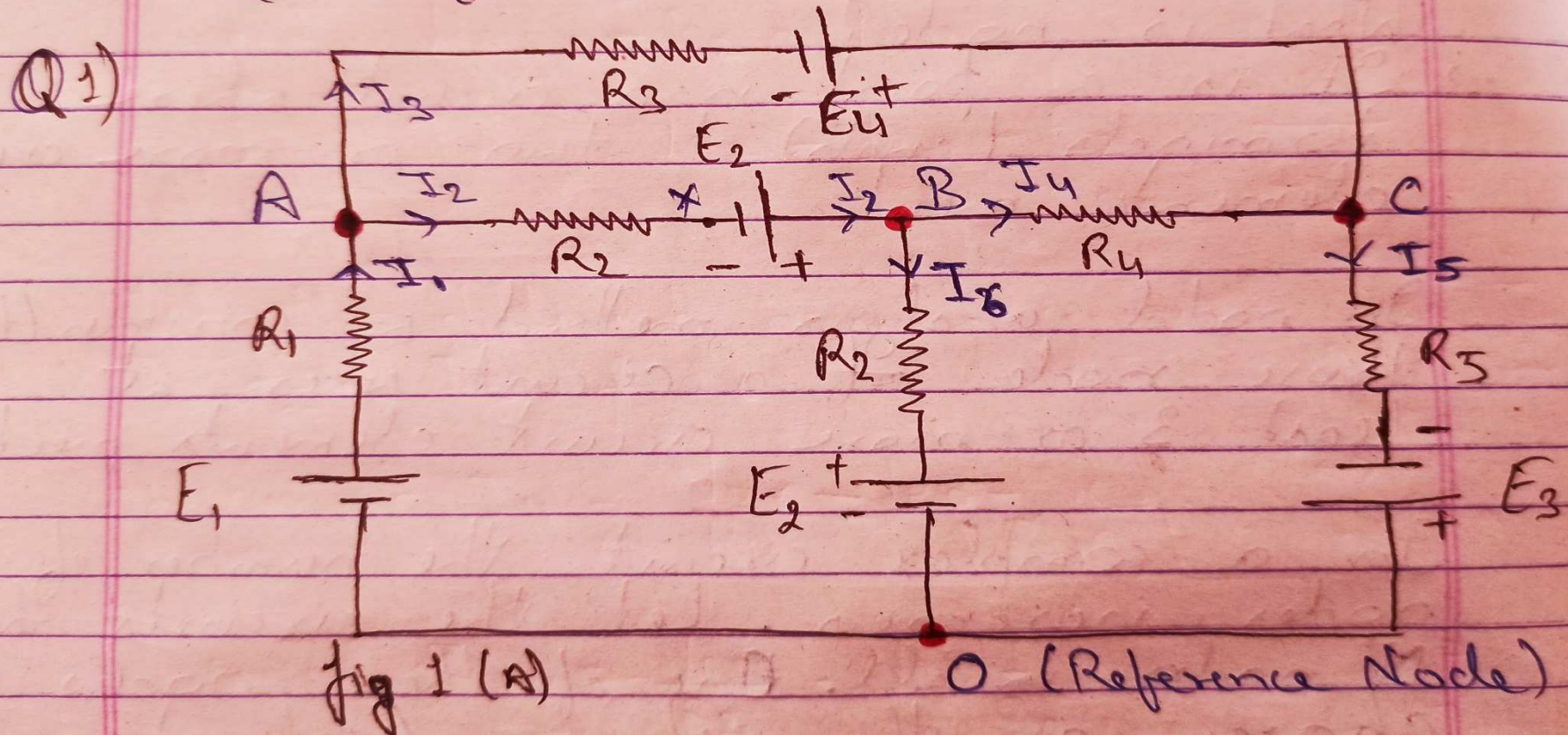For demonstration, consider the following circuit discussed below.



Mesh and Nodal Analysis in Passive Circuits

fig 1 (A)

O (Reference Node)

Find the current in each branch of the circuit, shown in figure 1 (A).

Soln: First of all in nodal analysis method we identify the **nodes** (i.e. those point where more than 2 branch elements ends are joined in a circuit and name those ~~nodes~~ identified nodes as A, B, C & O.

So there are 4 nodes i.e. $n = 4$

Mesh and Nodal Analysis in Passive Circuits

Now choose a reference node. Let the reference node be 'O'. (A reference node can be any node and a reference node is a node with respect to that potential of other nodes calculated.)

So here we get V_{AO} , V_{BO} , V_{CO}


[If C is our reference node then we calculate V_{AC} , V_{BC} , & V_{OC}]

$V_{AO} \rightarrow$ It is the potential of node A with respect to node O.

Similarly for V_{BO} & V_{CO}


Mesh and Nodal Analysis in Passive Circuits

Now, if somehow we find the value of V_{AO} , V_{BO} & V_{CO} then we can find ~~the~~ all of the branch current as ~~now~~ we know that
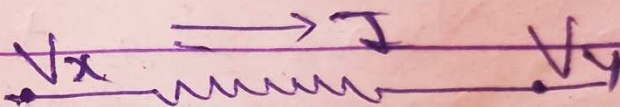
$$I = \frac{V_{xy}}{R} = \frac{V_x - V_y}{R}$$


So if the potential at the nodes are known then we can find the branch current.

Consider branch AB of figure 1(A).

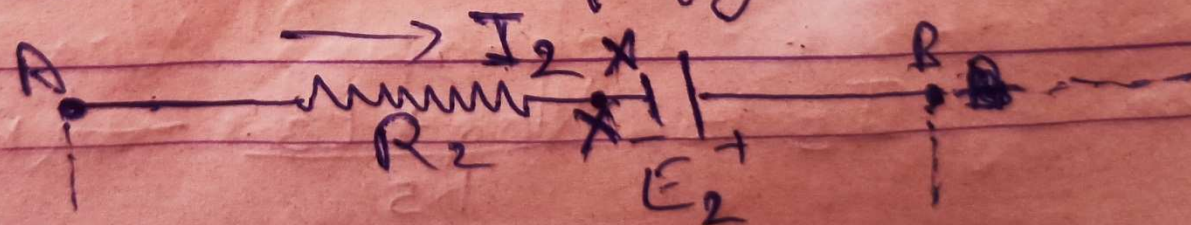

Mesh and Nodal Analysis in Passive Circuits

Let the current I_2 flows the branch AB i.e. through the resistor R_2


$$\text{then } I_2 = \frac{V_{Ax} - V_{Bx}}{R_2} = \frac{V_{A0} - V_{B0}}{R_2}$$

$$\text{and } V_{B0} = -E_2 + V_{B0}$$

$$\text{So, } I_2 = \frac{V_{A0} - V_{B0} + E_2}{R_2} \quad \text{--- (i)}$$


Let the different branch currents are I_1, I_2, I_3, I_4, I_5 & I_6 as shown in figure
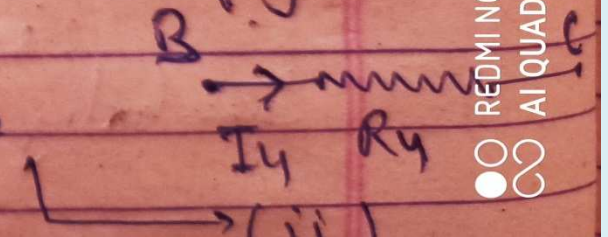
$$\text{The current } I_4 = \frac{V_{B0} - V_{C0} - V_{C0}}{R_4}$$




Mesh and Nodal Analysis in Passive Circuits

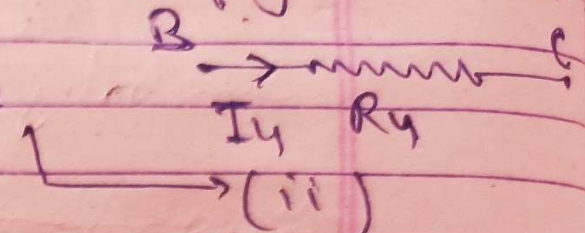the current $I_4 = \frac{V_{B0} - V_{B0} - V_{C0}}{R_4}$



current $I_6 = \frac{V_{B4}}{R_2} = \frac{V_{B0} - V_{40}}{R_2}$


and $V_{40} = E_2 + V_0 = E_2$

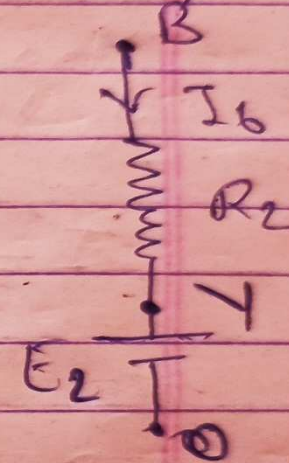

So, $I_6 = \frac{V_{B0} - E_2}{R_2}$ — (iii)

Similarly $I_5 = \frac{V_{C2}}{R_5} = \frac{V_{C0} - V_{20}}{R_5}$

and $V_{20} = -E_3$

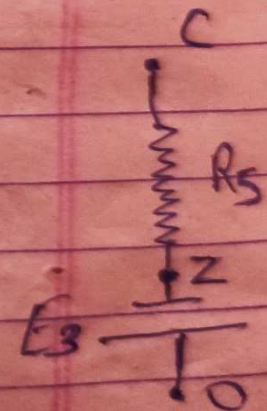

$I_5 = \frac{V_{C0} + E_3}{R_5}$ — (iv)

Mesh and Nodal Analysis in Passive Circuits

$$\text{Hence, } I_3 = \frac{V_{A0} - (-E_4 + V_{C0})}{R_3} = \frac{V_{A0} + E_4 - V_{C0}}{R_3} \quad \text{--- (v)}$$

$$\text{and at last Hence } I_1 = \frac{E_1 - V_{A0} - (v_i)}{R_1}$$

So if the potentials of all the nodes A, B & C are known then we can find the ~~all~~ branch currents, I_1, I_2, I_3, I_4, I_5 & I_6 .

Now to solve for V_{A0}, V_{B0} & V_{C0} we will write KCL at nodes A, B, & C respectively.

Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You