

Paper 1, TDC Part-1
Chapter– 3, Mesh and Node Analysis
Nodal Analysis - 4

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar


Mesh and Nodal Analysis in Passive Circuits

Nodal Analysis

Lecture 4

Let us discuss one more problem on Nodal Analysis.

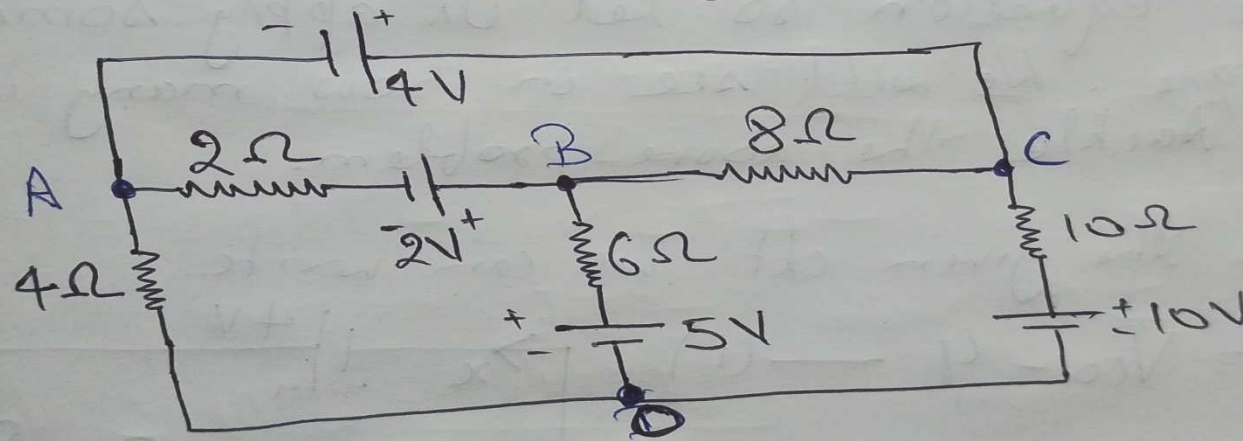Problem:- Solve the below shown network using Nodal Analysis method. The 4V voltage source is the ideal voltage source.



Soln:- Note that it is given "4V" source is ideal voltage source this means internal resistance of the voltage source is "0".

Mesh and Nodal Analysis in Passive Circuits

voltage source this means internal resistance of the voltage source is '0'.

Now let us proceed further, to solve the problem using Nodal Analysis.

So first let us identify the nodes and name them A, B, C & D. Also consider the voltage at A, B & C are V_A , V_B & V_C , while the voltage at node D is $V_D = 0V$ because it is grounded.

Now let us see what happens if we consider D as reference node.

Mesh and Nodal Analysis in Passive Circuits

Writing KCL at node A,

$$V_{A0}\left(\frac{1}{2} + \frac{1}{4} + \frac{1}{0}\right) - V_{B0}\left(\frac{1}{2}\right) - V_{C0}\left(\frac{1}{0}\right) = \frac{-2}{2} - \frac{4}{0} -$$

So dividing any thing with ~~respect to~~ 0 results in ∞ (infinite). This means we can't solve the above equation so let us apply some other technique. We will see in how many ways we can tackle the above problem.

From the given ckt. we can write.

$$V_{A0} = V_{B0} \quad (i) \quad \rightarrow \quad 14V$$

Mesh and Nodal Analysis in Passive Circuits

$$V_{AO} = V_{CO} - 4 \quad \text{--- (i)}$$

Let the current x flows in the branch AC from node A to node C.

At node A, writing KCL,

$$-I_1 - I_2 - x = 0$$

$$V_{AO} \left(\frac{1}{4} + \frac{1}{2} \right) - V_{BO} \times \frac{1}{2} = -\frac{2}{2} - x \quad \text{--- (ii)}$$


where $I_1 = \frac{V_{AO}}{4}$, $I_2 = \frac{V_{AO} - (V_{BO} - 2)}{2} = \frac{V_{AO}}{2} - \frac{V_{BO} - 2}{2}$

Now writing KCL at node B, we get

$$I_2 - I_3 - I_4 = 0$$

$$\frac{V_{AO} - (V_{BO} - 2)}{2} - \frac{V_{BO} - 5}{6} - \frac{V_{BO} - V_{CO}}{8} = 0$$
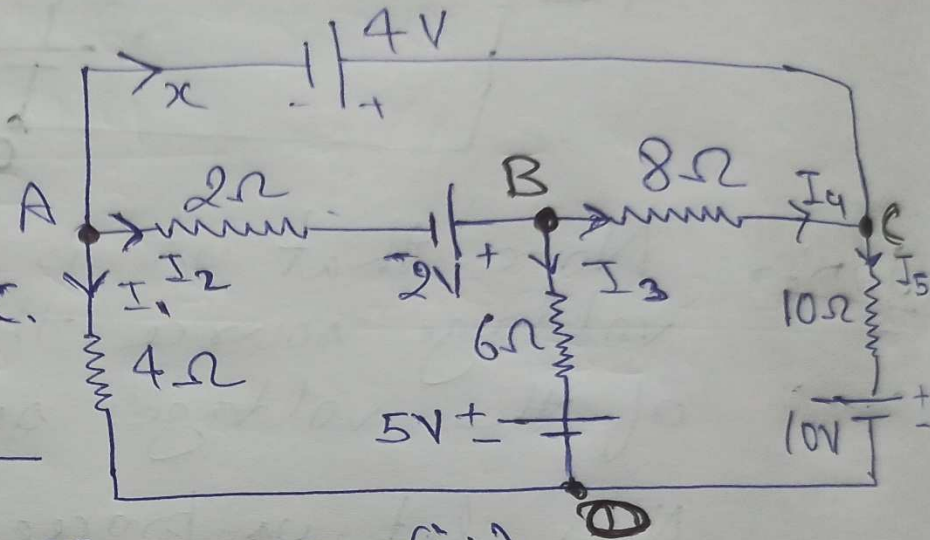
$$\text{or, } -\frac{1}{2} V_{AO} + V_{BO} \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{8} \right) - \frac{1}{8} V_{CO} = \frac{2}{2} + \frac{5}{6} \quad \text{--- (iii)}$$



Mesh and Nodal Analysis in Passive Circuits

Now writing KCL at node c

$$I_4 + x - I_5 = 0$$

$$\frac{V_{B0} - V_{C0}}{8} + x - \frac{V_{C0} - 10}{10} = 0$$

$$-\frac{V_{B0}}{8} + V_{C0} \left(\frac{1}{8} + \frac{1}{10} \right) = \frac{10}{10} + x \quad \text{--- (iv)}$$

Now to solve, putting value of $V_{A0} = V_{C0} - 4$ from eqn (i) in eqn. (iii) we get,

$$-\frac{1}{2} (V_{C0} - 4) + V_{B0} \left(\frac{12 + 4 + 3}{24} \right) - \frac{1}{8} V_{C0} = \frac{11}{6}$$

$$\text{or, } \frac{19 V_{B0}}{24} - \left(\frac{1}{2} + \frac{1}{8} \right) V_{C0} = \frac{11}{6} - 2$$

$$\text{or, } \frac{19 V_{B0} - 15 V_{C0}}{24} = \frac{-1}{6}$$

$$19 V_{B0} - 15 V_{C0} = -4 \quad \text{--- (v)}$$

Mesh and Nodal Analysis in Passive Circuits

$$\text{or, } 19V_{B0} - 15V_{C0} = -4 \quad \text{--- (v)}$$

putting value of V_{A0} from eqn. (i) into eqn. (ii)

$$(V_{C0} - 4) \left(-\frac{3}{4}\right) - \frac{V_{B0}}{2} = -1 - x$$

$$\text{or, } \frac{-2V_{B0} + 3V_{C0}}{4} = -1 - x + 3$$

$$\text{or, } -2V_{B0} + 3V_{C0} = 8 - 4x \quad \text{--- (vi)}$$

Solving eqn. (iv) yields.

$$\frac{-5V_{B0} + 9V_{C0}}{40} = 1 + x$$

$$\text{or, } -5V_{B0} + 9V_{C0} = 40 + 40x \quad \text{--- (vii)}$$

Multiplying eqn. (vi) by 10 and adding ^{with} eqn. (vii)

Mesh and Nodal Analysis in Passive Circuits

$$\begin{array}{rcl} -20V_{B0} + 30V_{C0} & = & 80 - 40x \\ -5V_{B0} + 9V_{C0} & = & 40 + 40x \\ \hline -25V_{B0} + 39V_{C0} & = & 120 \quad \text{--- (viii)} \end{array}$$

$$\text{or, } V_{C0} = \frac{120 + 25V_{B0}}{39}$$

Now putting value of V_{C0} in eqn. (vi) we get

$$19V_{B0} - \frac{15(120 + 25V_{B0})}{39} = -4$$

$$\text{or, } 741V_{B0} - 375V_{B0} - 1800 = -4 \times 39$$

$$\text{or, } 366V_{B0} = -156 + 1800$$

$$\text{or, } V_{B0} = \frac{1644}{366} \approx 4.5 \text{ V}$$

Mesh and Nodal Analysis in Passive Circuits

$$V_{co} = \frac{120 + 25 \times 4.5}{39} = \frac{120 + 112.5}{39} \approx 6V$$

$$\begin{aligned} V_{AO} &= V_{co} - 4V \\ &= 6V - 4V = 2V \end{aligned}$$

So different branch currents are,

$$I_1 = \frac{V_{AO}}{4} = \frac{2V}{4\Omega} = 0.5A$$

$$I_2 = \frac{2 - (4.5 - 2)}{2} = \frac{2 - 2.5}{2} = -\frac{0.5}{2} A = -0.25A$$

This means direction I_2 is from B to A.

$$I_3 = \frac{4.5 - 5}{6} = -\frac{0.5}{6} A = -0.083 A = -83 mA$$

$$I_4 = \frac{4.5 - 6}{8} = -\frac{1.5}{8} A \approx -0.19 A$$

Mesh and Nodal Analysis in Passive Circuits

$$I_5 = \frac{6 - 10}{10} \text{ A} = \frac{-4}{10} \text{ A} = -0.4 \text{ A}$$

By KCL at node A we have,

$$-I_1 - I_2 - x = 0$$

$$I_1 + I_2 + x = 0$$

$$0.5 \text{ A} - 0.25 \text{ A} + x = 0$$

or, $x = -0.25 \text{ A}$ so the direction of

current x is from C to A.

Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You