

Paper 1, TDC Part-1
Chapter– 3, Mesh and Node Analysis
Nodal Analysis -5

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics


L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Mesh and Nodal Analysis in Passive Circuits

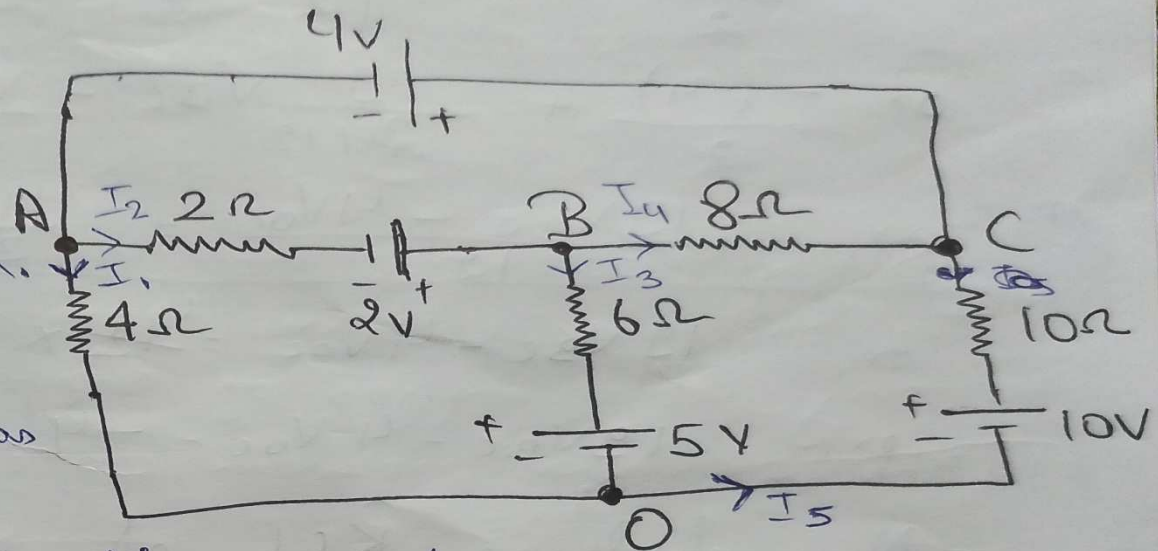Question

We solve this problem by another method. In this method we take node C as reference node.



first name all the nodes A, B, C & O. Let the voltages of this nodes are V_A, V_B, V_C, V_O respectively. Also let the currents I_1, I_2, I_3, I_4 & I_5

Now let us consider 'C' as reference node then we have to find V_{AC}, V_{BC} & V_{OC} .

and $V_{AC} = -4V$

Mesh and Nodal Analysis in Passive Circuits

So we get V_{AC} so there is no need to write KCL at node A.

Now we have to apply KCL at node B we get

$$I_2 - I_3 - I_4 = 0$$

$$\frac{V_{AB} + 2}{2} - \frac{V_{BO} - 5}{6} - \frac{V_{BC}}{8} = 0$$

$$\frac{V_{AC} - V_{BC} + 2}{2} - \frac{V_{BC} - V_{OC} - 5}{6} - \frac{V_{BC}}{8} = 0$$

$$-\frac{V_{AC}}{2} + V_{BC} \left(\frac{1}{2} + \frac{1}{6} + \frac{1}{8} \right) - \frac{V_{OC}}{6} = \frac{5}{6} + 1 = \frac{11}{6}$$

$$\text{or, } -\frac{(-4)}{2} + \frac{19}{24} V_{BC} - \frac{V_{OC}}{6} = \frac{11}{6}$$

$$\text{or, } \frac{19V_{BC} - 4V_{OC}}{12} = \frac{11}{3} - 4$$

Mesh and Nodal Analysis in Passive Circuits

$$\text{or, } \frac{19V_{BC} - 4V_{OC}}{12} = \frac{11}{3} - 4$$

$$\text{or, } 19V_{BC} - 4V_{OC} = 12 \times \frac{11}{3} - 4 = -4$$

$$\text{or, } 19V_{BC} - 4V_{OC} = -4 \Rightarrow V_{BC} = \frac{-4 + 4V_{OC}}{19}$$

Now applying KCL at node O, we get

$$I_1 + I_3 - I_5 = 0$$

$$\frac{V_{AO}}{4} + \frac{V_{BO} - 5}{6} - \frac{V_{OC} + 10}{10} = 0$$

$$\text{or, } \frac{-V_{AO}}{4} - \frac{V_{BO} - 5}{6} - \frac{V_{OC}}{10} + 1 = 0$$

$$\text{or, } -\frac{V_{AO}}{4} - \frac{V_{BO}}{6} + \frac{V_{OC}}{10} = -1 - \frac{5}{6} = -\frac{11}{6}$$

$$\text{or, } -\frac{V_{AC}}{4} - \frac{V_{BC}}{6} + V_{OC} \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{10} \right) = -\frac{11}{6}$$

Mesh and Nodal Analysis in Passive Circuits

Putting $V_{AC} = -4$ we get

$$\frac{-(-4)}{4} - \frac{V_{BC}}{6} + V_{OC} \left(\frac{15+10+6}{60} \right) = \frac{-11}{6}$$

$$\frac{-V_{BC} \times 10 + 31 V_{OC}}{60} = -\frac{11}{6} - 1$$

$$\text{or, } -10 V_{BC} + 31 V_{OC} = \frac{10}{60} \times \frac{-17}{6} = \frac{-5}{9} - 170$$

$$\text{or, } \frac{-10(-4 + 4 V_{OC})}{19} + 31 V_{OC} = -170$$

$$\text{or, } 40 - 40 V_{OC} + 31 \times 19 V_{OC} = -170 \times 19$$

$$\text{or, } (589 - 40) V_{OC} = -3230 - 40 = -3270$$

$$\text{or, } V_{OC} = \frac{-3270}{549} = -5.95 \text{ V}$$

$$V_{OC} \approx -6 \text{ V}$$

Mesh and Nodal Analysis in Passive Circuits

$$V_o - V_c = -6V$$

$$\Rightarrow 0 - V_c = -6V \Rightarrow V_c = 6V$$

$$V_{AC} = -4 \Rightarrow V_A - V_c = -4$$

$$V_A = -4 + V_c = -4 + 6 = 2V$$

$$V_{BC} = \frac{-4 + 4 \times 6}{19} = \frac{-20}{19} \approx -1.05V$$

$$V_B - V_c \approx -1.5V \Rightarrow V_B \approx -1.5 + V_c \\ \approx -1.5 + 6 = 4.5V$$

from this we get,

$$I_1 = \frac{V_{AO}}{4} = \frac{2}{4} = 0.5A,$$

$$I_2 = \frac{V_{AB} + 2}{2} = \frac{V_A - V_B + 2}{2} = \frac{2 - 4.5 + 2}{2} = -0.25$$

Mesh and Nodal Analysis in Passive Circuits

$$I_3 = \frac{V_{BO} - 5}{6} = \frac{V_B - V_O - 5}{6} = \frac{4.5 - 0 - 5}{6} = \frac{-0.5}{6} = -83 \text{ mA}$$

$$I_4 = \frac{V_{BC}}{8} = \frac{V_B - V_C}{8} = \frac{4.5 - 6}{8} \approx 0.19 \text{ A}$$

$$I_5 = \frac{V_{OC} + 10}{10} = \frac{V_O - V_C + 10}{10} = \frac{0 - 6 + 10}{10} = 0.4 \text{ A}$$

Current in Branch AC is let I then

$$I + I_1 + I_2 = 0$$

$$I = -I_1 - I_2 = -0.5 - (-0.25)$$

$$I = -0.25 \text{ A} \quad \text{i.e. direction of current is into the node A.}$$

Mesh and Nodal Analysis in Passive Circuits


Supernode method of Nodal Analysis

The problem discussed earlier can also be solve using nodal analysis by super node. let us consider the previous problem once more.

In Supernode method we treat node A, node B and voltage source together as a sort of super node

and apply KCL to both nodes

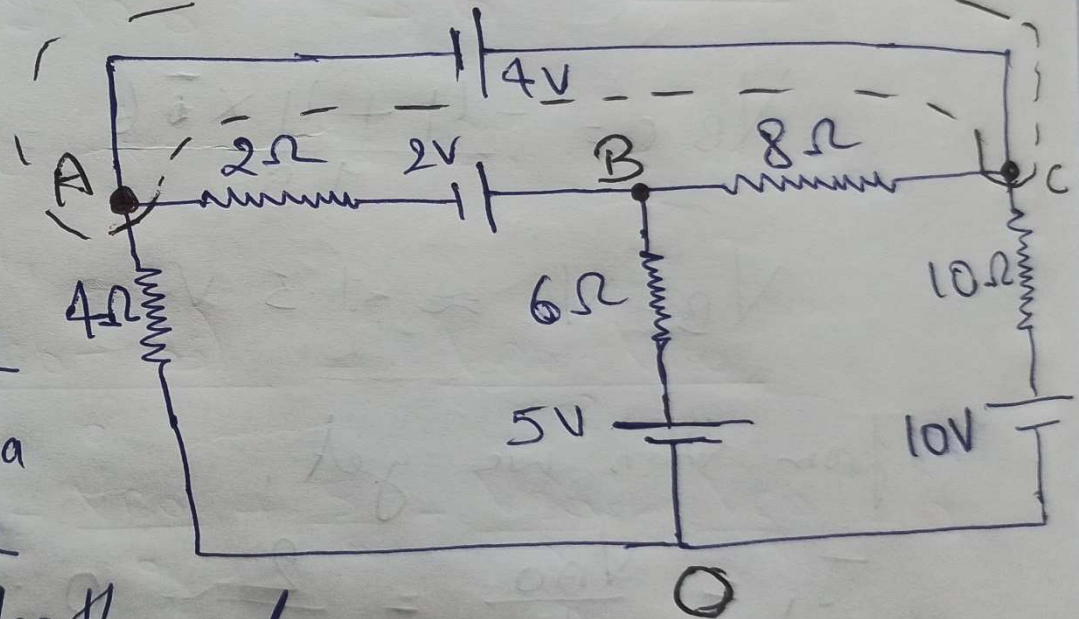at the same time. The super node is indicated by the dotted line in the ckt. shown above



Mesh and Nodal Analysis in Passive Circuits


Supernode method of Nodal Analysis

The problem discussed earlier can also be solve using nodal analysis by super node. let us consider the previous problem once more.

In Supernode method we treat node A, node B and voltage source together as a sort of super node

and apply KCL to both nodes

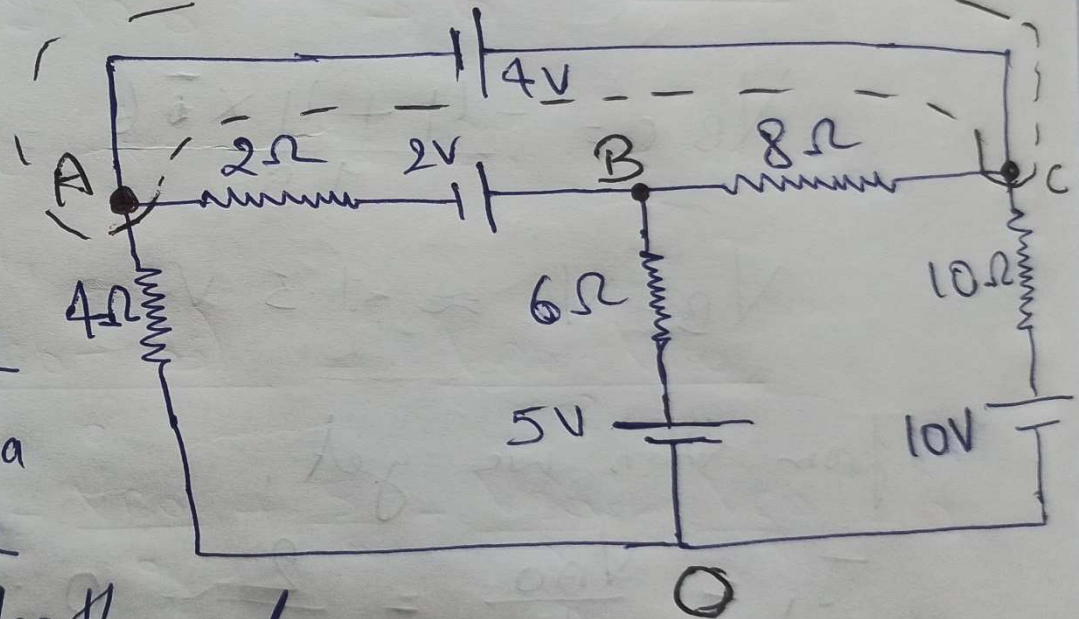at the same time. The super node is indicated by the dotted line in the ckt. shown above





Mesh and Nodal Analysis in Passive Circuits


or, it has been shown separately below also.

As we have treated node A, node C and the voltage source together

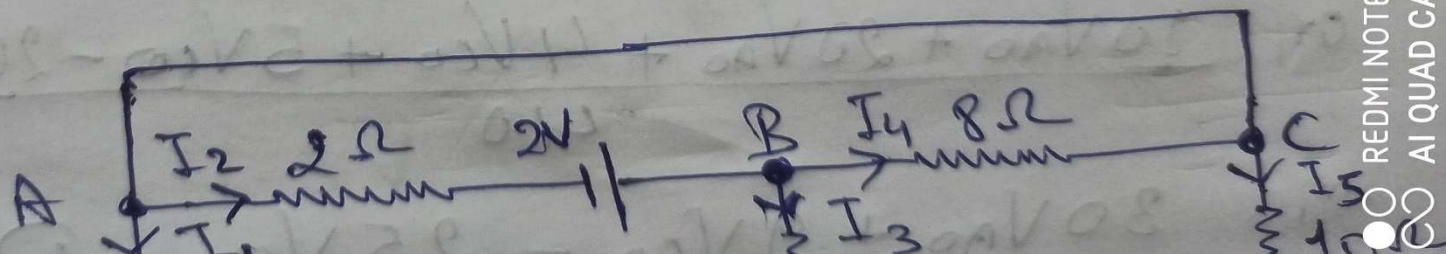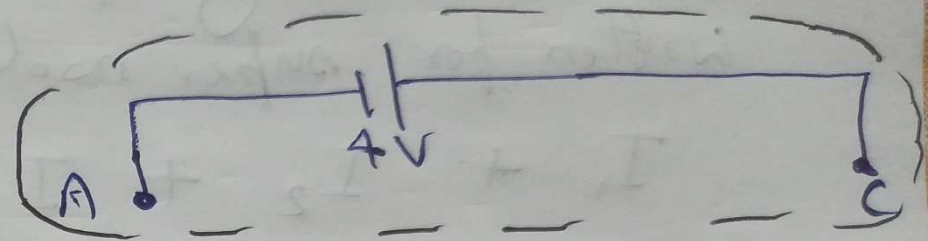as a sort of supernode so the voltage $V_A = V_C$ and hence there will be no current flow in branch AC and also the both nodes A and C will be considered together for writing KCL. The ckt is redrawn once again according to supernode



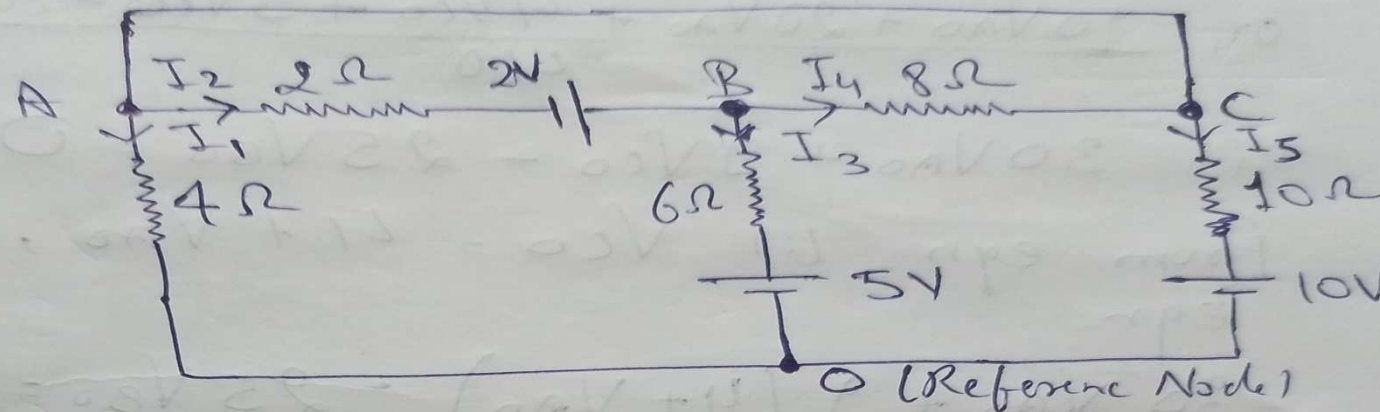Mesh and Nodal Analysis in Passive Circuits



In above ckt. A-C is super node, for this ckt we will assume ~~ckt~~ ^{current} direction as shown in the ckt above. For supernode A-C, current I_1 , I_2 leaving for node A and current I_5 leaving node C while ~~there~~ there is only one entering current i.e. I_4 at node C so KCL for supernode A-C is written,

$$I_1 + I_2 + I_5 = I_4$$

Also for branch AC there is 4V voltage source between nodes A and C so we have.

$$V_A - V_C = -4V \Rightarrow \boxed{V_C = V_A + 4V} \quad \text{--- (i)}$$

Mesh and Nodal Analysis in Passive Circuits

Now substituting eqn. for I_1, I_2, I_4 & I_5 in KCL written for super node A-C. i.e.

$$I_1 + I_2 + I_5 = I_4$$

$$\frac{V_{AO}}{4} + \frac{V_{AO} - (V_{BO} - 2)}{2} + \frac{V_{CO} - 10}{10} = \frac{V_{BO} - V_{CO}}{8}$$

$$\text{or, } \frac{V_{AO}}{4} + \frac{V_{AO}}{2} - \frac{V_{BO}}{2} + \frac{2}{2} + \frac{V_{CO}}{10} - \frac{10}{10} = \frac{V_{BO}}{8} - \frac{V_{CO}}{8}$$

$$\text{or, } \frac{V_{AO}}{4} + \frac{V_{AO}}{2} + \frac{V_{CO}}{10} + \frac{V_{CO}}{8} - \frac{V_{BO}}{2} - \frac{V_{BO}}{8} = 0$$

$$\text{or, } \frac{10V_{AO} + 20V_{AO} + 4V_{CO} + 5V_{CO} - 20V_{BO} - 5V_{BO}}{40} = 0$$

$$\text{or, } 30V_{AO} + 9V_{CO} - 25V_{BO} = 0$$

From eqn. (i) $V_{CO} = 4 + V_{AO}$, putting in above

Mesh and Nodal Analysis in Passive Circuits

From eqn. (i) $V_{C0} = 4 + V_{A0}$, putting in above eqn.

$$30 V_{A0} + 9(4 + V_{A0}) - 25 V_{B0} = 0$$

$$\text{or } 25 V_{B0} - 39 V_{A0} = 36 \quad \text{--- (ii)}$$

Now ~~the~~ writing KCL at node B, we have:

$$I_2 = I_3 + I_4$$

$$\frac{V_{A0} - (V_{B0} - 2)}{2} = \frac{(V_{B0} - 5)}{6} + \frac{V_{B0} - V_{C0}}{8}$$

$$\text{or } \frac{V_{A0}}{2} - \frac{V_{B0}}{2} + \frac{2}{2} - \frac{V_{B0}}{6} + \frac{5}{6} - \frac{V_{B0}}{8} + \frac{V_{C0}}{8} = 0$$

$$\text{or } -\frac{V_{A0}}{2} + \frac{V_{B0}}{2} + \frac{V_{B0}}{6} + \frac{V_{B0}}{8} - \frac{V_{C0}}{8} = 1 + \frac{5}{6} = \frac{11}{6}$$

$$\text{or } \frac{-12V_{A0} + 19V_{B0} - 3V_{C0}}{24 - 4} = \frac{11}{6}$$

Mesh and Nodal Analysis in Passive Circuits

again putting $V_{C0} = 4 + V_{A0}$

$$-12V_{A0} + 19V_{B0} - 3(4 + V_{A0}) = 44$$

$$\Rightarrow 19V_{B0} - 15V_{A0} = 44 + 12 = 56$$

$$\text{or } V_{B0} = \frac{56 + 15V_{A0}}{19}$$

putting this in eqn. (ii) we get,

$$25 \times \left(\frac{56 + 15V_{A0}}{19} \right) - 39V_{A0} = 36$$

On solving it gives, $V_{A0} \approx 2.0V$

$$\text{So, } V_{C0} = 4 + V_{A0} \approx 6.0V$$

$$V_{B0} \approx 4.5V$$

Mesh and Nodal Analysis in Passive Circuits

All currents I_1, I_2, I_3, I_4 & I_5 can be obtained putting values of V_{A0}, V_{B0} & V_{C0} in their respective eqn.

We observe that out of 3 methods that we discuss for this problem, the super node method is more easier method comparison to other two methods. Applying super node method reduces to write 1 eqn. here, so it is more convenient.

Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You