

Paper 1, TDC Part-1
Chapter– 3, Mesh and Node Analysis
Nodal Analysis - 6

By:

Mayank Mausam

Assistant Professor (Guest Faculty)


Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Mesh and Nodal Analysis in Passive Circuits

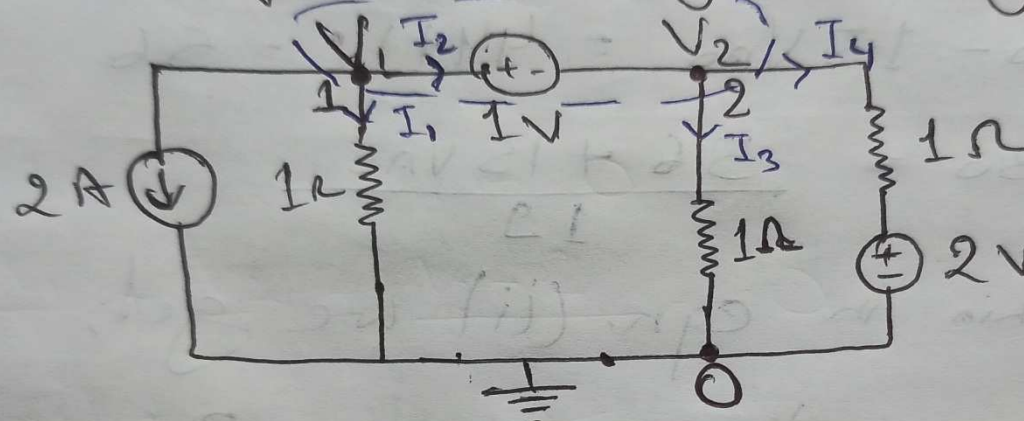Q1) Find V_1 and V_2 and also different branch currents of the ckt given using super node method.



Sol. In the given problem let us first name the nodes which we consider for nodal analysis. Let the nodes are 1, 2 and 0. Where 0 is reference node.

Let the different branch currents are I_1 , I_2 , I_3 & I_4 as shown in the ckt. diagram.




REDMI NOTE 8 PRO
AI QUAD CAMERA

Since there is only voltage source between the nodes 1 and 2 so we will consider 1 and 2 as a super node.

Mesh and Nodal Analysis in Passive Circuits

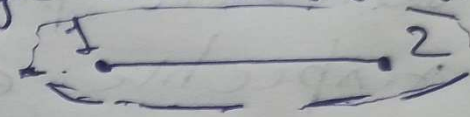Since there is only voltage source between the nodes 1 and 2 so we will consider super node 1-2 (i.e. node 1, 2 and voltage source 1V are ~~part~~ ^{part}) then we have



$$V_1 - V_2 = 1$$

$$\text{or, } V_1 = 1 + V_2 \quad (i)$$

Now applying KCL at supernode (1-2) we get at node 1 there is no incoming current only outgoing currents 2A, I_1 and at node 2 also there is no incoming current, we have only outgoing currents I_3 & I_4 so KCL at supernode (1-2).

$$2 + I_1 + I_3 + I_4 = 0$$

DMI NOTE 8 PRO
QUAD CAMERA

$$\frac{V_1}{1} + \frac{V_2}{1} + \frac{V_2 - 2}{1} = 0$$

Mesh and Nodal Analysis in Passive Circuits

$$\text{or, } 2 + V_1 + V_2 + V_2 - 2 = 0$$

putting $V_1 = 1 + V_2$ from eqn (i) we get,

$$1 + V_2 + V_2 + V_2 = 0 \Rightarrow V_2 = -1/3 \text{ V}$$

$$\text{then, } V_1 = 1 - \frac{1}{3} = \frac{2}{3} \text{ V}$$

So the branch currents are,

$$I_1 = \frac{V_1}{1} = \frac{2}{3} \text{ A}, \quad I_3 = \frac{-1/3}{1} \text{ A} = -\frac{1}{3} \text{ A}$$

$$I_4 = \frac{-\frac{1}{3} - 2}{1} = -\frac{7}{3} \text{ A}$$

Apply KCL at node 1,


$$2 + I_1 + I_2 = 0$$

$$\text{or } I_2 = -(2 + \frac{2}{3}) = -\frac{8}{3} \text{ A}$$

Mesh and Nodal Analysis in Passive Circuits

Now let us discuss this problem by another method where we consider ~~node 1~~ ^{node 2} as reference node

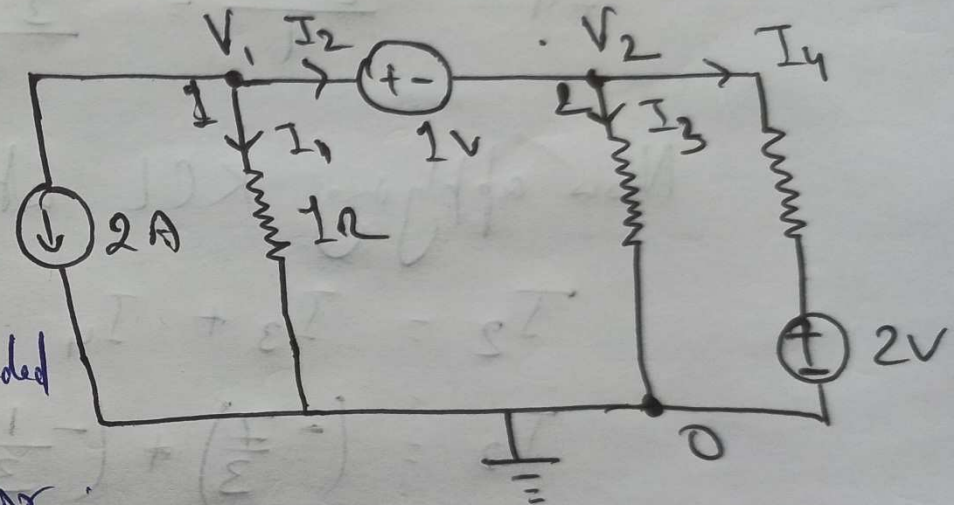In this method again first we identify the nodes that 1, 2 and 0 where node 0 is ~~at~~ grounded



Here we consider V_2 as our reference node. Let the different branch currents are I_1 , I_2 , I_3 & I_4 as shown in figure.

Since node 2 is our reference node so,

$$V_1 - V_2 = 1$$

$$V_1 = 1 + V_2 \quad \text{--- (i)}$$

Mesh and Nodal Analysis in Passive Circuits

As we get V_1 so no need to write KCL for V_1 .
Now our other node is 0. So applying KCL at 0.
we get,

$$2 + I_1 + I_3 + I_4 = 0$$

$$2 + \frac{V_1}{1} + \frac{V_2}{1} + \frac{V_2 - 2}{1} = 0$$

$$2 + (V_2 + 1) + V_2 + V_2 - 2 = 0 \quad \left[\text{Putting } V_1 = V_2 + 1 \right]$$

$$3V_2 + 1 = 0$$

$$V_2 = -1/3$$

$$\text{then } V_1 = 1 - \frac{1}{3} = \frac{2}{3}$$

So the different branch currents are

REDMI NOTE 8 PRO
AI QUAD CAMERA

$$I_1 = \frac{V_1}{1} = \frac{\frac{2}{3}}{1} = \frac{2}{3} \text{ A.}$$

Mesh and Nodal Analysis in Passive Circuits

So the different branch currents are

$$I_1 = \frac{V_1}{1} = \frac{2}{3} = \frac{2}{3} \text{ A}$$

$$I_3 = \frac{V_2}{1} = \frac{-1}{3} = -\frac{1}{3} \text{ A}$$

$$I_4 = \frac{V_2 - 2}{1} = \frac{-\frac{1}{3} - 2}{1} = -\frac{7}{3} \text{ A}$$


Now applying KCL at node 2, we have.

$$I_2 = I_3 + I_4$$

$$I_2 = \left(-\frac{7}{3}\right) + \left(-\frac{1}{3}\right) = -\frac{8}{3} \text{ A}$$

So I_2 is going ~~out~~ from node 2 to 1.

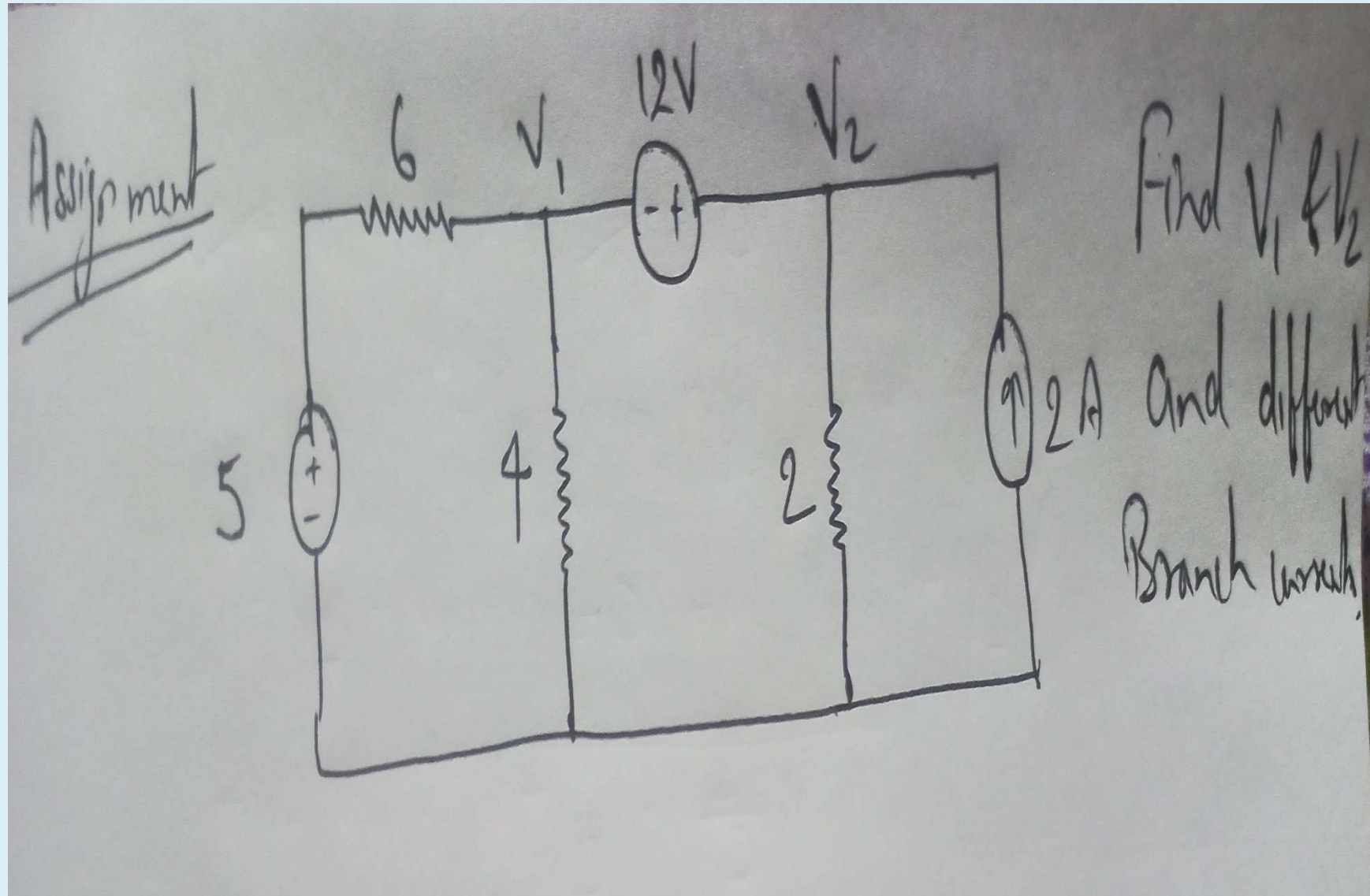Mesh and Nodal Analysis in Passive Circuits



Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You