

Department of Electronics  
LS college, Muzaffarpur

# **POWER AMPLIFIERS**

## **Classification of power a mplifiers**

Dr. Navin kumar

# POWER AMPLIFIERS

## Required

- To deliver a large current to a small load resistance e.g. a audio speaker; or to deliver a large voltage to a large load resistance e.g. switching power supply;
- To be of low output resistance in order to avoid loss of gain and to maintain linearity (to minimize harmonic distortion)
- To deliver power to the load efficiently


# POWER TRANSISTORS - BJT


## Transistor limitations

- 1 maximum rated current,
- 2 maximum rated voltage,
- 3 maximum rated power, and
- 4 maximum allowed temperature.

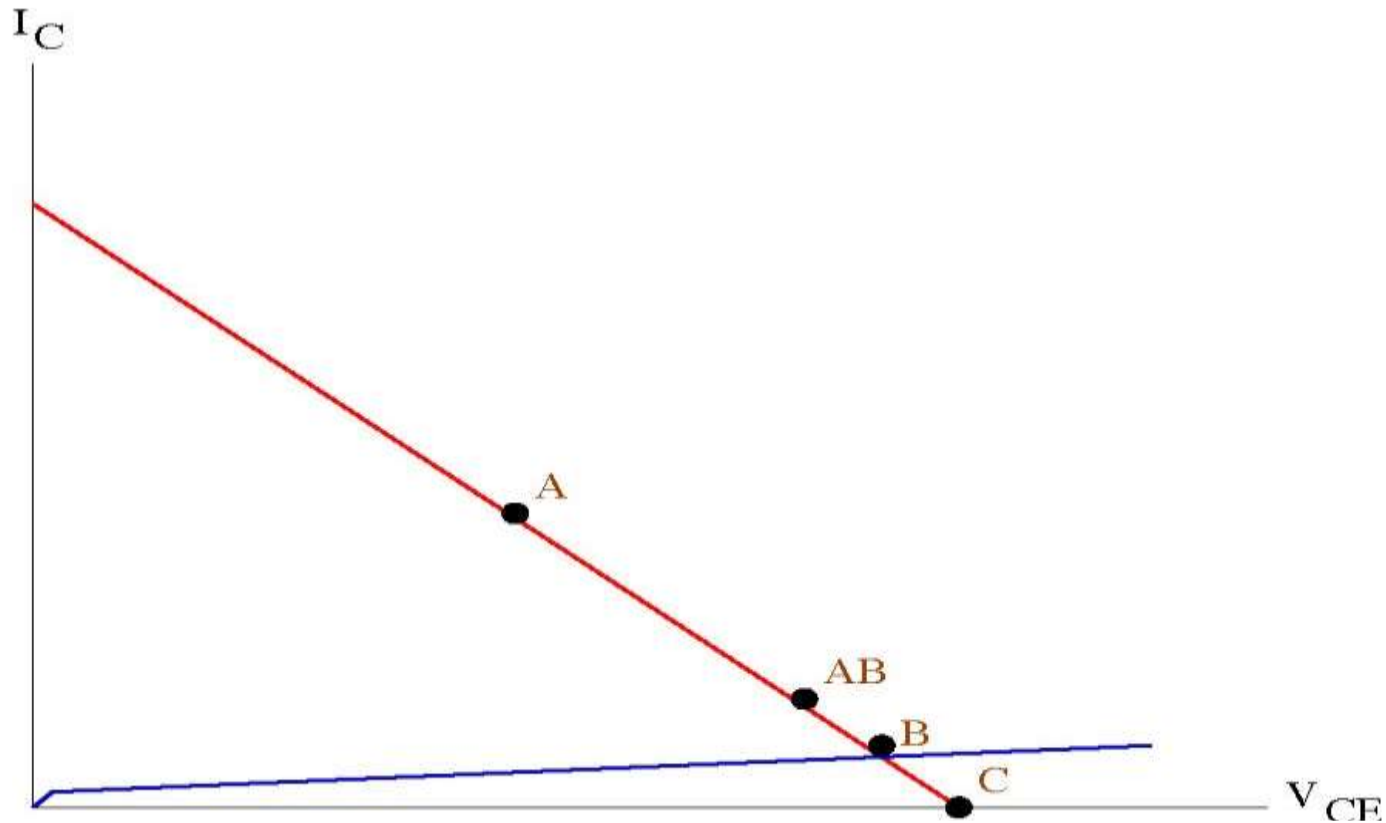
# Classes of Amplifiers

They are grouped together based on their Q-points on the DC load line.




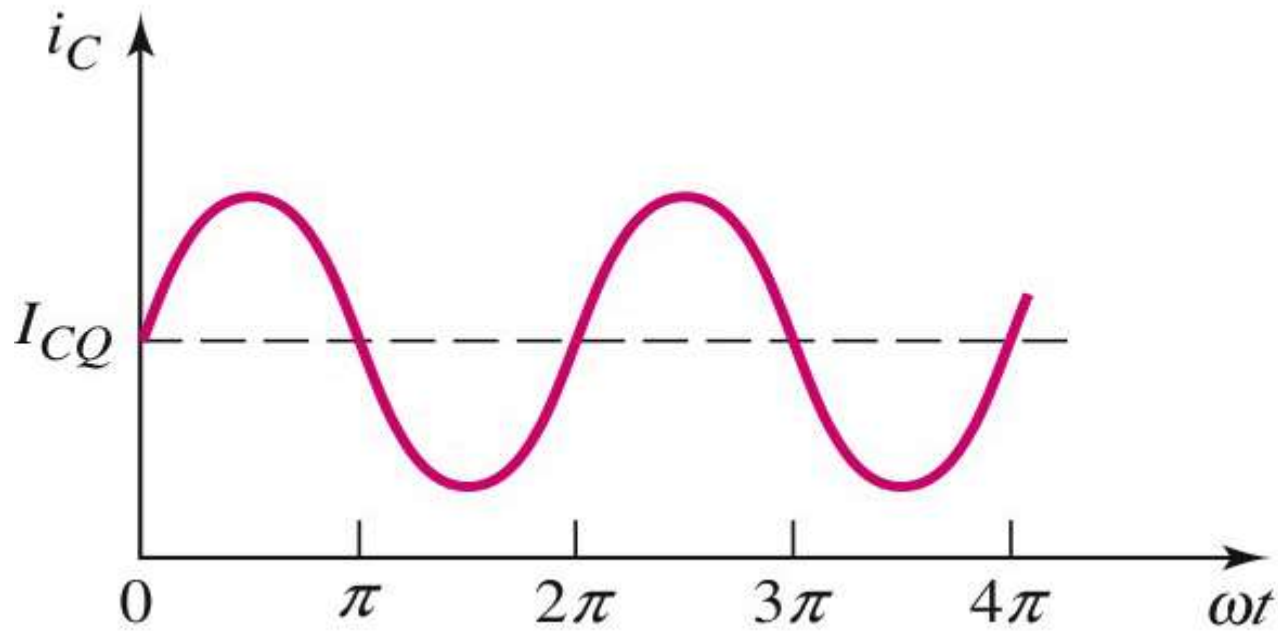

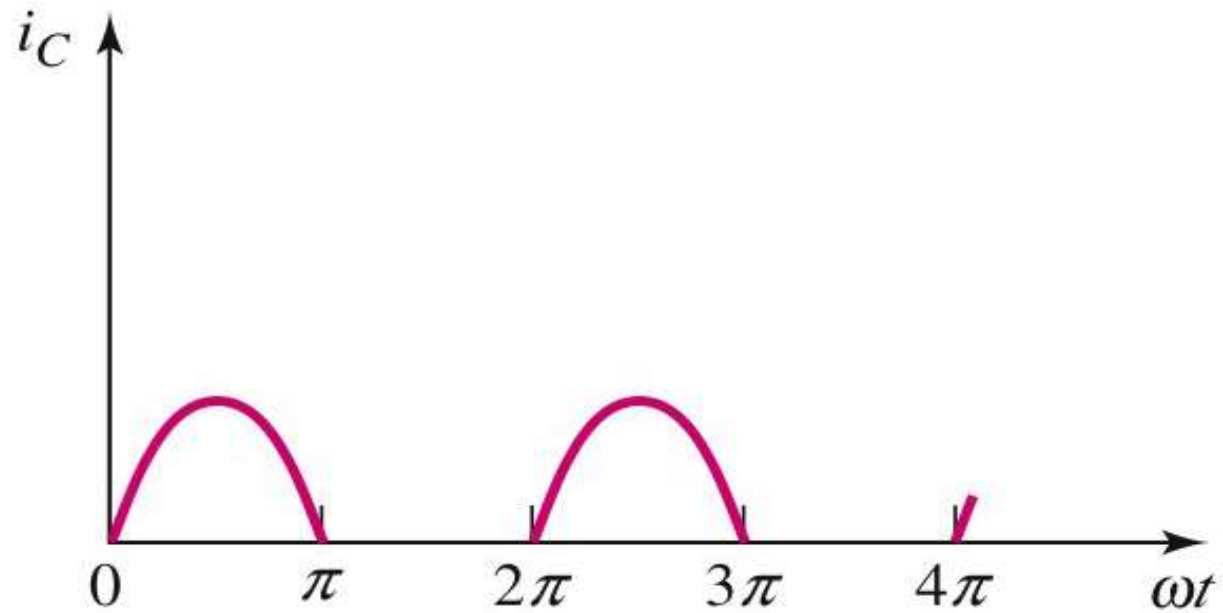
In class-A; the transistor conducts during the whole cycle of sinusoidal input signal



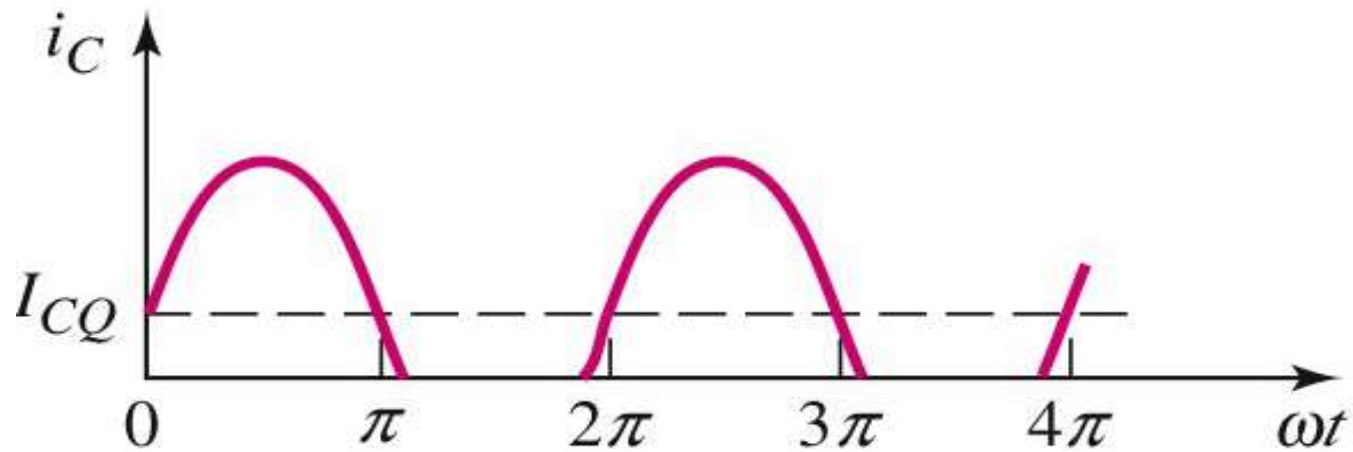In class-B; the transistor conducts during on e-half cycle of input signal



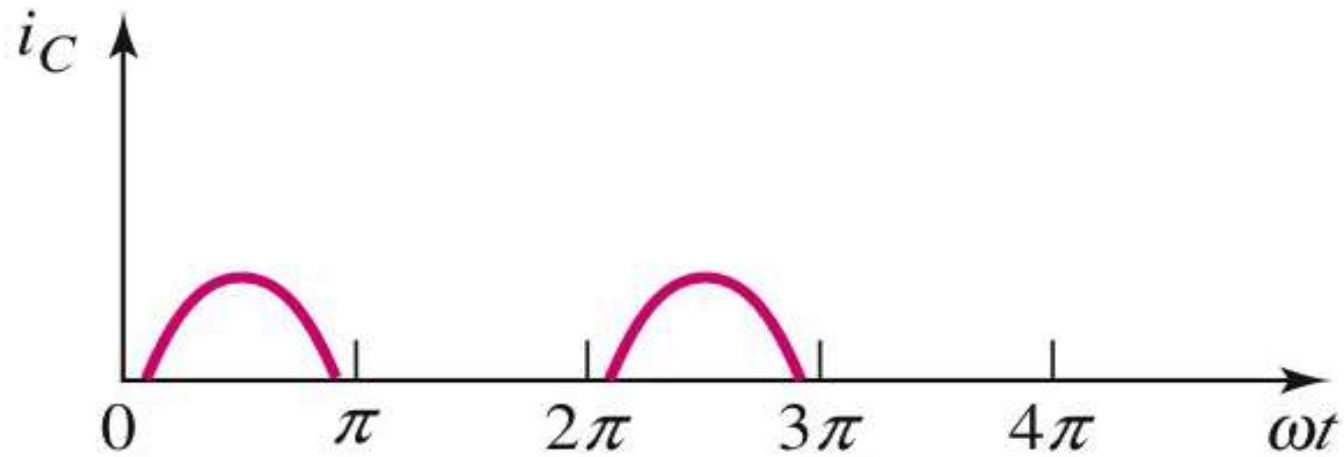In class-AB; the transistor conducts for slightly more than half a cycle of input signal




In class-C; the transistor conducts for less than half a cycle of input signal


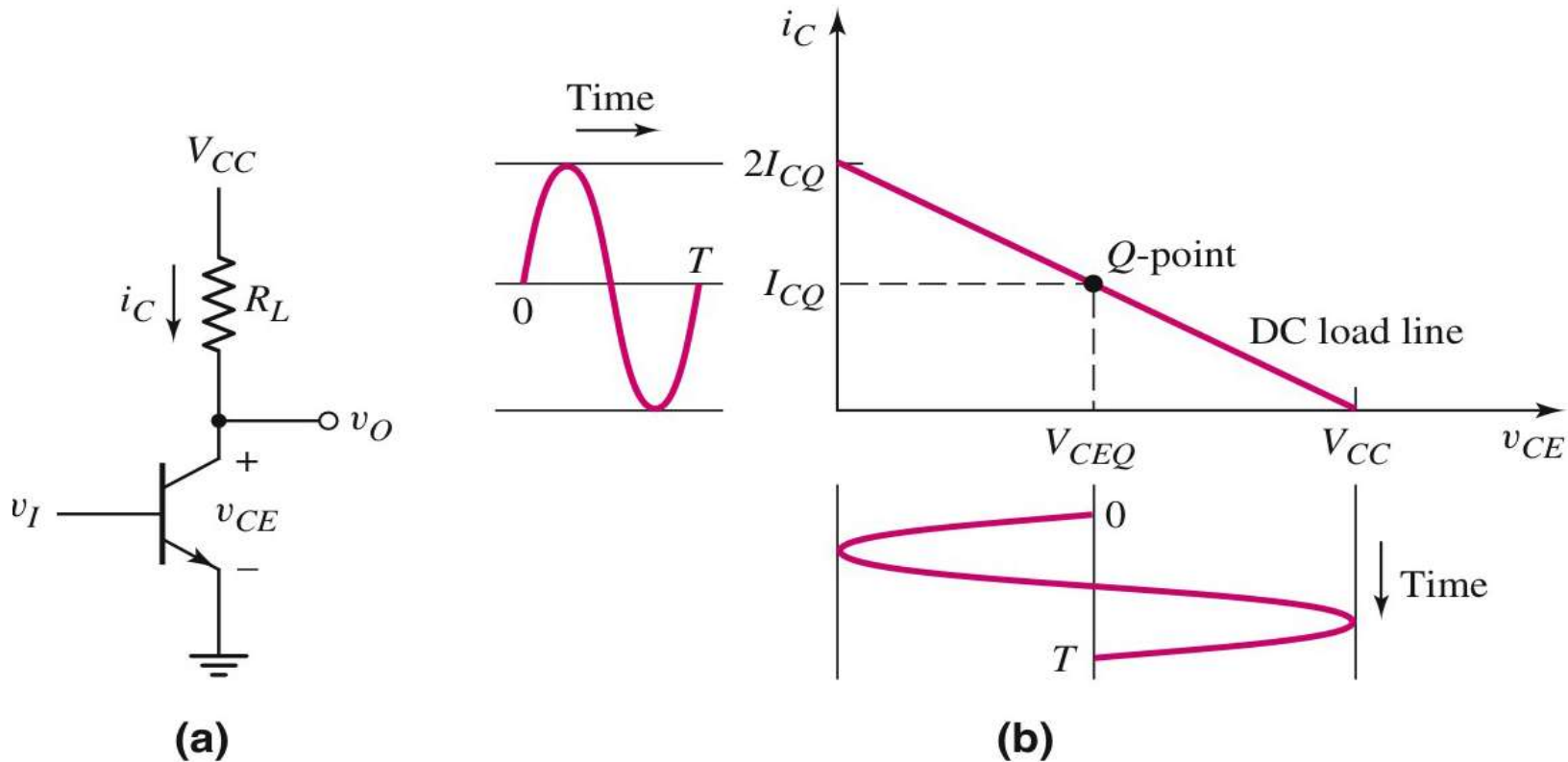
## Cass-A operation

For maximum swing (+ve and -ve), transistor is biased such that the Q point is at centre of the load line.

The transistor conducts for a full cycle of the input signal



Instantaneous power dissipation in transistor is;

$$P_D = V_{CE} i_C$$

For sinusoidal input signal;

$$i_C = I_{CQ} + i_p \sin \omega t$$

And;

$$V_{CE} = \frac{V_{CC}}{2} - v_p \sin \omega t$$


For maximum possible swing;

$$I_{CQ} = \frac{I_{Cp}}{2} \text{ and } v_p = \frac{V_{CC}}{2}$$

Therefore;

$$P_Q = \frac{V_{CC}}{2} (I_{CQ})$$

(See graphical representation)

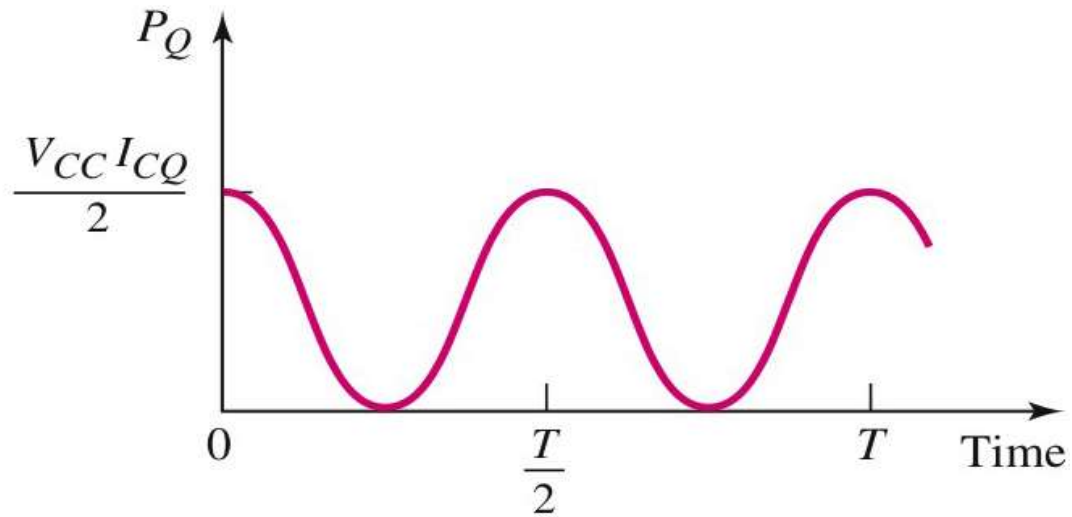

(c)

When the input signal = 0, the transistor must be capable of handling a continuous power of;

$$\frac{V_{CC}I_{CQ}}{2}$$

Efficiency;

$$\eta = \frac{P_L}{P_S}$$

$P_L$  = average ac power to the load

$P_S$  = average power supplied by the source ( $V_{CC}$ )

For maximum possible swing;

$$P_{L2} = \frac{V_{CEQ}^2}{2R_L} = \frac{V_{CC}^2}{4R_L}$$

Power supplied by the source;

$$P_{S_{CC}} = V_{CC} I_{CQ}$$

The efficiency;

$$\eta = \frac{P_{L2}}{P_{S_{CC}}} = \frac{V_{CEQ}^2}{4V_{CC} I_{CQ}}$$

Maximum theoretical efficiency of class A amplifier is therefore 25 %


## **Cass-B operation**

Consists of complementary pair electronic devices


One conducts for one half cycle of the input signal and the other conducts for another half of the input signal

Both devices are off when the input is zero


(See Figure)

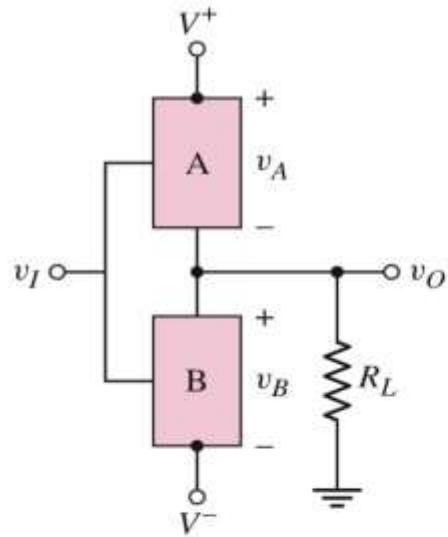


(a)

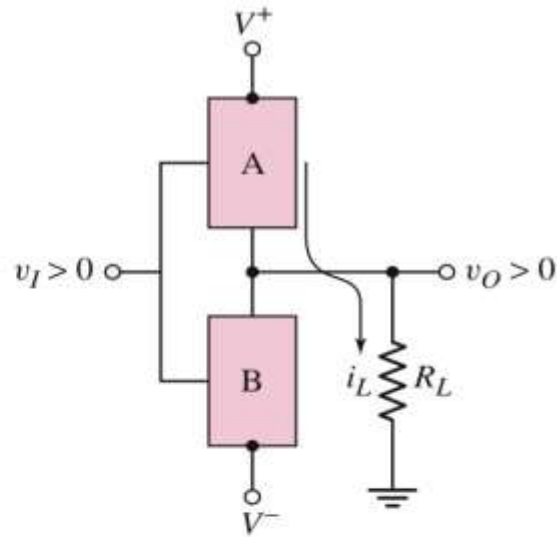

(b)

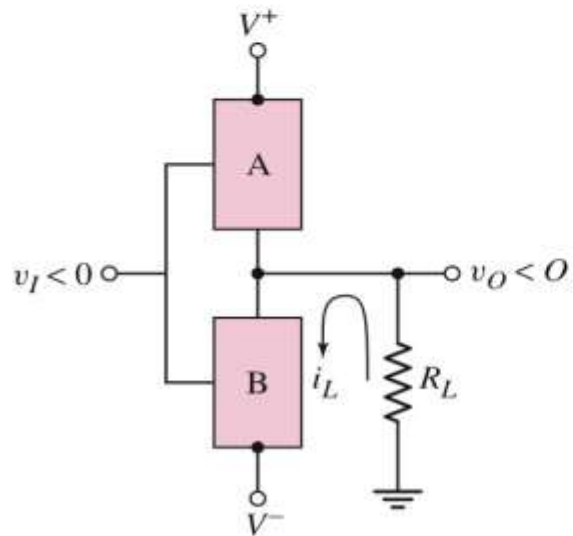

(c)

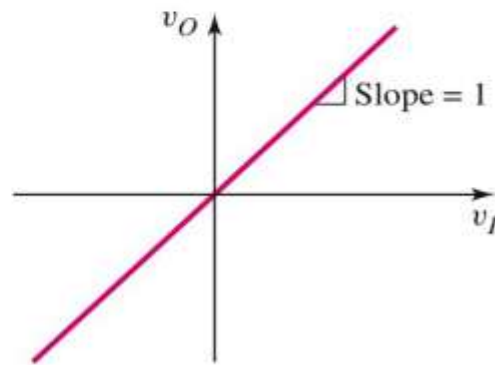

(d)


# Complementary push-pull circuit

Assuming ideal transistor;

when  $v_I = 0$ ;  
both  $Q_n$  &  $Q_p$  are off;

when  $v_I > 0$ ;  
 $Q_n$  conducts &  $Q_p$  is off;

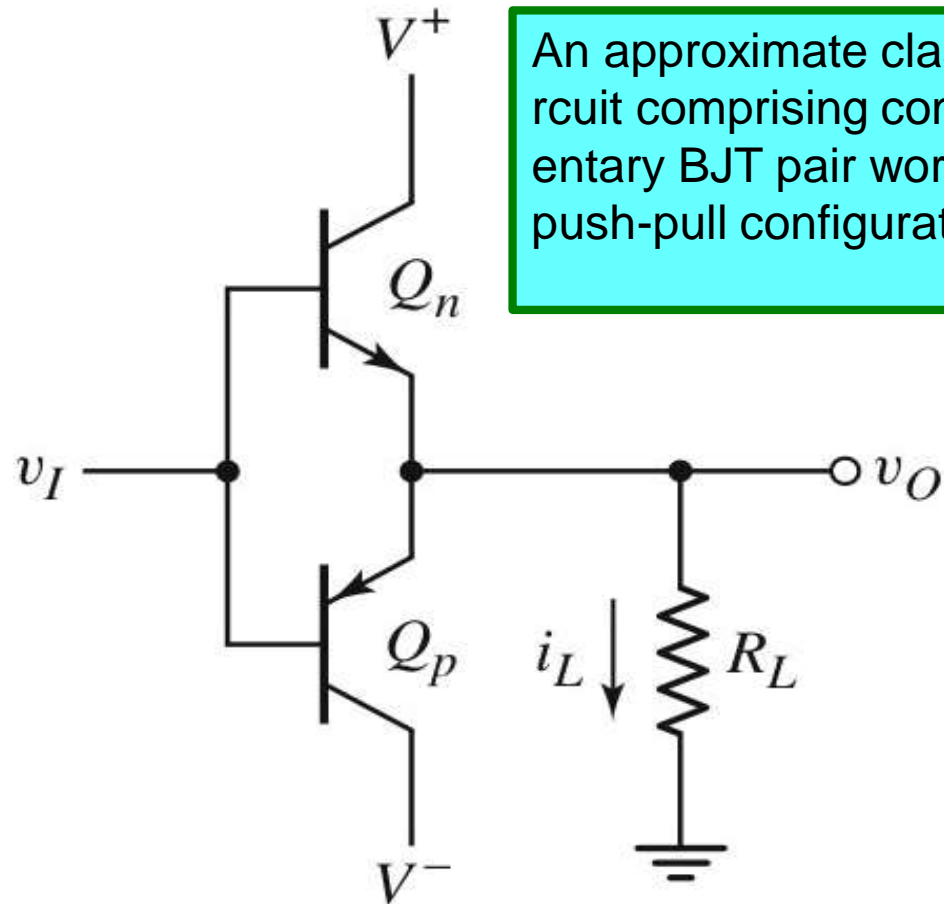when  $v_I < 0$ ;  
 $Q_p$  conducts &  $Q_n$  is off






Assuming cut-in voltage of transistor is 0.6 V,  $v_O = 0$  for a range  $0.6 \text{ V} < v_I < 0.6 \text{ V}$ .

The transfer characteristic becomes non-linear (See Figure)


The range where both transistors are simultaneously off known as the *dead band*



The output will be distorted – **crossover distortion** (See Figure)

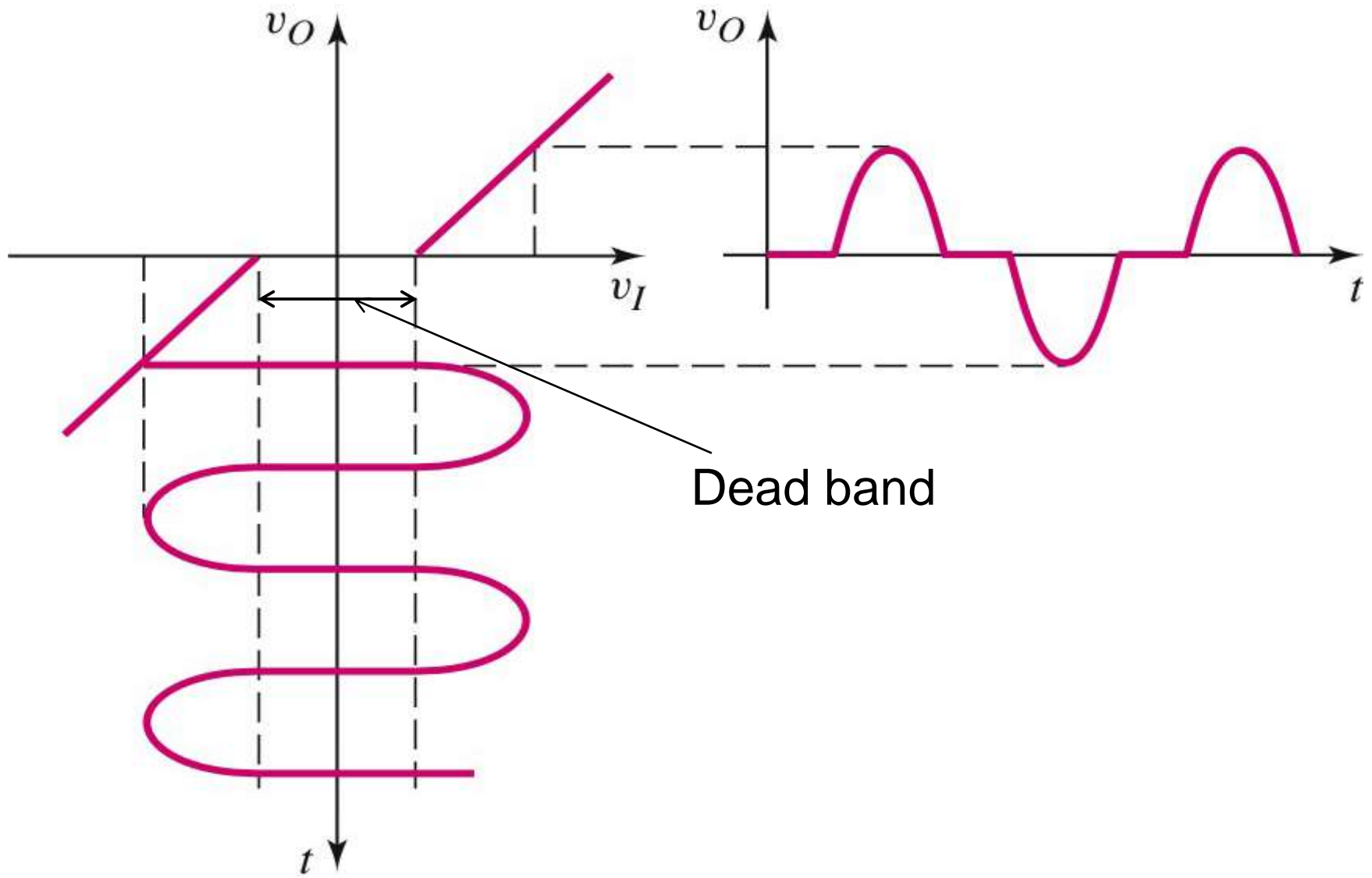Crossover distortion can be eliminated by biasing the transistor with small quiescent current – class-AB


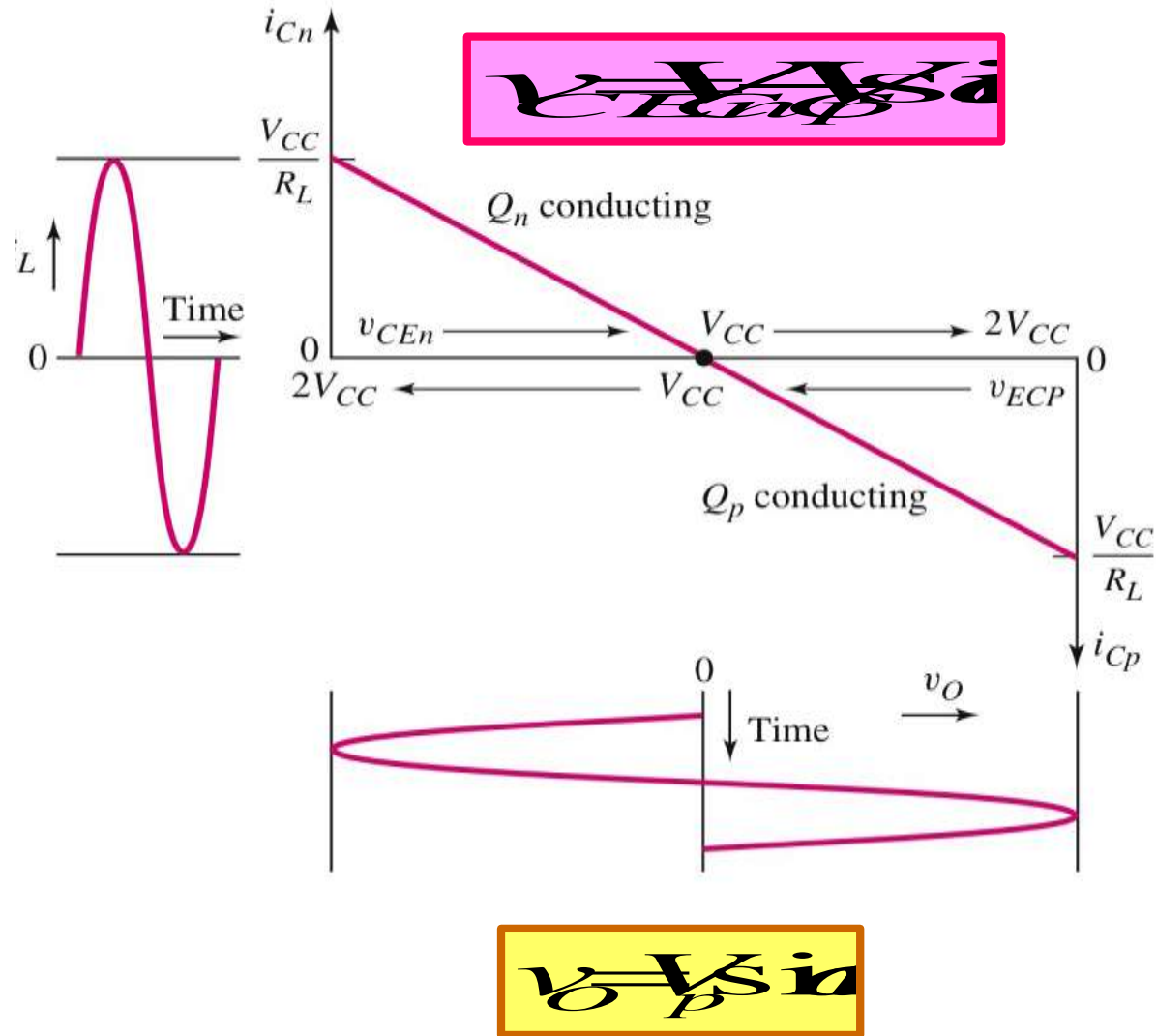
# Theoretical maximum efficiency of class-B amplifiers



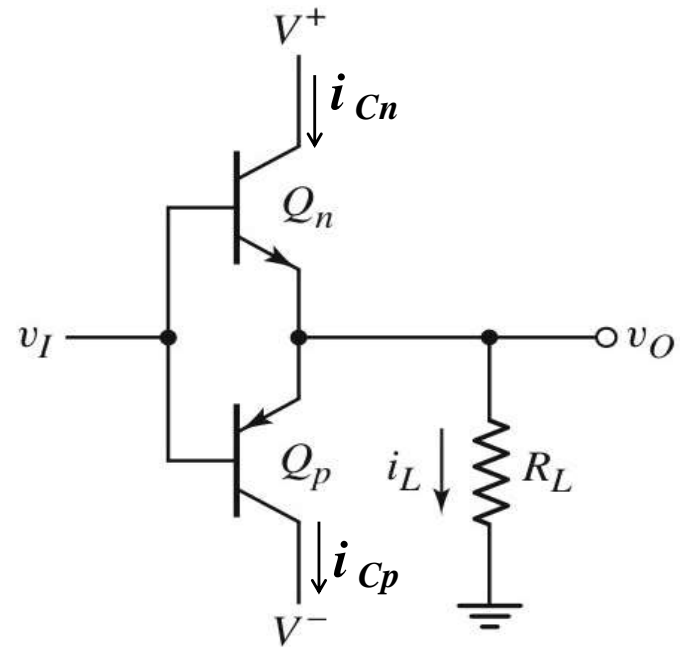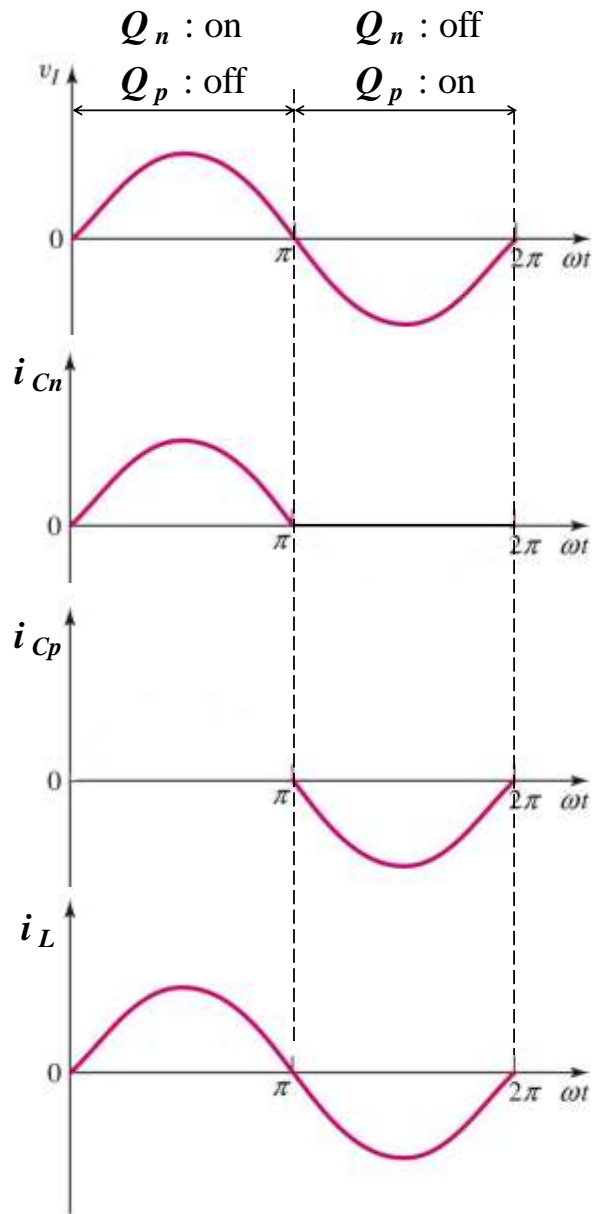

$$v_o = V_p \sin \omega t$$


Maximum possible value of  $V_p$  is  $V_{CC}$ .

~~$$v_o = V_p \sin \omega t$$~~

~~$$i_{Cn} = \frac{V_p}{R_L} \sin \omega t$$~~

and

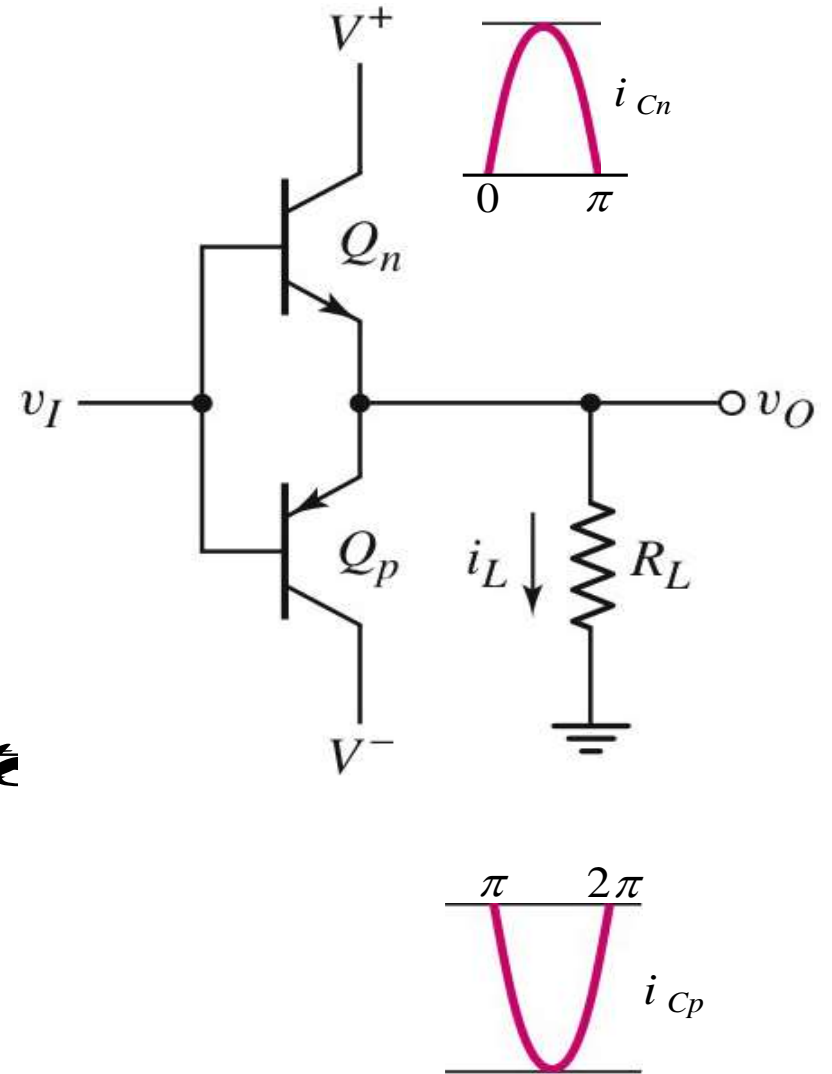~~$$i_{Cp} = \frac{V_p}{R_L} \sin \omega t$$~~



The instantaneous power in  $Q_n$  is;

$$P_{Qn} = v_c i_c$$

$$= \left( V_{CC} - V_p \sin \omega t \right) \left( \frac{V_p \sin \omega t}{R_L} \right)$$

for  $0 < \omega t < \pi$

and

$$P_{Qn} = 0 \quad \text{for } \pi < \omega t < 2\pi$$

The average power in  $Q_n$  is;

$$P_{Qn} = \frac{V_{CC} V_p}{\pi R_L} - \frac{V_p^2}{4R_L}$$

$$P_{Qn} = P_Q \quad (\text{symmetry})$$

Differentiating for maximum  $P_{Qn}$  with respect to  $V_p$  gives us;

$$P_{Qn}(\text{max}) = \frac{V_{CC}^2}{\pi R_L}$$

$$\left( \text{when } \frac{V_p}{V_{CC}} = \frac{2}{\pi} \right)$$

Since each power source supplies half sinewave of current, the average value is;

$$I_S = \frac{V_p}{\pi R_L}$$

The total power supplied by the two sources is;


$$P_S = V_{CC} I_C = 2V_{CC} \left( \frac{V_p}{R_L} \right)$$

The power delivered to the load is;

$$P_L = \frac{V_{(rms)}^2}{R_L} = \frac{(V_p/\sqrt{2})^2}{R_L} = \frac{V_p^2}{2R_L}$$

The efficiency is;
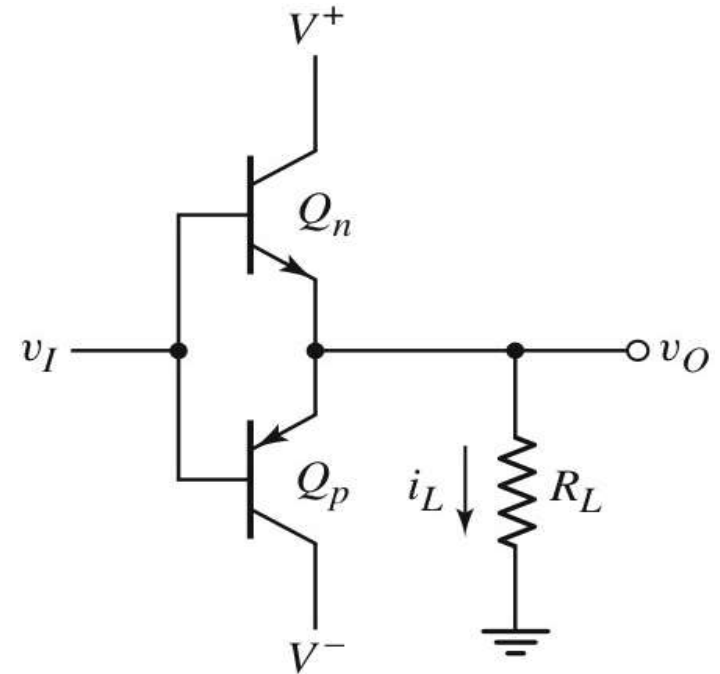
$$\eta = \frac{P_L}{P_S} = \frac{V_p}{4V_{CC}}$$





Maximum efficiency occurs when

$$V_p = V_c$$

Under this condition;


$$\eta = \frac{\pi}{4} = 0.785$$


Maximum theoretical efficiency  
of class B amplifier is therefore  
78.5%
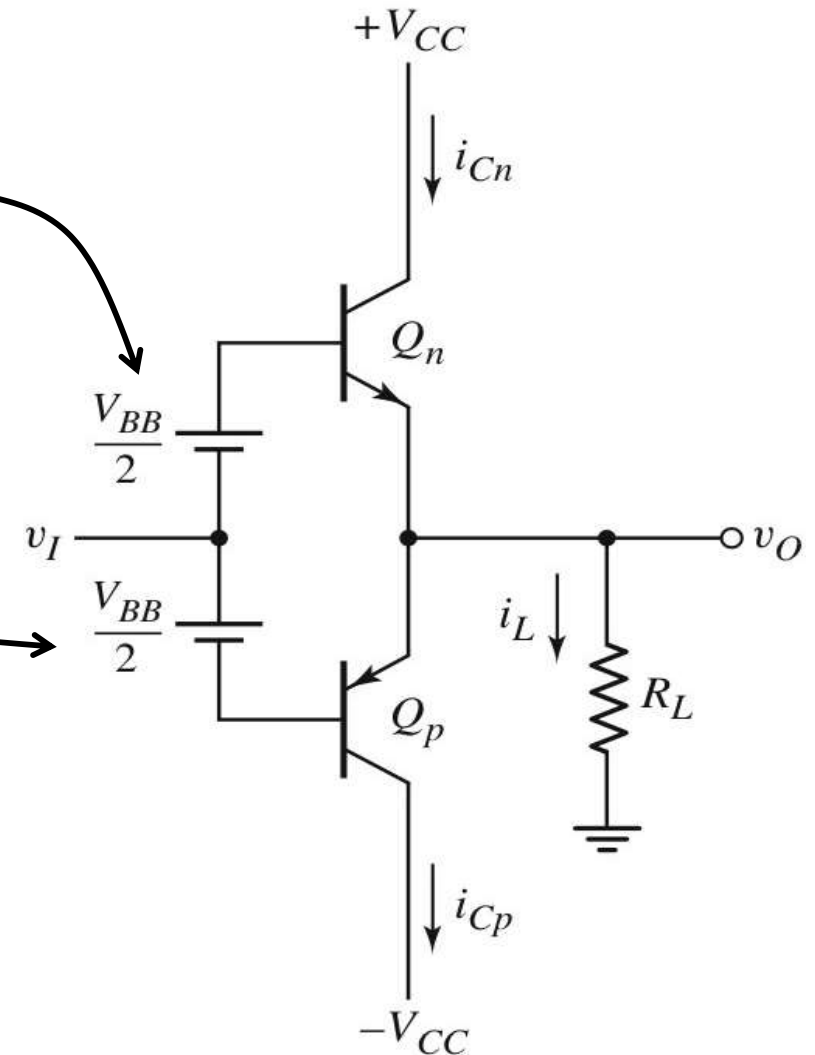
## Cass-AB operation


Small quiescent bias on each output transistor to eliminate crossover distortion

Small  $I_{CQ}$  flows through each transistor in the absence of input signal




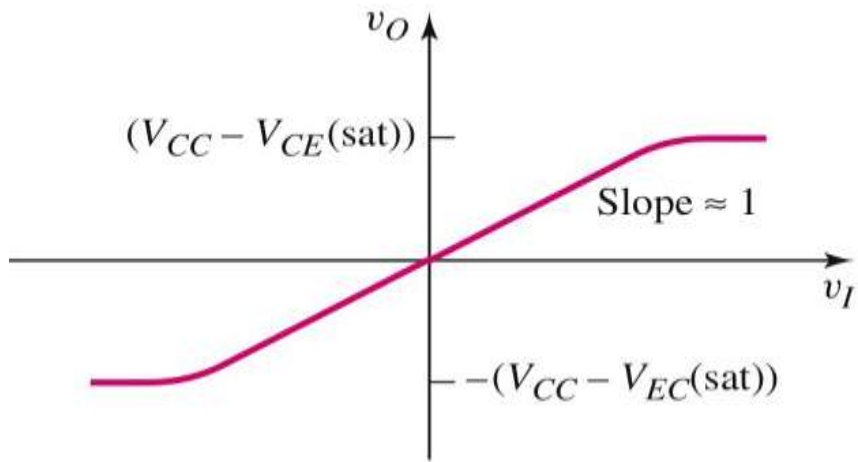


(a)

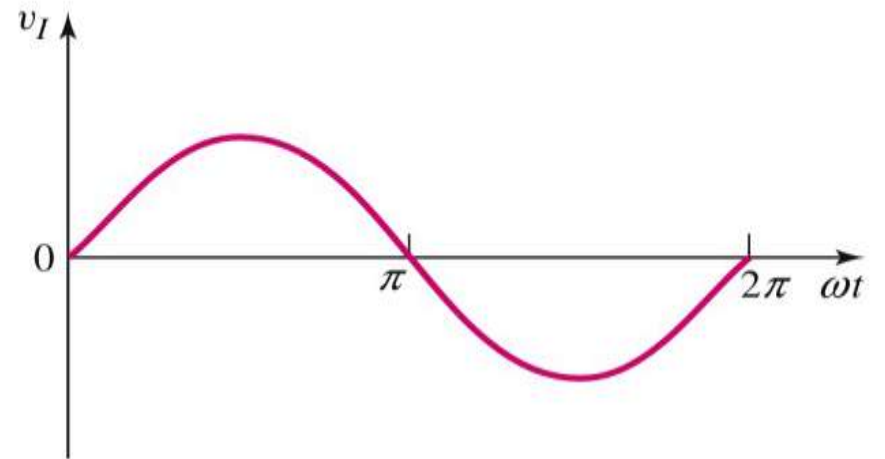

(b)

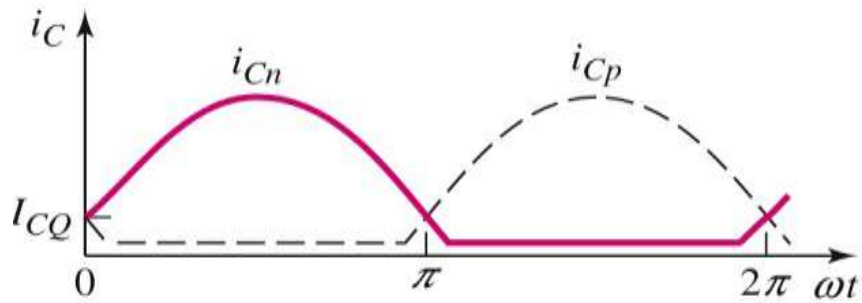


(c)

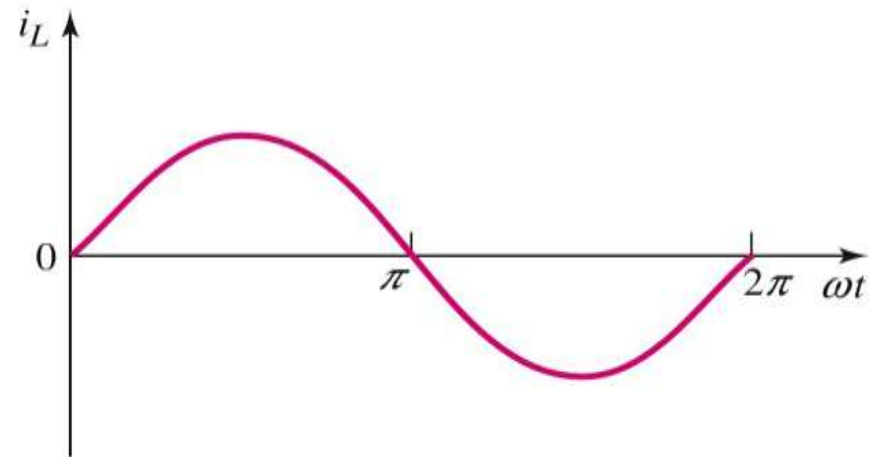

(d)
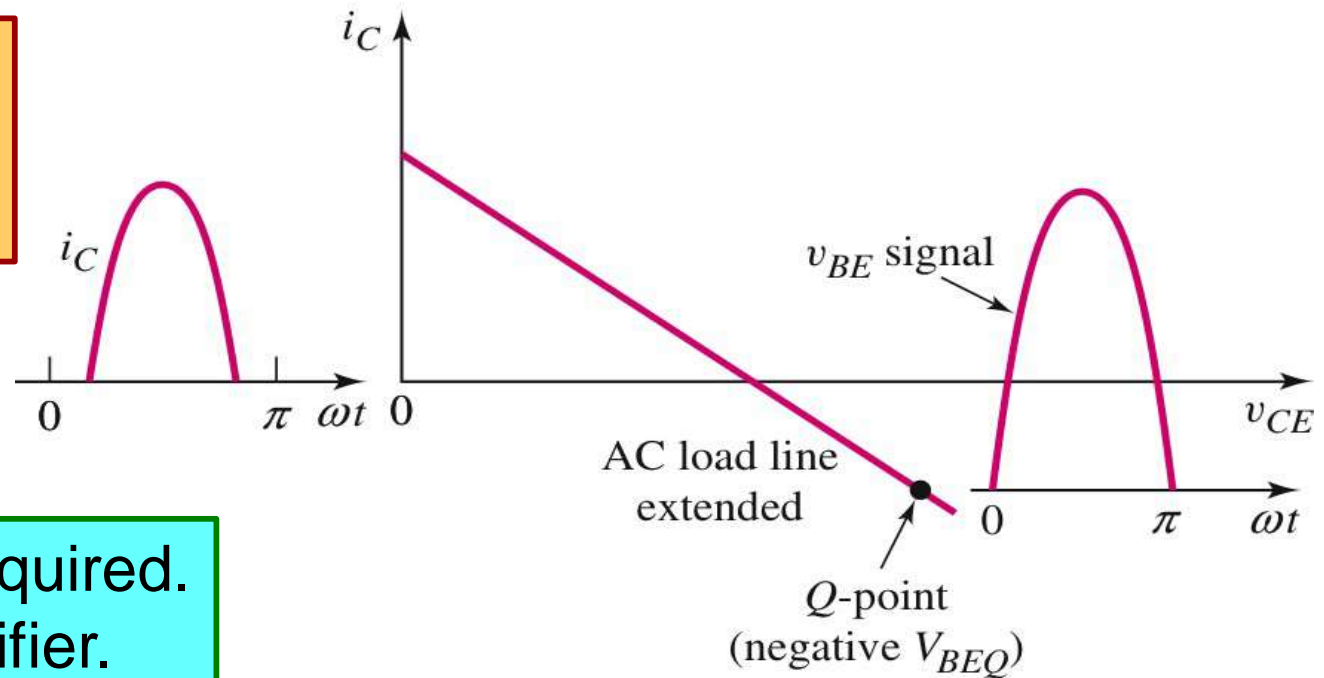
## Cass-C operation

Transistor conducts for less than half a cycle of input signal



- Tuned circuit is required.
- Used for RF amplifier.
- Efficiency  $> 78.5\%$

B – E junction is reverse-biased to obtain Q-point beyond cut-off.