

-3.
=>


Logic gates

The digital ckt. that can be analyzed with the help of Boolean algebra is called Logic Gate or Logic ckt, OR, AND, NOT, and Flip-Flop are the most commonly used logic gates.


→ OR GATES:- This has two or more input and one output. OR gate configuration with diode known as diode Logic (DL) & with transistor is called Transistor Logic (TL). output = Sum of input

$$Y = A + B + \dots$$

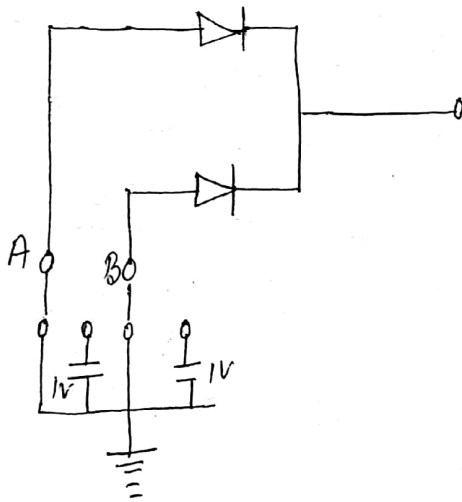
Output is obtained by when any of input is in 'on' state.



(a) Two input OR gate

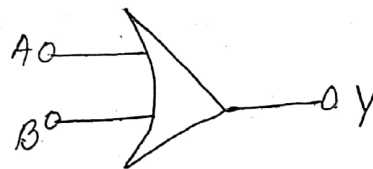

(b) Symbol of OR gate

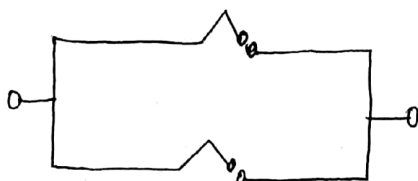


(c) Electrical equivalent

TRUTH TABLE

Input		output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

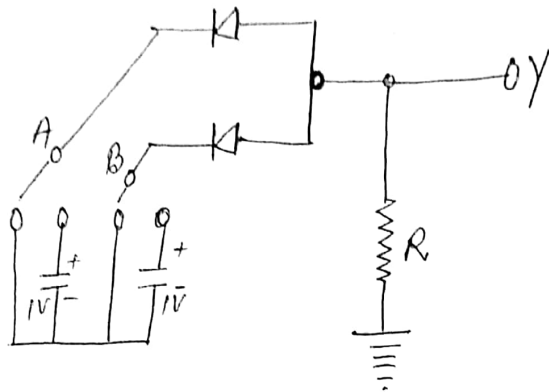
→ AND GATE:- It has two or more inputs and only one output. The output attains 1 state only when all inputs are in 1 state.



2. (a) Two input AND gate



(b) Symbol of AND gate

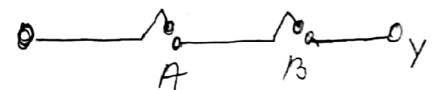


(c) Electrical Equivalent

TRUTH TABLE



Input		Output
A	B	$Y = A \cdot B$
0	0	0
1	0	0
0	1	0
1	1	1

→ NOT GATE (Negator or Inverter):-

It has one input & one output.

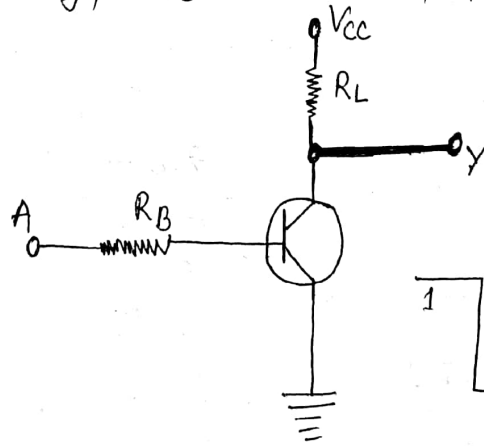

3(a) NOT CRT

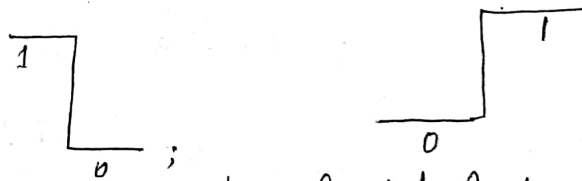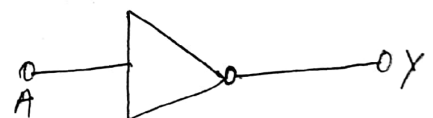

(b) Symbol of NOT gate

If input is low (0-state) output will be high (1-state) and vice-versa. This ckt. is called inverter or Negator or NOT gate.

If the input voltage is high enough to saturate the transistor (Fig-30a), the output is held at low value. If the input is low, the transistor becomes cut-off and output is high.

TRUTH TABLE

Input	Output
A	B
0	1
1	0